

Complete solutions to Exercise 13(c)

1. (i) By applying Kirchhoff's voltage law we have

$$iR + L \frac{di}{dt} = 0, \quad \frac{di}{dt} = -\frac{iR}{L}$$

(ii) Separating variables $\frac{di}{i} = -\frac{R}{L} dt$. Integrating

$$\int \frac{di}{i} = -\int \frac{R}{L} dt$$

$$\underbrace{\ln(i)}_{\text{by (8.2)}} = -\frac{R}{L} t + C$$


Substituting $t = 0, i = 1$

$$\ln(1) = 0 + C \text{ which gives } C = 0 \text{ because } \ln(1) = 0$$

$$\ln(i) = -\frac{R}{L} t$$

Taking exponentials gives $i = e^{-\frac{R}{L}t}$

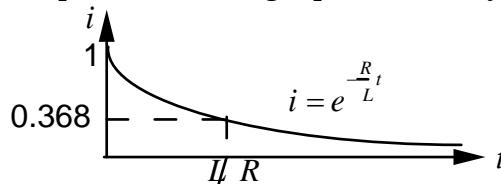(iii) Since R and L are positive the i graph is a decaying graph:



(iv) Substituting $t = \tau = L/R$ into i gives $i = e^{-\frac{R}{L} \cdot \frac{L}{R}} = e^{-1} = 0.368 \text{ A}$ (A = amp)

2. (i) Applying Kirchhoff's law we have

$$(\text{voltage across resistor}) + (\text{voltage across capacitor}) = 0$$

There is no applied voltage so the right hand side is zero. Let v be the voltage across the capacitor then by using (13.6) we have

$$iR + v = 0 \quad (*)$$

By (13.8) we have $i = C \frac{dv}{dt}$, substituting this into (*) gives a first order differential equation

$$CR \frac{dv}{dt} + v = 0 \text{ and so } \frac{dv}{dt} = -\frac{v}{RC}$$

(ii) Separating variables

$$\frac{dv}{v} = -\frac{dt}{RC}$$

Integrating $\int \frac{dv}{v} = -\int \frac{dt}{RC}$ gives

$$\underbrace{\ln(v)}_{\text{by (8.2)}} = -\frac{t}{RC} + D \quad (\dagger)$$

Substituting the initial condition $t = 0, v = E$ gives $\ln(E) = D$. Substituting this into (\dagger) yields

$$(8.2) \quad \int du/u = \ln|u|$$


$$(13.6) \quad v = iR$$

$$\ln(v) = -\frac{t}{RC} + \ln(E), \text{ rearranging } \underbrace{\ln\left(\frac{v}{E}\right)}_{\text{by (5.12)}} = -\frac{t}{RC}$$

Taking exponentials gives

$$\frac{v}{E} = e^{-\frac{t}{RC}} \text{ which gives } v = Ee^{-\frac{t}{RC}}$$

(iii) Similar to solution 1.

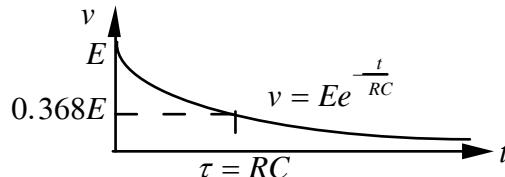

(iv) We have $v = Ee^{-RC/RC} = Ee^{-1} = 0.368E$

3. Similar to solution 2. Applying Kirchhoff's voltage law we have

$$E = iR + v \text{ where } v \text{ is the voltage across capacitor}$$

Substituting $i = C \frac{dv}{dt}$ from (13.8), gives $E = C \frac{dv}{dt} R + v = RC \frac{dv}{dt} + v$. Rearranging

$$\frac{dv}{dt} = \frac{E - v}{RC}$$

Separating variables

$$\frac{dv}{E - v} = \frac{dt}{RC}$$

Integrating both sides $\int \frac{dv}{E - v} = \int \frac{dt}{RC}$ gives

$$\underbrace{-\ln(E - v)}_{\text{by (8.42)}} = \frac{t}{RC} + D \quad (*)$$

Substituting the initial condition $t = 0, v = 0$ yields $-\ln(E) = D$. The remaining solution is very similar to 2. Thus we have

$$v = E(1 - e^{-t/RC})$$

4. (i) By Kirchhoff's law we have (v is the voltage across the capacitor)

$$15 = iR + v = (10 \times 10^3)i + v \quad (*)$$

We have $C = 10 \times 10^{-6}$ (because $\mu = 10^{-6}$), by (13.8) $i = C \frac{dv}{dt} = (10 \times 10^{-6}) \frac{dv}{dt}$.

Substituting for i into (*)

$$(10 \times 10^3)(10 \times 10^{-6}) \frac{dv}{dt} + v = 15$$

$$0.1 \frac{dv}{dt} + v = 15, \text{ rearranging } 0.1 \frac{dv}{dt} = 15 - v$$

(5.12) $\ln(A) - \ln(B) = \ln(A/B)$

(8.42) $\int \frac{f'(x)}{f(x)} dx = \ln|f(x)|$

(ii) Separating variables

$$\frac{0.1dv}{15-v} = dt, \quad \int \frac{0.1dv}{15-v} = \int dt$$

$$-0.1\ln(15-v) = t + C$$

Using the initial condition $t = 0, v = 0$ gives

$$-0.1\ln(15) = C$$

Thus by rearranging and using properties of logs we have

$$t = 0.1\ln(15) - 0.1\ln(15-v) = 0.1[\ln(15) - \ln(15-v)] \underset{\text{by (5.12)}}{\equiv} 0.1\ln\left(\frac{15}{15-v}\right)$$

Multiplying by 10:

$$10t = \ln\left(\frac{15}{15-v}\right)$$

Taking exponentials


$$e^{10t} = e^{\ln\left(\frac{15}{15-v}\right)} \underset{\text{by (5.16)}}{\equiv} \frac{15}{15-v}$$

Rearranging yields

$$15-v = \frac{15}{e^{10t}} = 15e^{-10t}$$

$$v = 15 - 15e^{-10t} = 15(1 - e^{-10t})$$

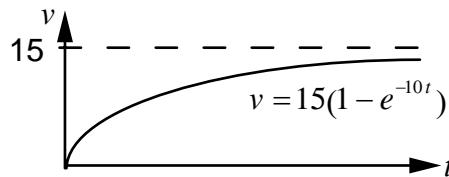(iii) As $t \rightarrow \infty, v \rightarrow 15$ and when $t = 0$ the voltage $v = 15(1 - 1) = 0$. Thus



(iv) By substituting the given values of t into $v = 15(1 - e^{-10t})$ we have

$$t = 0.1, v = 15 \times (1 - e^{-1}) = 15 \times 0.632, \quad 63.2\% \text{ of } 15 \text{ volts}$$

$$t = 0.2, v = 15 \times (1 - e^{-2}) = 15 \times 0.865, \quad 86.5\% \text{ of } 15 \text{ volts}$$

$$t = 0.3, v = 15 \times (1 - e^{-3}) = 15 \times 0.950, \quad 95.0\% \text{ of } 15 \text{ volts}$$

5. (i) Let v be the voltage across the capacitor then with $C = (3 \times 10^{-6})$:

$$i = C \frac{dv}{dt} = (3 \times 10^{-6}) \frac{dv}{dt}$$

By Ohm's law the voltage across resistor is $iR = (15 \times 10^3)i$. Substituting for i gives $iR = (15 \times 10^3)i = (15 \times 10^3)(3 \times 10^{-6}) \frac{dv}{dt} = 0.045 \frac{dv}{dt}$

Using Kirchhoff's law yields

$$(5.16) \quad e^{\ln(x)} = x$$

$$0.045 \frac{dv}{dt} + v = 15t^2$$


$$0.045 \frac{dv}{dt} = 15t^2 - v$$

5. (ii) Maple output is:

```
> de_5:=0.045*diff(v(t),t)=15*t^2-v(t);
de_5 := 0.045  $\left( \frac{d}{dt} v(t) \right) = 15 t^2 - v(t)$ 

> soln:=dsolve({de_5,v(0)=1},v(t));
soln := v(t) = 15 t^2 -  $\frac{27}{20} t + \frac{243}{4000} + \frac{3757}{4000} e^{\left(-\frac{200 t}{9}\right)}$ 

> plot(rhs(soln),t=0..0.5);
```

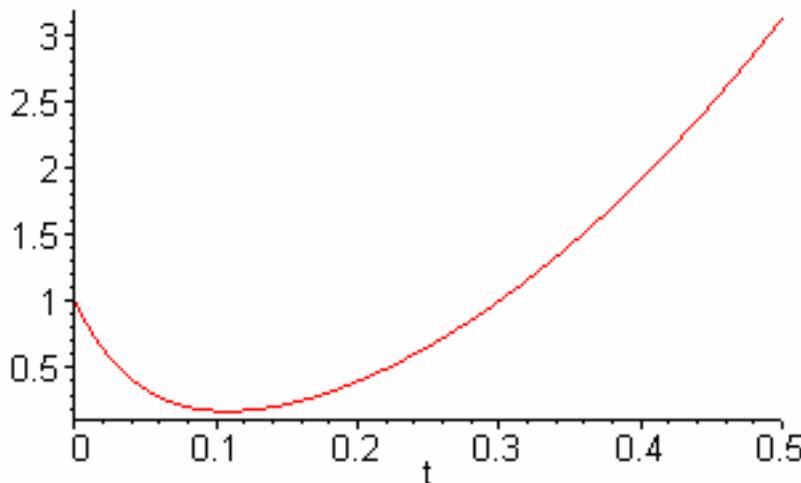

6. (i) Applying Kirchhoff's law gives $L \frac{di}{dt} + iR = 9 \sin(t)$. Substituting the given values in the circuit, $L = 0.1 \times 10^{-3}$, $R = 3 \times 10^3$:

$$(0.1 \times 10^{-3}) \frac{di}{dt} + (3 \times 10^3) i = 9 \sin(t)$$

$$(0.1 \times 10^{-3}) \frac{di}{dt} = 9 \sin(t) - (3 \times 10^3) i$$

Dividing both sides by 0.1×10^{-3} gives


$$\frac{di}{dt} = (90 \times 10^3) \sin(t) - (30 \times 10^6) i$$

(ii) Maple output is:


```
> de_6:=diff(i(t),t)=(90*10^3)*sin(t)-(30*10^6)*i(t);
de_6 :=  $\frac{d}{dt} i(t) = 90000 \sin(t) - 30000000 i(t)$ 

> soln:=evalf(dsolve({de_6,i(0)=1*10^(-3)},i(t)));
soln := i(t) = -0.10000000000 10^{-9} \cos(t) + 0.0030000000000 \sin(t)
+ 0.001000000100 e^{(-0.30000000000 10^8 t)}
```
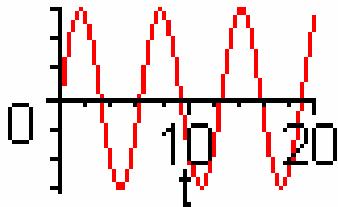
```
> plot(rhs(soln),t=0..20);plot(rhs(soln),t=0..2*10^(-7));
```



(a)

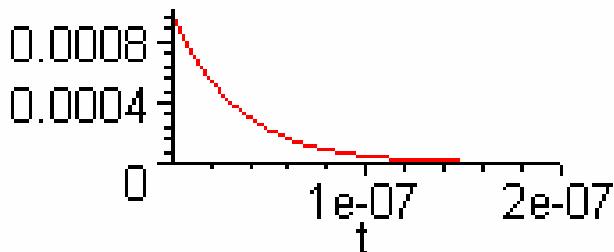

(b)

7. (i) Applying Kirchhoff's law gives $L\frac{di}{dt} + iR = 5\cos(100\pi t)$. Substituting the given values



$$\begin{aligned} (0.1 \times 10^{-3}) \frac{di}{dt} + (9 \times 10^3) i &= 5 \cos(100\pi t) \\ (0.1 \times 10^{-3}) \frac{di}{dt} &= 5 \cos(100\pi t) - (9 \times 10^3) i \\ \frac{di}{dt} &= (50 \times 10^3) \cos(100\pi t) - (90 \times 10^6) i \end{aligned}$$

Maple output is:

```
> de_7 := diff(i(t),t)=(50*10^3)*cos(100*Pi*t)-
(90*10^6)*i(t);
de_7 :=  $\frac{d}{dt} i(t) = 50000 \cos(100 \pi t) - 90000000 i(t)$ 

> soln := evalf(dsolve({de_7, i(0)=0}, i(t)));
soln := i(t) = -0.0005555555554 e(-0.90000000108t) + 0.0005555555555 cos(314.1592654 t)
+ 0.1939254724 10-8 sin(314.1592654 t)
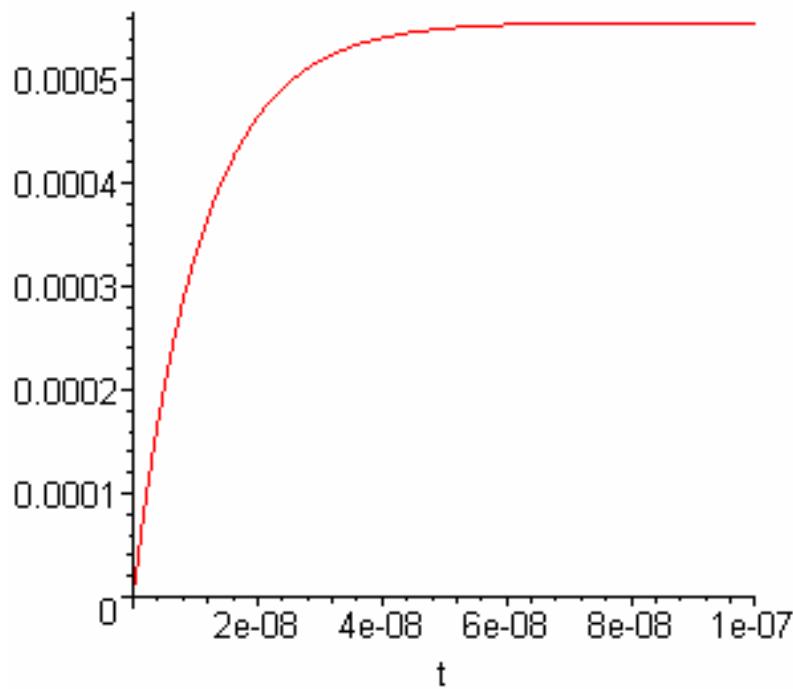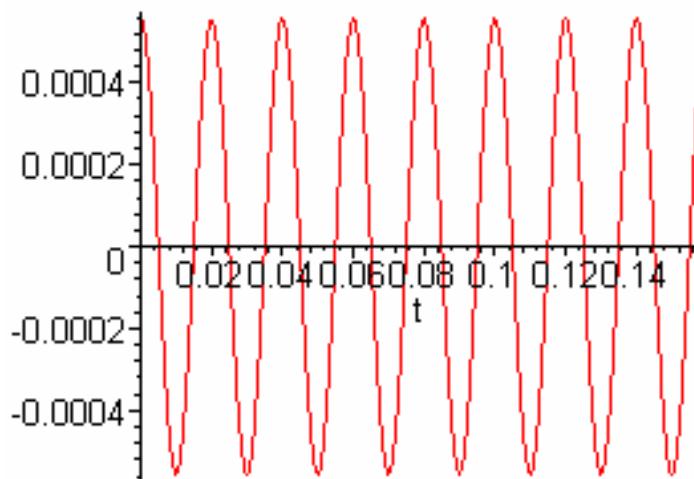
> plot(rhs(soln),t=0..Pi/20);plot(rhs(soln),t=0..10^(-7));
```



8. (i) Using Kirchhoff's law we have

$$(3 \times 10^{-3}) \frac{di}{dt} + (9 \times 10^3) i = 240 \sin(\omega t)$$

Dividing through by 3×10^{-3} gives

$$\frac{di}{dt} + (3 \times 10^6) i = \frac{240}{3 \times 10^{-3}} \sin(\omega t)$$

$$\frac{di}{dt} = (80 \times 10^3) \sin(\omega t) - (3 \times 10^6) i$$

(ii) Maple output is:

```
> de_8:=diff(i(t),t)=(80*10^3)*sin(omega*t)-(3*10^6)*i(t);
```



$$de_8 := \frac{d}{dt} i(t) = 80000 \sin(\omega t) - 3000000 i(t)$$

```

> soln:=evalf(dsolve({de_8,i(0)=0},i(t)));
soln :=


$$i(t) = \frac{80000. e^{(-0.3000000 \cdot 10^7 t)} \omega}{0.9000000000 \cdot 10^{13} + \omega^2} + \frac{80000. (-1. \cos(\omega t) \omega + 0.3000000 \cdot 10^7 \sin(\omega t))}{0.9000000000 \cdot 10^{13} + \omega^2}$$


> subs(omega=10000,rhs(soln));
0.00008888790128 e^{(-0.3000000 \cdot 10^7 t)} - 0.00008888790128 \cos(10000 t)
+ 0.02666637038 \sin(10000 t)
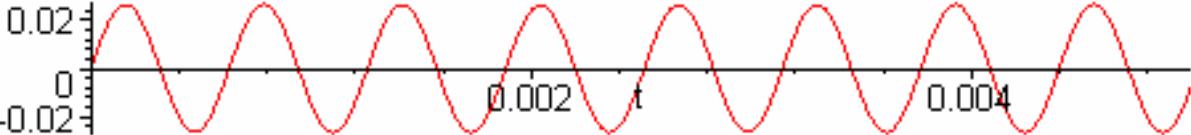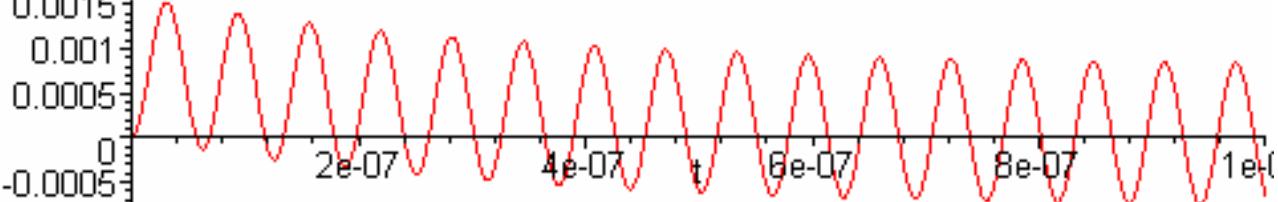
> plot(% ,t=0..0.005);

> subs(omega=100000000,rhs(soln)):plot(% ,t=0..1e-6);


```