

Total No. of Questions : 8]

PB3590

SEAT No. :

[Total No. of Pages : 3

[6260]-5

F.E. (All Branches)

BASIC ELECTRICAL ENGINEERING

(2019 Pattern) (Semester - I & II) (Credit System) (103004)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.
- 5) Use of non-programmable electronic pocket calculator is permitted.

Q1) a) Derive the expression for resonant frequency in a series RLC circuit. [4]

b) Prove that a pure inductor excited by sinusoidal voltage source never consumes any power. Draw the circuit diagram and write all necessary equations in steps. [6]

c) A voltage given by $v = 200 \sin \omega t$ is applied across 50Ω pure resistor. Obtain the expressions for instantaneous current and instantaneous power for this circuit. Also calculate rms value of current and power consumed [8]

OR

Q2) a) Define admittance of a circuit and hence draw the admittance triangle for a capacitive circuit. [4]

b) Obtain the expressions for instantaneous power and average power in a series R-L circuit excited by purely sinusoidal voltage. [6]

c) An R-C series circuit dissipates 100 W at 0.75 leading power factor when connected across single phase, 230 V, 50 Hz sinusoidal AC supply. Calculate: [8]

- i) current drawn
- ii) impedance in polar and rectangular form
- iii) resistance of the circuit and
- iv) value of capacitance

P.T.O.

Q3) a) Define the following terms in the context of polyphase AC circuits: [3]

- Symmetric AC supply
- Phase sequence
- Balanced Load

b) Derive the emf equations of a single phase transformer. [6]

c) A delta connected balanced load consists of three coils; each of resistance 6Ω and inductive reactance 8Ω supplied by $400V$, 3-phase AC. Determine [8]

- impedance per phase
- phase current and line current
- power factor of the circuit
- total power absorbed

OR

Q4) a) State any three advantages offered by an autotransformer. [3]

b) A direct loading test is performed on a 1 KVA , $230\text{V}/115\text{V}$, 50 Hz single phase transformer. Draw the connection diagram showing all necessary measuring instruments with appropriate ranges and determine the rated primary and secondary current. [6]

c) Obtain the relationship between line current and phase current, line voltage and phase voltage for 3-phase star connected balanced inductive load with the help of neat circuit diagram and phasor diagram. Assume phase sequence as RYB. [8]

Q5) a) A practical voltage source supplies a load resistance R_L . Draw the circuit representation and the V_L , I_L characteristics of this arrangement. [4]

b) Obtain the formulae for converting a delta connection of resistors into its equivalent star connection. [6]

c) Write the Kirchhoffs Voltage Law equations for the circuit shown in Fig. below and hence find the current through branch AB. All resistance values are in Ω . [8]

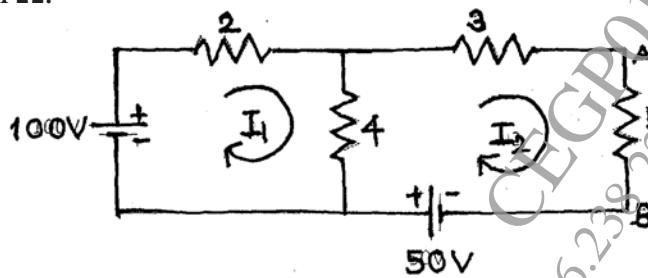


Fig. Q.5 (c)

OR

Q6) a) State and explain Kirchhoff's Laws for DC circuits. [4]
 b) Find the equivalent resistance obtained across B and C terminals for the circuit shown in Fig. below. All resistance values are in Ω . [6]

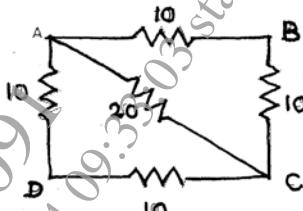


Fig. Q. 6 (b)

c) State Superposition Theorem. Explain the steps to apply Superposition Theorem for finding the current through branch A B of the circuit shown in fig. below. [8]

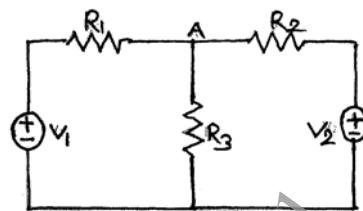


Fig. Q. 6 (c)

Q7) a) Specify the following in case of a Lithium Ion Battery: [3]
 i) Cathode material
 ii) Anode material
 iii) Electrolyte material
 b) Prove that $\alpha_2 = \frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$ where all terms have their usual meaning. [6]
 c) Define insulation resistance and hence derive an expression for insulation resistance of a single core cable. [8]

OR

Q8) a) Define resistance temperature coefficient (RTC) and write its unit. [3]
 b) An electric pump lifts 72 m^3 of water per hour to a height of 15 m. If the overall efficiency of the system is 70 %, find the input power. If the pump is used for 4 hours in a day, find the daily cost of energy at Rs. 10 per unit. [6]
 c) Explain the following in case of a Lead Acid Battery: [8]
 i) Construction and working
 ii) Maintenance procedure
 iii) Any two applications

X X X