

Total No. of Questions : 8]

PD4028

SEAT No. :

[6401]-1905

[Total No. of Pages : 4

First Year Engineering (All Branches)
BASIC ELECTRICAL ENGINEERING

(2019 Pattern) (Credit System) (Semester - I/II) (103004)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable additional data, if necessary.
- 5) Use of non-programmable calculator is allowed.

Q1) a) For the Resonance in RLC Series circuit-Comment on reactance's, impedance, current & power factor. **[4]**

b) The R-L circuit when supplied by 180V, 50 Hz ac voltage, the voltage drop across the inductance is 150 V. The current drawn by the circuit is 5 A. Calculate: **[6]**

- i) Inductive Reactance
- ii) Inductance
- iii) Resistance
- iv) Impedance
- v) Voltage across Resistance and
- vi) P.F.

c) A voltage of $V = V \angle 0^\circ$ V is applied across a R-L-C series circuit. Write the equation for impedance, current & comment on power factor --- when **[8]**

- i) $X_L > X_C$
- ii) $X_L < X_C$

Also draw the phasor diagram in each case.

OR

P.T.O.

Q2) a) Define and state the unit of [4]

- i) Admittance, susceptance,& conductance
- ii) Impedance

b) If $v = V_m \sin(\omega t)$ is applied across single phase circuit and current flowing through the circuit is $i = I_m \sin \left(\omega t + \frac{\pi}{2} \right)$. Draw the circuit diagram & derive the expression for average power consumed in the circuit. [6]

c) A Pure resistance of 15Ω is connected in series with a pure inductor of 25mH . This series circuit is connected across 230V , 50-Hz supply. Find [8]

- i) The Inductive Reactance
- ii) Impedance
- iii) Current
- iv) Power factor
- v) Phase angle
- vi) Voltage across Resistor
- vii) Voltage across inductor
- viii) Draw the phasor diagram

Q3) a) State the advantages of three phase systems over single phase system.[3]

b) Derive the EMF Equation of single-phase transformer. [6]

c) In a 3-phase Star-connected load, each phase has a an impedance of $(50+j32) \Omega$. This load is fed from three phase supply voltage of 400 V with frequency of 50Hz . Calculate: [8]

- i) Phase Voltage and Line Voltage;
- ii) Phase Current and Line Current;
- iii) Total Active Power, Reactive Power and Apparent Power consumed.

OR

Q4) a) State the different types of losses in the transformer. [3]

b) A 80 KVA, 3200/400V, 50Hz, single phase transformer has 111 turns on the secondary winding. Calculate [6]

- Number of turns on primary side
- Primary & Secondary full load current
- Cross sectional area of the core if the maximum flux density is 1.2T

c) Derive the relationship between the line current and phase current, line voltage and phase voltage, for a balanced three phase STAR connected load across three phase AC supply. Draw the circuit diagram & required phasor diagram. Assume phase sequence RYB and inductive load. [8]

Q5) a) Compare the ideal & practical voltage source by means of [4]

- definition
- Symbol & V-I characteristics.

b) Write the three steps to find current flowing through load resistance R_L using Thevenins Theorem for the circuit shown in Figure-5 (b). [6]

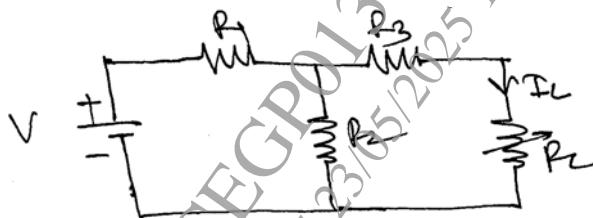


Figure-5 (b)

c) Derive the formulae to convert DELTA connected resistances into equivalent STAR connected resistances. Draw the circuit diagram in each case. [8]

OR

Q6) a) State and Explain Kirchhoffs Laws. [4]

b) Find the Resistance between terminal A and C. [6]

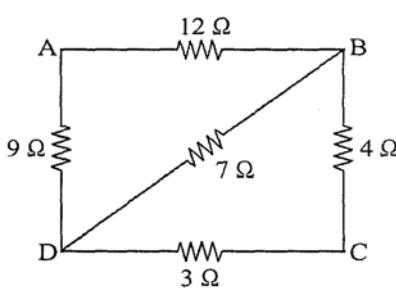


Figure-6 (b)

c) Find the current flowing through 5Ω by applying Super Position Theorem. [8]

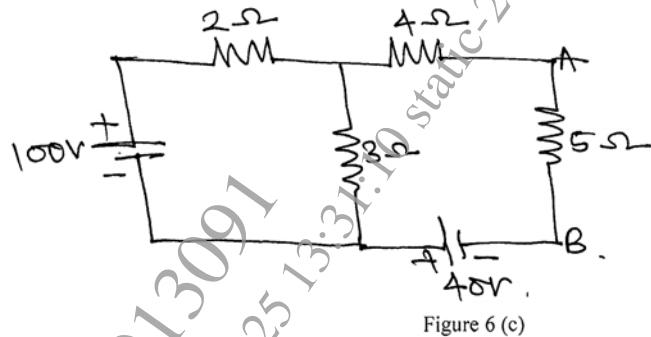


Figure 6 (c)

Q7) a) Comment on effect of increase in temperature on Resistance of [3]

- i) metallic conductor
- ii) alloys &
- iii) insulators

b) Explain the construction and working of Lead acid battery. [6]

c) Derive the expression of insulation resistance of the single core cable. Draw the cut section diagram & label it. [8]

OR

Q8) a) State the 3 applications of lithium ion battery. [3]

b) With usual notations derive the expression [6]

$$\alpha_2 = \frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$$

c) Find the current flowing at the instant of switching 40 W, 240 V filament lamp. The temperature coefficient of resistance of filament is 5.5×10^{-3} per degree Celsius at 20°C. The working temperature of lamp is 2000°C. Also find the working current & compare it with starting current. [8]

X X X