

Total No. of Questions : 8]

SEAT No. :

PC-1679

[Total No. of Pages : 4

[6351]-105

F.E. (All Branches)

**BASIC ELECTRICAL ENGINEERING**  
**(2019 Pattern) (Semester - I/II) (103004)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) Attempt Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.
- 5) Use of non-programmable electronic pocket calculator is permitted.

**Q1)** a) Derive the expression for resonant frequency in case of an RLC series circuit. [4]

b) Obtain an expression for instantaneous current in a pure capacitance excited by a sinusoidal voltage source. Hence obtain the instantaneous and average power. [6]

c) An AC voltage given by  $e = 200 \sin 100\pi t$  is applied to a load having  $R = 200 \Omega$  in series with  $L = 638 \text{ mH}$ . Find (i) Expression for current (ii) power consumed by load (iii) Reactive power of load (iv) voltage across R and L. [8]

OR

**Q2)** a) Define admittance of an AC circuit. Write the admittance in complex form for an inductive circuit and state the meaning of each term. [4]

b) Obtain the expression for average power drawn by an R-L series circuit when excited with a sinusoidal voltage source. Hence draw the power triangle. [6]

c) A resistance of  $10 \Omega$  is connected in series with a pure capacitor of  $150 \mu\text{F}$ . The circuit is connected across a  $100\text{V}, 50\text{Hz}$  supply. Calculate (i) impedance of circuit (ii) power factor of circuit (iii) current in the circuit (iv) voltages across resistor and capacitor (v) active, reactive and apparent power in the circuit. [8]

*P.T.O.*

**Q3)** a) Define the following terms as applicable to a three phase AC system :[3]

- Symmetric AC supply
- Phase sequence
- Balanced load

b) Derive an expression for emf induced in a single phase transformer. [6]

c) A balanced 3- phase load consists of three coils, each of series combination of  $6 \Omega$  resistance and  $8 \Omega$  inductive reactance. Determine the line current and power absorbed when the coils are (i) star-connected and (ii) delta-connected across 400V, 3-phase supply. [8]

OR

**Q4)** a) State and explain principle of working of a single phase transformer. [3]

b) State the relationship between line and phase voltage, Line and phase current in case of three phase star connected balanced load. Hence, obtain the expression for 3-ph power. [6]

c) A direct loading test is performed on a 1 kVA, 230 V/115 V, 50 Hz single phase transformer. Draw the connection diagram involving all necessary measuring instruments and determine the following : [8]

- Full load primary and secondary current
- Range of ammeters and voltmeters
- Range of wattmeters

**Q5)** a) State and explain Kirchhoff's Laws in the context of DC circuits. [4]

b) Obtain the formulae for converting a set of given delta connected resistances into equivalent star connection. [6]

c) Using Thevenin's theorem, find the current through  $10 \Omega$  resistor in following circuit. [8]

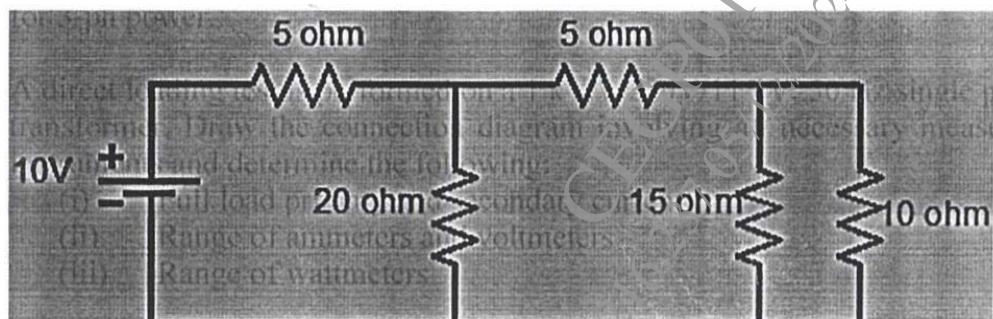


Fig. Q.5

OR

**Q6)** a) What is an ideal voltage source? Mention the following for an ideal voltage source : [4]

- Diagrammatic representation
- Internal resistance value
- Voltage and output current characteristics

b) State the Superposition Theorem and apply it for finding current through AB for the circuit given below. Fig 6(b) [6]

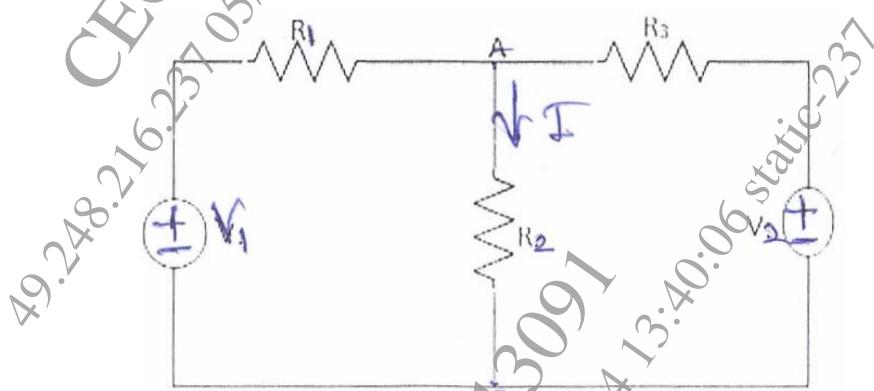


Fig 6(b)

c) Determine the effective resistance between terminals A and B for the circuit shown in Fig. below. [8]

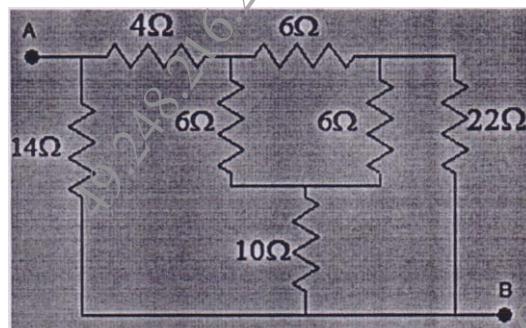


Fig. Q.6(c)

**Q7)** a) Explain the concept of depth of discharge (DoD) of a battery in brief. [3]

b) Derive an expression for insulation resistance of a single core cable. [6]

c) Explain the construction and working of a Lead Acid Battery and state it's any two applications. [8]

OR

**Q8)** a) State any three major precautions taken while maintaining a Lead Acid Battery. [3]

b) Explain the construction and working of a Lithium-Ion Cell and state it's any two applications. [6]

c) The electrical installation in a house is utilised as mentioned below:

- 5 Tubelights, 18W each, for 12 hrs a day
- 3 ceiling fans, 60W each, for 10 hrs a day
- 2 electric ovens, 1.2 KW each, for 2 hrs a day
- 2 electric geysers, 3 KW each for 30 minutes a day

Calculate (i) Daily energy consumption in kWh (ii) total cost of energy at a rate of Rs.6 per unit for 30 days. [8]