

Total No. of Questions : 4]

**PC378**

SEAT No. :

[Total No. of Pages : 1

**[6358]-109**

**F.E. (Insem)**

**BASIC ELECTRONICS ENGINEERING**  
**(2019 Pattern) (Semester - I) (104010)**

*Time : 1 Hour]*

*[Max. Marks : 30]*

*Instructions to the candidates:*

- 1) Answer Q.1 or Q.2, Q.3 or Q.4.
- 2) Assume suitable data if necessary.

**Q1)** a) Explain forward biasing of P-N Junction diode with its V-I characteristics. [5]

b) Compare half wave, center tapped transformer full wave rectifier and Bridge full wave rectifier. [5]

c) Draw and explain voltage regulator circuit using zener diode. [5]

OR

**Q2)** a) What is depletion region? Explain the effect of forward biasing and reverse biasing of P-N Junction diode on depletion region. [5]

b) For Bridge full wave rectifier, applied input voltage is  $10\sin \omega t$ , calculate average output voltage, RMS voltage and PIV rating of diode used. [5]

c) Explain principle of operation and construction of photodiode. List its applications. [5]

**Q3)** a) Explain BJT as an amplifier in common Emitter configuration. [5]

b) Explain construction and operation of N-channel EMOSFET. [5]

c) For an inverting amplifier using Op-Amp if  $R_f = 10k\Omega$ ,  $R_i = 1k\Omega$  and  $V_{cc} = \pm 15V$  calculate 'V<sub>o</sub>' for  $V_{in} = 100\text{ mv}$ . [5]

Comment on the phase relation between input and output voltage.

OR

**Q4)** a) Explain regions of operation of transistor with respect to biasing conditions. For BJT, if  $J_B = 10\text{ }\mu\text{A}$  and  $I_E = 1\text{ mA}$  [5]  
Calculate value of  $I_C$  and  $\beta$ (Beta).

b) Compare BJT and MOSFET. [5]

c) Draw and explain Op-amp as inverting amplifier. Write the expression for voltage gain. [5]