

B.Tech-1st
Basic Electrical Engineering

Full Marks : 50

Time : $2\frac{1}{2}$ hours

Answer all questions

The figures in the right-hand margin indicate marks

Symbols carry usual meaning

1. Answer all questions : 2 × 5

(a) Two filament lamps A and B take 0.8 A and 0.9 A respectively when connected across 110 V supply. Calculate the value of current when they are connected in series across a 220 V supply.

(b) Find the effective value of

$$v(t) = 50 + 70.7 \cos(377t) V.$$


(Turn Over)

(2)

- (c) What are the different speed control methods of DC motor ?
- (d) State the EMF equation for a single phase transformer with proper notion.
- (e) What are energy sources used in India ? Give some examples.

2. (a) Using Source conversion technique find the load current I_L in the circuit shown


4

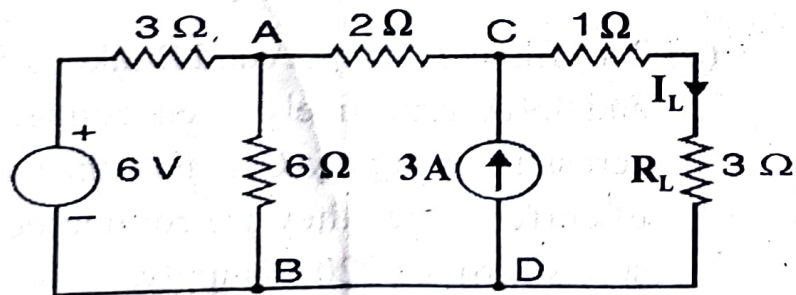

- (b) Using superposition Theorem find the current through 23 Ω .

4


(3)

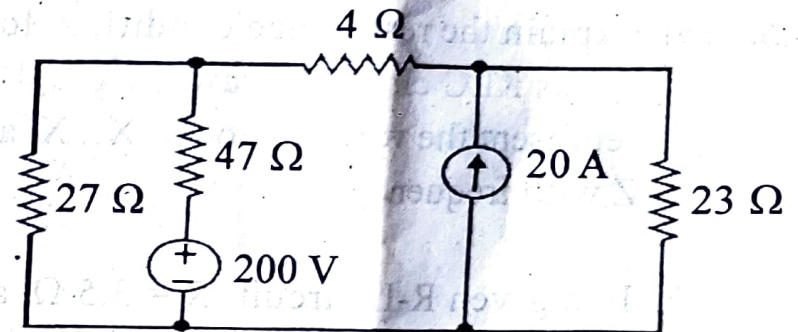

Or

- (a) Using Norton's Theorem find current through 5 Ω resistor in the circuit shown

4

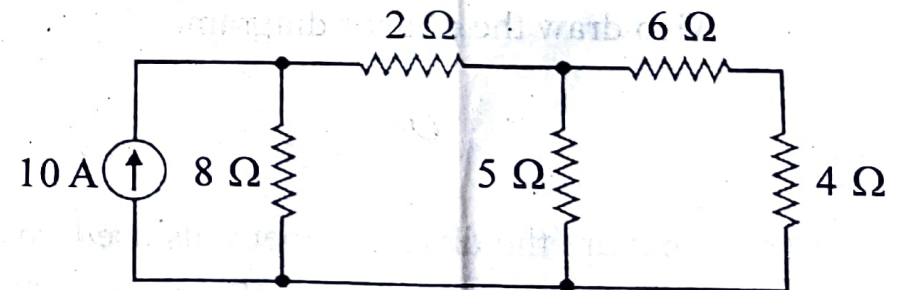

- (b) State & Explain Maximum Power Transfer Theorem.

4

3. (a) Explain the resonance condition for a series RLC circuit. Draw the graph to represent the variation of R , X_L , X_C and Z with frequency. 4

(b) In a given R-L circuit, $R = 3.5 \Omega$ and $L = 0.1 \text{ H}$. 4

Find :

- (i) the current through the circuit and
- (ii) power factor if a 50-Hz voltage $V = 220 \angle 30^\circ$ is applied across the circuit.

Also draw the phasor diagram.

Or

(a) What are the different methods used to measure power in a three-phase circuit? Explain the two watt-meter method with proper diagram. 4

(b) A balanced star-connected load of $(8+j7) \Omega$ per phase is connected to a balanced 3-phase 400 V supply. Find the line current, power factor, power and total apparent power. 4

4. (a) Derive torque equation of DC motor. 4

(b) A coil is wound uniformly with 300 turns over a steel ring of relative permeability 900 having a mean diameter of 20 cm and cross section of 2 cm diameter. Current in the coil is 5A. Calculate (i) MMF, (ii) Reluctance (iii) field intensity in the ring (iv) flux (v) permeance. 4

Or

(a) What is hysteresis loss? In which type of machine it occurs? On which factors it depend? 4

- (b) A 4 pole wave wound armature has 720 conductors and is rotated at 1000 rpm. If useful flux is 20 mWb, Calculate the generated voltage. 4
5. (a) Find the full-load rotor slip and frequency of the induced voltage at rated speed in a four-pole induction motor with ratings : 230 V; 60 Hz; full-load-speed : 1,725 r/min. 4
- (b) How power is transferred in a single phase transformer? Why the frequency remains constant? 4
- Or
- (a) A 220-V DC shunt motor has an armature resistance of 0.2 ohm and a rated armature current of 50 A. Find (i) The voltage generated in the armature, (ii) The power developed. 4

- (b) What is the principle of operation of a DC generator? Explain the motoring operation in a DC generator. 4
6. (a) What are the available sources of energy? Why is electrical energy so popular? 4
- (b) Give a brief idea about the electrical power system and its components. 4
- Or
- (a) Why do we go for poly-phase AC system over DC system? 4
- (b) Give a general layout of a hydro-electric power station. 4