

Total Pages : 8

**B.Tech-3rd (EE)**

**Analog and Digital Electronic Circuits**

*Full Marks : 50*

*Time : 2.30 hours*

*Answer all questions.*

*The figures in the right-hand margin indicate marks.*

*Symbols carry usual meaning.*

1. Answer *all* questions : 2 × 5

- (a) Draw the hybrid equivalent model of a transistor in common emitter configuration.
- (b) State the characteristics of an ideal OPAMP.
- (c) Draw the transfer characteristic of FET.
- (d) Design a half adder circuit with truth table.

( Turn Over )

( 2 )

(e) Differentiate between combinational and sequential logic circuits.

2. (a) For a DC bias with voltage feedback circuit of  $V_{CC} = 10\text{ V}$ ,  $\beta = 90$ ,  $R_C = 4.7\text{ k}\Omega$ ,  $R_E = 1.2\text{ k}\Omega$ , resistance across collector and base =  $250\text{ k}\Omega$ . Draw the circuit and find  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CE}$ ,  $V_B$ ,  $V_C$ ,  $V_E$ ,  $I_{Csat}$ .

4

(b) Draw an emitter follower circuit and derive the expression for input impedance  $Z_i$  of the circuit.


4

Or

(a) For the network below determine (i)  $Z_p$ , (ii)  $Z_o$ , (iii)  $A_v$ , (iv)  $A_i$ .

4

( 3 )

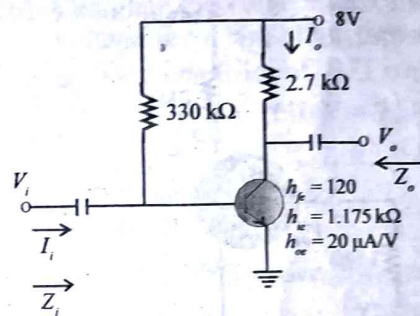

(b) Draw the frequency response curve and explain the Miller effect on gain at high frequencies.

4

3. (a) Determine the following for the network given below

4


(i)  $V_{GS}$

(ii)  $I_D$

(iii)  $V_{DS}$

(iv)  $V_G$

( 4 )

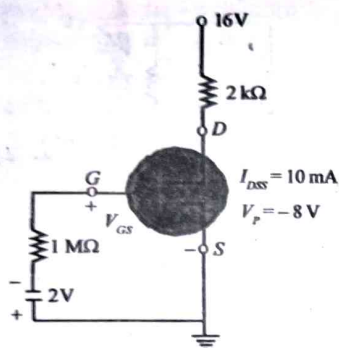

- (b) Discuss the magnitude of gain response curve of a RC coupled amplifier and find out its bandwidth. 4

Or

- (a) With a neat diagram analyze an FET in Self-bias configuration. 4

( 5 )

- (b) Calculate the voltage gain and output voltage for a two stage cascaded RC coupled amplifier of BJT parameters  $V_{CC} = 20 \text{ V}$ ,  $\beta = 200$ ,  $V_i = 25 \mu\text{V}$ ,  $R_1 = 15 \text{ K}\Omega$ ,  $R_2 = 4.7 \text{ K}\Omega$ ,  $R_C = 2.2 \text{ K}\Omega$ ,  $R_E = 1 \text{ K}\Omega$ . 4

4. (a) Design a first-order, low-pass filter using OPAMP. State its voltage gain and cutoff frequency. 4


- (b) What is a class A power amplifier ? Derive its conversion efficiency. 4

Or

- (a) What range of output voltage is developed in the circuit below. 4



( 6 )

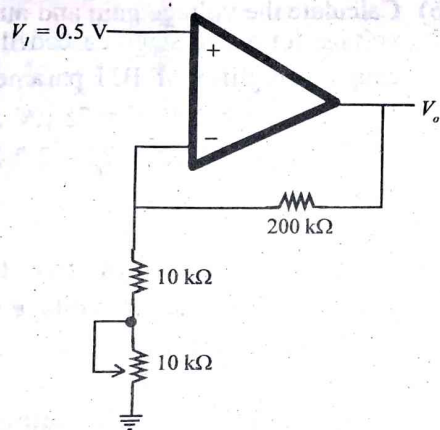

(b) Discuss OPAMP as an integrator and differentiator. 4

5. (a) Simplify the following Boolean function  $F$ , together with the don't care conditions  $d$ . 4

$$F(A, B, C, D) = \sum_m(1, 3, 5, 7, 9, 15)$$

$$d(A, B, C, D) = \sum_m(4, 6, 12, 13)$$

( 7 )

(b) Given the Boolean function 4

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

(i) Obtain the truth table of the function.

(ii) Simplify the expression.

(iii) Draw the logic diagram using logic gates.

Or

(a) Explain the BCD addition rules and perform the BCD addition for the decimal number  $72 + 35$ . 4

(b) Convert the following expressions into sum of products and product of sums : 4

(i)  $(AB + C)(B + C'D)$

(ii)  $x' + x(x + y')(y + z')$

6. (a) What are the different types of shift register. Discuss the operation of 4-bit SISO shift register using J-K flip-flop. 4

(b) What is Race-around Condition of J-K flip-flop ? Describe J-K flip-flop operation with logic diagram and truth table. 4

*Or*

(a) Implement the following expressions using a multiplexer. 4

(i)  $Y(A, B, C) = \Sigma_m(0, 1, 2, 6, 7)$

(ii)  $Y(A, B, C) = \prod_M(0, 1, 4, 5)$

(b) Implement a 4:16 decoder using 2:4 decoders. 4