

B.Tech-3rd (EE)

Network Theory

Full Marks : 50

Time : 2.30 hours

Answer **all** questions.

The figures in the right-hand margin indicate marks.

Symbols carry usual meaning.

1. Answer *all* questions : 2 × 5

(a) Derive the expression of coefficient of coupling.

(b) Find the value of C in the circuit shown in Figure 1 to get resonance.

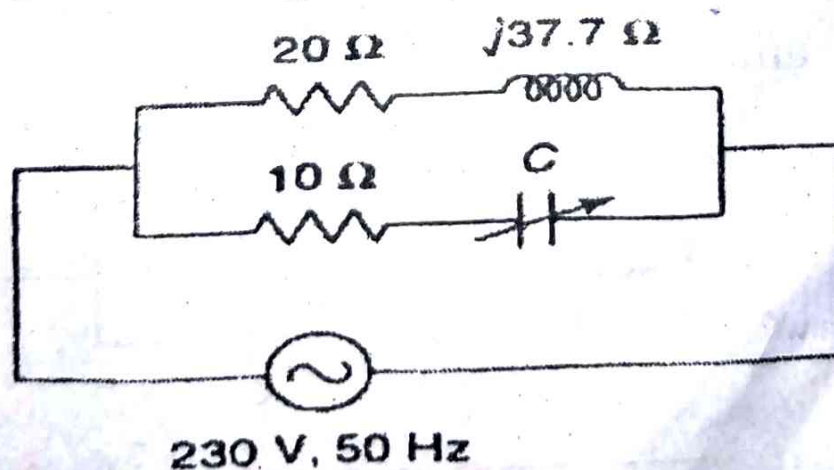


Figure 1

(Turn Over)

(2)

(c) What are the conditions of symmetry and reciprocity in a transmission two-port network?

(d) What are the necessary conditions of stability of a network function? Check whether the system with characteristics polynomial $P(s) = s^4 + 3s^3 + 2s^2 + 5s + 1$ is stable or not?

(e) What are the different types of filters? Mention the frequency limits for their pass band and attenuation band.

2. (a) Find the value of R_1 such that the following circuit given in Figure 2 is resonant. Here, $R_2 = 10 \Omega$, $\omega L = j6 \Omega$ and $\omega C = -j4 \Omega$. 4

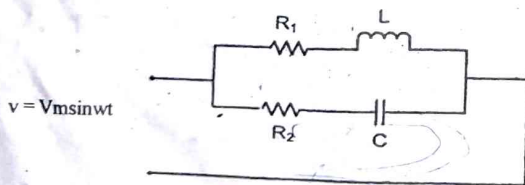


Figure 2

B.Tech-3rd(EE)/N.T

(Continued)

(3)

(b) (i) Derive the Transient Response of series RL-circuit with D.C excitation.

(ii) In the circuit shown in Figure 3, determine the complete solution for the current when switch is closed at $t = 0$, applied voltage is

$$V(t) = 20 \cos\left(100t + \frac{\pi}{4}\right), \text{ resistance}$$

$$R = 10 \Omega \text{ and capacitance } C = 2 \mu\text{F}. \quad 4$$

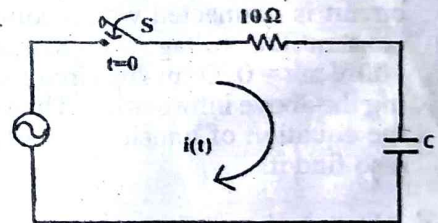


Figure 3

Or

(a) Find the current I_x resistor shown in Figure 4 using Thevenin's equivalent network. 4

B.Tech-3rd(EE)/N.T

(Turn Over)

(4)

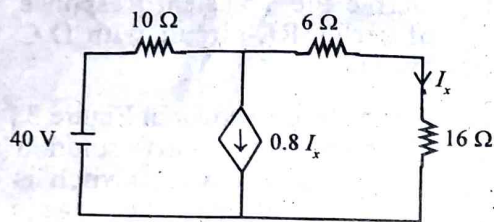


Figure 4

- (b) A circuit consists of a resistance with $25\ \Omega$, an inductance with $50\ \text{mH}$ and a capacitance with $20\ \mu\text{F}$ in Series. The circuit is connected with a source of constant DC voltage with magnitude $100\ \text{V}$ at $t = 0$. Draw the circuit showing the above information. Then write the equation of transient current and also find it.

4

3. (a) What are the different types of two-port networks? Define their dependent and independent parameters. Write the expression of equivalent parameters in case of two series networks.

4

(5)

- (b) How a two-port network is different from one-port network? The given $ABCD$ parameters of the two-port network are, $A = 2$, $B = 0.9$, $C = 1.2$, $D = 0.5$. Find its equivalent Y -parameters.

4

Or

- (a) Find the h -parameters for the circuit shown in Figure 5.

4

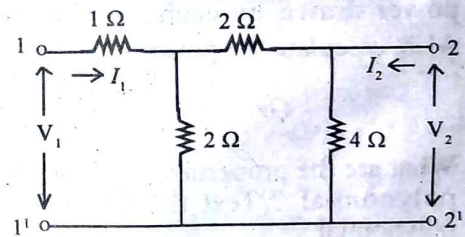


Figure 5

- (b) Derive the expression for Image impedances in terms of $ABCD$ parameters.

4

(6)

4. (a) Two coupled coils have $K = 0.6$, $N_1 = 450$ turns, $N_2 = 750$ turns and mutual flux being 0.9 Weber. If primary current is 10 A, then find the primary and secondary coil inductances. 4
- (b) Three impedances Z_A , Z_B and Z_C are connected in star. They are supplied from a source with 3- ϕ , 50 Hz and 100 V. Calculate the line current, power drawn by each impedance. Also, calculate the power factor. 4

Or

- (a) What are the properties of a Hurwitz polynomial? Test the following polynomial.

$$P(s) = s^4 + 11s^3 + 39s^2 + 51s + 20 \quad 4$$

- (b) Explain two-wattmeter method for power and power factor calculation of a balanced three-phase load. 4

(7)

5. (a) What do you mean by positive real function? What are its properties? 4
- (b) Driving point impedance of a network is given by $Z(s) = \frac{s^3 + 3s}{s^2 + 1}$. Realize the network. 4

Or

- (a) Discuss Foster's canonical form for LC network synthesis. 4
- (b) The driving point impedance is given by

$$Z(s) = \frac{s(s^2 + 2)(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$$

Obtain the first form of Cauer's network. 4

6. (a) For the graph shown in Figure 6 find incidence and cut set matrices. 4

(8)

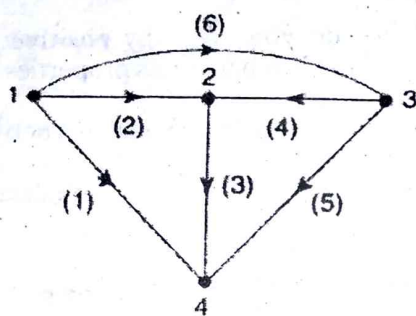


Figure 6

- (b) Define the following with appropriate diagrams.
 (i) Branch (ii) Loop (iii) Node
 (iv) Tree and (v) Co-tree. 4

Or

- (a) For the circuit shown in Figure 7, draw the oriented graph and write the (i) incidence matrix, (ii) tie-set matrix, and (iii) f-cut-set matrix. 4

(9)

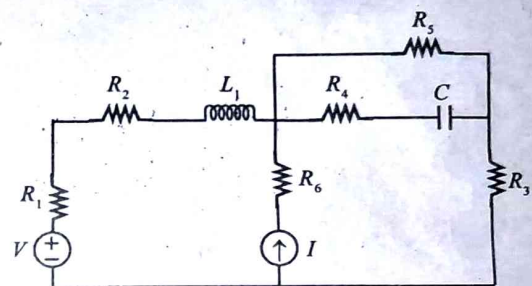


Figure 7

- (b) Draw the oriented graph for the following reduced incidence matrix. Write its (i) incidence matrix and (ii) tie-set matrix. 4

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$