

B.Tech-3rd(EEE)

Analog Electronic Circuit

Full Marks : 50

Time : $2\frac{1}{2}$ hours

Answer all questions

The figures in the right-hand margin indicate marks

Symbols carry usual meaning

Any supplementary materials to be provided

1. Answer all questions : 2 × 5

(a) What is operating point of an amplifier ?
Write its significance.

(b) What is stability factor ?

(c) What is pinch of voltage ?

(d) Draw the Darlington circuit.

(e) State and explain Barkhausen's criteria.


(Turn Over)

(2)

2. (a) What is biasing ? Explain Emitter biasing with neat sketch. 4
- (b) Explain the output characteristic of CE transistor. Draw its load line. 4


Or

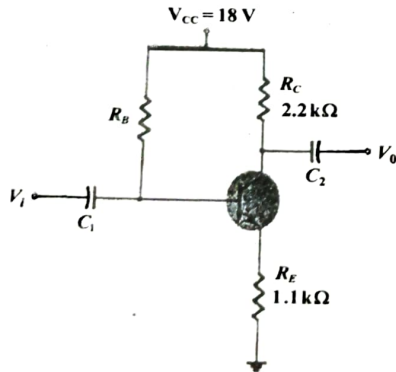- (a) Discuss voltage divider bias configuration of BJT amplifier using exact method and approximate method with suitable circuit diagram. 4
- (b) Determine I_C , V_{CE} and suitable I_{CQ} and V_{CEQ} . Given $R_B = 430 \text{ k}\Omega$. 4




(3)

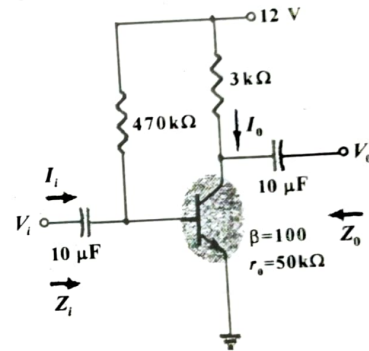3. (a) Determine the following for the above circuit. Given $r_o = \infty$ 4
 (i) r_e , (ii) A_v , (iii) Z_o , (iv) Z_i



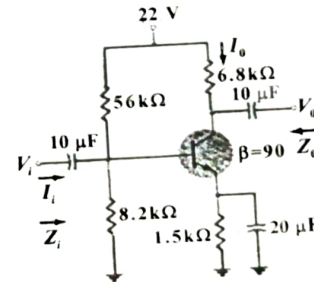- (b) Determine the following for the above circuit. Given $r_o = \infty$ 4
 (i) r_e , (ii) A_v , (iii) Z_o , (iv) Z_i




(4)

Or

(a) Determine the following for the above circuit. Given $r_o = \infty$

4

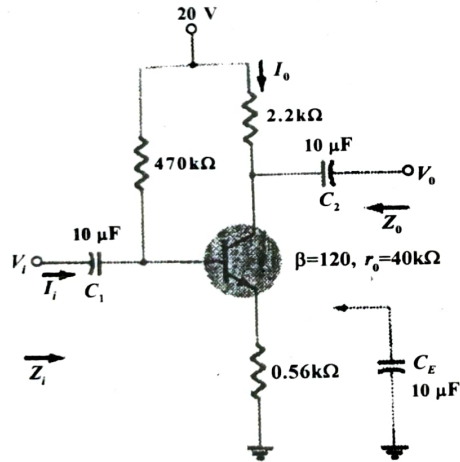(i) r_e , (ii) A_v , (iii) Z_o , (iv) Z_i




(b) Determine the following for the above circuit. Given $r_o = \infty$

4

(i) r_e , (ii) A_v , (iii) Z_o , (iv) Z_i

(5)

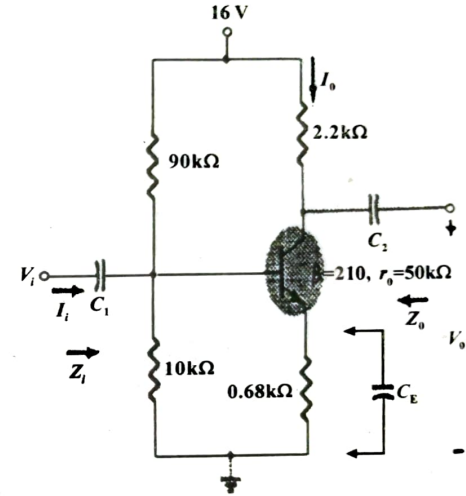

4. (a) How FET differs from BJT ? Explain Self Bias circuit for Depletion type MOSFET.

5


(b) Sketch the transfer characteristics for an p-channel depletion type MOSFET with $I_{DSS} = 10\text{mA}$ and $V_p = -4\text{V}$.

3

(6)

Or

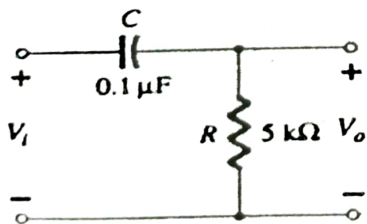- (a) Discuss hybrid- π common emitter transistor model. 4
- (b) Discuss a.c. analysis of JFET amplifier fixed bias configuration. 4
5. (a) Explain the frequency response of RC coupled amplifier. Compare it with that of transformer coupled and direct-coupled amplifiers. 4
- (b) Determine the break frequency and gain at $A_{v(dB)} = -6\text{dB}$. Sketch the frequency response curve showing asymptotes and -3dB point. 4



(7)

Or

Demonstrate Miller effect capacitance for an inverting amplifier. 8

6. Explain the concept of positive feedback. With a neat diagram discuss various oscillator circuits. 8

Or

How do you differentiate between voltage amplifier and power amplifier? Compare class A and Class B amplifiers. 8