

VEER SURENDRA SAI UNIVERSITY OF TECHNOLOGY (VSSUT), ODISHA
Odd Mid Semester Examination for session 2024-25

COURSE NAME:

SEMESTER: 3rd

BRANCH NAME: EEE

SUBJECT NAME: Analog Electronics Circuit

FULL MARKS: 30

TIME: 90 Minutes

Answer All Questions.

The figures in the right hand margin indicate Marks. Symbols carry usual meaning.

Q1. Answer all Questions.

[2 × 3]

- a) What are the biasing conditions for different operating regions of BJT?
- b) Explain Emitter follower circuit.
- c) Write output current equation for Depletion and Enhancement type MOSFET.

Q2. a) What is biasing? Explain Emitter-biasing circuit with neat diagram.

[8]


- b) For emitter bias network, determine I_C , V_{CE} , V_C , V_E

Given $R_B = 430 \text{ k}\Omega$, $V_{CC} = 20\text{V}$

$R_C = 2 \text{ k}\Omega$,

$R_E = 1 \text{ k}\Omega$,

$\beta = 50$

 

OR

- a) Explain fixed bias circuit with neat diagram. Compare the stability criteria with Emitter bias.
- b) What is quiescent point? What is the preferred location of the operating point for faithful amplification and why?

[8]

Q3. Explain the h-parameter model and find A_v , A_i , Z_i , Z_o for common emitter fixed bias configuration.


OR

Explain the r_e -model and compute the parameters for common emitter fixed bias configuration.

Q4. a) Sketch the transfer characteristics of an n-channel depletion type MOSFET with $I_{DSS} = 10\text{mA}$ and $V_p = -4\text{V}$.

[8]

 - b) Determine the following for the circuit. Given $I_{DSS} = 10 \text{ mA}$, $V_P = -8 \text{ V}$
i) V_{GSQ} , ii) I_{DQ} , iii) V_{DS} , iv) V_D



OR

Compare fixed bias and emitter bias for n-channel JFET using DC analysis.