

**B.Tech-3rd(EEE)**

**Network Theory**

*Full Marks : 50*

*Time :  $2\frac{1}{2}$  hours*

**Answer all questions**

*The figures in the right-hand margin indicate marks*

**Symbols carry usual meaning**

**Any supplementary materials to be provided**

1. Answer *all* questions : 2 × 5

(a) Considering a live conductor, (i) State whether the change in flux linkage ( $\delta\lambda$ ), will be uniform or not if the core of conductor is made by a ferromagnetic material, and (ii) Is superposition theorem applicable here or not ?

(b)  $[Z_{11}] = [Y_{11}]^{-1}$ ; The statement is valid or invalid, and why ?

( Turn Over )

- (e) In which condition, a second order circuit settles fast after changing the state of switch? Justify.
- (d) Write the necessary and sufficient conditions for a rational function with real coefficients to be a positive real function?
- (e) Define the term 'Linked Tree' and 'Oriented Graph' in graph theory.
2. (a) A first order R-L circuit is connected with a voltage source  $v(t) = V\sin(\omega t + \phi)$  through a switch ( $k$ ). The switch is closed/ established a contact with the network at  $\omega t = 90^\circ$  and  $\phi = 0$ . (i) Assuming the circuit is driven by the linear differential equations, draw the circuit and find its response. (ii) How shall you be able to control the transient/ steady state conditions of the network? Justify.

4

- (b) At time  $t = 0+$ , the switch is closed considering a generator's voltage expressed by  $v(t) = V \sin \sqrt{t/MC}$  to the circuit shown in Fig. 1; All the symbols have their conventional notations used in the network and expressions.

4

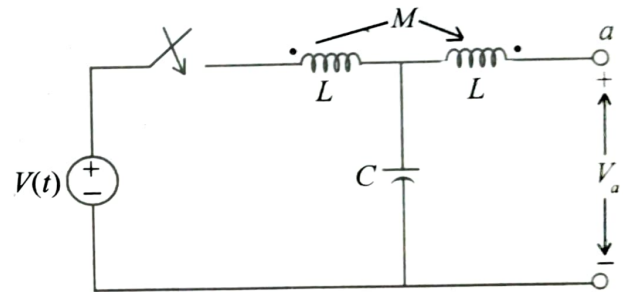


Fig. 1

Show that;

$$V_a(0+) = 0; \frac{dV_a(0+)}{dt} = \frac{V}{L} \sqrt{\frac{M}{C}},$$

$$\text{and } \frac{d^2 V_a(0+)}{dt^2} = 0$$

Or

- (a) At time  $t = 0+$ , the switch is closed considering the circuit is energized using a voltage source,  $v(t) = 5V$  to a R-C circuit; find the response of the circuit

$i(t)$ ,  $\frac{di(t)}{dt}$  at time  $t = 0+$  if values of  $R = 1-\Omega$ ,  $C = 1-F$ . 4

- (b) Fig. 2 shows a peicwise linear characteristic. Let  $x = q_c$  and  $y = v_c$  so that the characteristic represents a nonlinear capacitor. If the voltage applied to the capacitor, plot the corresponding  $i_c(t)$ . 4


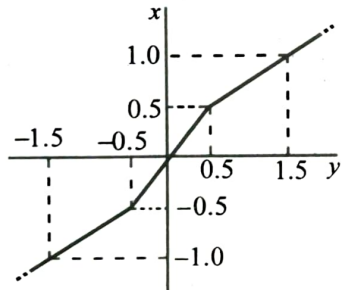


Fig. 2

3. (a) Find the Z-parameters of the Fig. 3 shown in below. 4

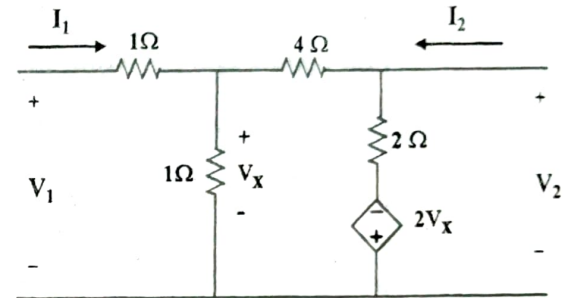

[Fig. 3]

- (b) If a small signal (incremental analysis) of a two-port model is represented by Fig. 4, then answer following : 4

$$\begin{aligned} v_b &= h_{ie} i_b + h_{re} v_c \\ i_c &= h_{fe} i_b + h_{oe} v_c \end{aligned}$$

[Fig. 4]

- (i) Which parameter is used to represent the model ?
- (ii) Enlist one application that can be modeled and analyzed using Fig. 4.


Or

(a) As shown in Fig. 5 below;

8

(i) Prove that  $Y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{11}(y_{22} + Y_L)}$

(ii) Find the voltage gain of the circuit ( $V_2/V_1$ ).

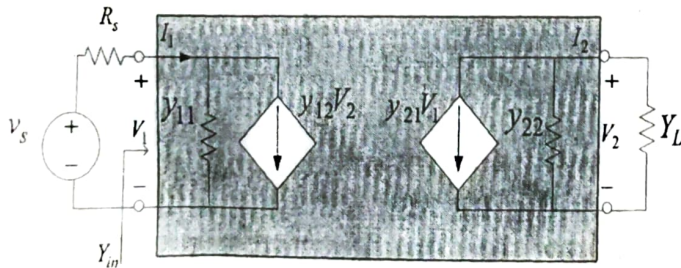

[Fig. 5]

4. (a) Design an electrical equivalent circuit of the transfer function mentioned below, find the value of 'K' of the admittance function.

$$Y(s) = \frac{K(s+1)}{(s+2)(s+4)}$$

Considering that series-arm impedance and shunt-arm impedance of the network are parallel tuning circuits. Where, the values of series-arm elements are  $R_1$  of  $1.5\text{-}\Omega$  resistance connected in parallel to a capacitor  $C_1$   $0.67\text{-F}$  while; the values of shunt-arm elements are  $R_2$  of  $0.167\text{-}\Omega$  resistance connected in parallel to a capacitor  $C_2$  of  $2\text{-F}$ .

4

- (b) Write down the driving-point impedance  $Z(s)$  of the network shown in Fig. 6. Locate the poles and zeros of  $Z(s)$  on the s-plane.

4

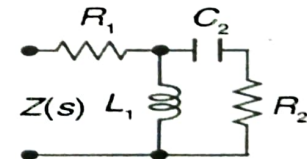


Fig. 6

Or

- (a) The differential equation of a system is given as;

$$4 \frac{d^2 e_0}{dt^2} + 2 \frac{de_0}{dt} + e_0 = 3 \frac{de_i}{dt}$$

Where,  $e_i$  is input signal and  $e_0$  is the output signal of the analogy.

- (i) Find the system function.  
(ii) Plot the pole-zero configurations.

A potential of the form  $5e^{it}$  is applied to the system. Find the output ? 8

5. (a) Identify the type of network, and apply Foster-Form to synthesize a electrical/ electronic network.

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

Can it be realizable ?

4

- (b) Comment over the possibility to realize an  $R$ - $L$  network based on given admittance function using either Foster-Form I/II. 4

$$Y(s) = \frac{s(s+2)}{(s+1)(s+3)}$$

Or

- (a) Comment over the possibility to realize an  $R$ - $L$  network based on given admittance function using either Foster-Form I / Cauer-Form II. 4

$$Y(s) = \frac{(s^4 + 10s^2 + 9)}{(s^3 + 4s)}$$


- (b) Apply the Cauer-Form of the impedance function given below, and comment over the realization of the network. 4

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

6. (a) Draw the oriented incidence matrix  $M$  given below, and the participating Nodes and Branches are as follows : 4

Nodes ↓	Branches →					
	1	2	3	4	5	6
A	-1	0	0	1	-1	0
B	1	-1	0	0	0	-1
C	0	1	-1	0	1	0
D	0	0	1	-1	0	1

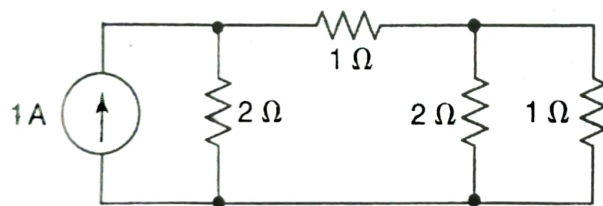
- (b) For the network shown in Fig.7, develop a fundamental cut-set matrix, and thus, find the KCL Equations. 4



[Fig-7]

Or

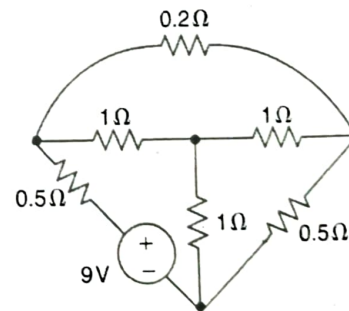- (a) For the network shown in Fig.7, develop a fundamental tie-set matrix, and oriented graph of it. Also, find the possible numbers of tree that can be constructed of the given graph. 4
- (b) For the network as sketched in Fig.8, draw the graph and write a Tie-set schedule. Using the Tie-set schedule obtain the loop equations and find the currents in all branches. 4



[Fig-8]