

**VEER SURENDRA SAI UNIVERSITY OF TECHNOLOGY (VSSUT), ODISHA**  
**Odd Mid Semester Examination for Academic Session 2024-25**

COURSE NAME: B.Tech.

SEMESTER: 3<sup>rd</sup>

BRANCH NAME: Electrical and Electronics Engineering

SUBJECT NAME: Network Theory

FULL MARKS: 30

TIME: 90 Minutes

Answer All Questions.

The figures in the right hand margin indicate Marks. Symbols carry usual meaning.

Q1. Answer all Questions. [2x3]

a) When a complex matrix (electrical/electronic circuit) is analyzed for the multiple given/ known input(s) to find desired output/ responses, is also called "network analysis". Typically, this exercise is done by graph theory as the mathematical modeling-based analysis consumes longer time to reach the solutions. React over the statement?

- CO1

b) A Bridge-T network can be easily analyzed in terms of interconnected network using . State the reason of selecting a two port parameters.

- CO2

c) Mark any two necessary conditions to validate a system function.

- CO3

Q2. [8]

How inductance of a conductor relates to internal flux if a conductor is made of ferromagnetic material?


- CO1

OR

As shown in Fig. 1, the switch is opened at time  $t = 0$ . Find the instantaneous voltage  $v_2(t)$  for  $t \geq 0$ .

- CO1

**Fig. 1**

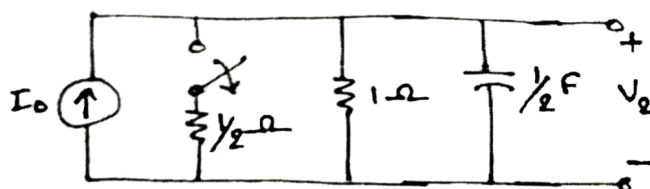


Q3. [8]

Find the Z-parameters of the circuit shown in below, Fig. 2.

- CO1

**Fig. 2**

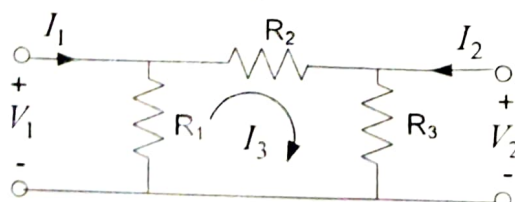

OR

	Find the h-parameter of the circuit in Fig. 3, assuming $L_1 = L_2 = M = 1\text{-H}$ .	- CO2
	<p style="text-align: center;"><b>Fig. 3</b></p>	
Q4.		[8]
	<p>Design an electrical equivalent circuit of the transfer function mentioned below, find the value of 'K' of the admittance function.</p> $Y(s) = \frac{K(s + 1)}{(s + 2)(s + 4)}$ <p>Considering that series-arm impedance and shunt-arm impedance of the network are parallel tuning circuits. Where, the values of series –arm elements are <math>R_1</math> of <math>1.5\text{-}\Omega</math> resistance connected in parallel to a capacitor <math>C_1</math> <math>0.67\text{-F}</math> while; the values of shunt–arm elements are <math>R_2</math> of <math>0.167\text{-}\Omega</math> resistance connected in parallel to a capacitor <math>C_2</math> of <math>2\text{-F}</math>.</p>	- CO3
	OR	
	<p>An inductor <math>L</math> in series with a resistor <math>R</math> of <math>9\text{-}\Omega</math> resistance is connected in parallel to a capacitor <math>C</math>. The driving point impedance, <math>Z(s)</math> of the parallel combination has a zero at <math>s = -3</math> and two poles at <math>s = -1.5 \pm \frac{j1}{2}\sqrt{111}</math>. Calculate the value of <math>L</math> and <math>C</math>? Also, plot the pole-zero locations on the s-plane.</p>	- CO3