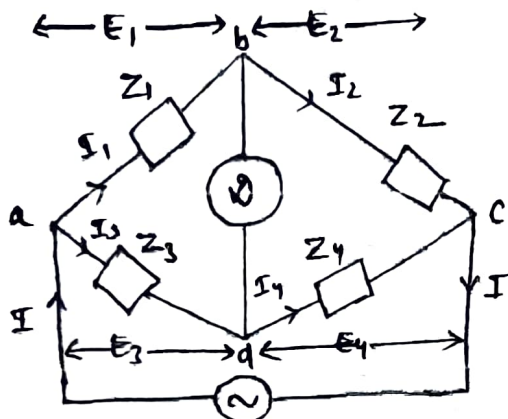


MODULE



Alternating Current Bridges (A.C. Bridges) :-



ab, bc, cd, da $\rightarrow$ 4 arms.

$Z_1, Z_2, Z_3, Z_4 \rightarrow$ 4 impedances

D $\rightarrow$ detector

When the bridge is balanced;

$$E_1 = E_3$$

$$I_1 Z_1 = I_3 Z_3 \quad \text{--- (1)}$$

$$I_1 = I_2 \quad I_3 = I_4$$

$$I_1 = \frac{E}{Z_1 + Z_2} \quad I_3 = \frac{E}{Z_3 + Z_4} \quad \text{--- (2)}$$

putting the value of (2) in (1);

$$\frac{E}{Z_1 + Z_2} Z_1 = \frac{E}{Z_3 + Z_4} Z_3$$

$$\Rightarrow Z_1(Z_3 + Z_4) = Z_3(Z_1 + Z_2)$$

$$\Rightarrow Z_1 Z_3 + Z_1 Z_4 = Z_1 Z_3 + Z_2 Z_3$$

$$\Rightarrow Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow \boxed{\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}} \rightarrow \text{General balance equation}$$

$$Y = \text{admittance} = \frac{1}{\text{impedance } (Z)}$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow \frac{1}{Y_1} \frac{1}{Y_4} = \frac{1}{Y_2} \frac{1}{Y_3}$$

$$\Rightarrow \boxed{Y_1 Y_4 = Y_2 Y_3} \text{ admittance form}$$

Impedance in polar form

$$Z_1 = Z_1 \angle \theta_1 \quad Z_3 = Z_3 \angle \theta_3$$

$$Z_2 = Z_2 \angle \theta_2 \quad Z_4 = Z_4 \angle \theta_4$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow Z_1 Z_4 \angle \theta_1 + \theta_4 = Z_2 Z_3 \angle \theta_2 + \theta_3$$

$$\boxed{Z_1 Z_4 = Z_2 Z_3}$$

$\rightarrow$ product of magnitude of opposite impedances must be equal to other product of opposite impedances.

$$\angle \theta_1 + \theta_4 = \angle \theta_2 + \theta_3$$

$\rightarrow$ sum of phase angle of opposite impedances must be equal to sum of other opposite impedances.

For inductive impedances :-

$$Z_L = R + jX_L \quad |Z_L| + \angle \theta$$


For capacitive impedances.

$$Z_C = R - jX_C \quad |Z_C| - \angle \theta$$

$$X_L = 2\pi fL \quad X_C = \frac{1}{2\pi fC}$$

Maxwell Inductance Bridge :-

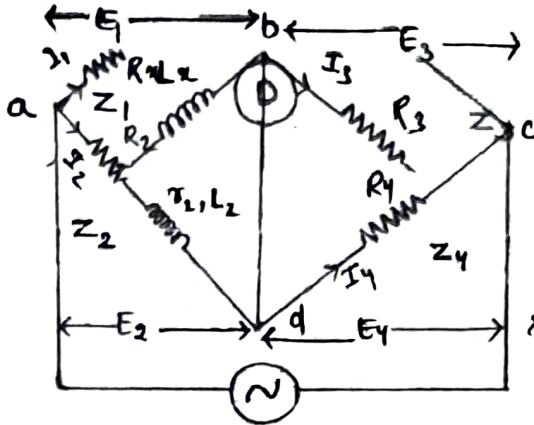- measures an unknown inductance by comparing it with a known inductance.
- four arms present → 4 impedances $\begin{cases} 3 \text{ known} \\ 1 \text{ unknown} \end{cases}$



$$E_1 = I_1 R_1 + I_1 \omega L_1$$

$$E_2 = I_2 R_2 + I_2 r_2 + I_2 \omega L_2$$

At balanced condition;
current in $\odot$ branch = 0

$$E_1 = E_2$$

$$E_3 = E_4$$

$$I_1 = I_3$$

$$I_2 = I_4$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow (R_1 + j\omega L_1) R_4 = (R_2 + r_2 + j\omega L_2) R_3$$


$$\Rightarrow R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + R_3 r_2 + j\omega L_2 R_3$$

⇒ So, by comparing;


$$L_1 = L_2 \frac{R_3}{R_4}$$

$$R_1 = \frac{(R_2 + r_2) R_3}{R_4}$$

phasor diagram :-

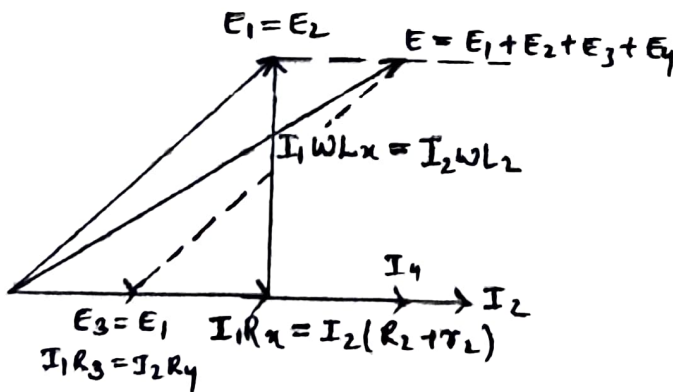

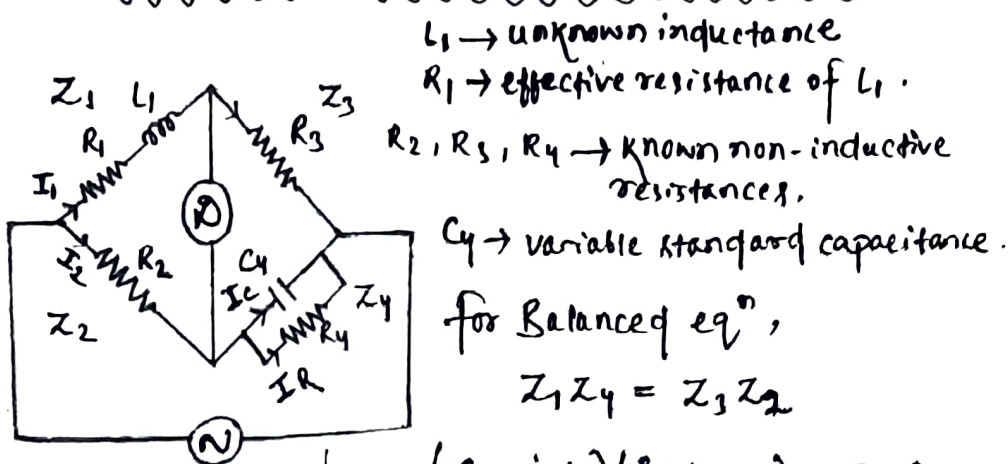Maxwell inductance - capacitance Bridge :-



$L_1 \rightarrow$ unknown inductance

$R_1 \rightarrow$ effective resistance of L_1 .

$R_2, R_3, R_4 \rightarrow$ known non-inductive resistances.

$C_4 \rightarrow$ variable standard capacitance.

for Balanced eqⁿ,

$$Z_1 Z_4 = Z_3 Z_2$$

$$(R_1 + j\omega L_1) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right) = R_2 R_3$$

$$\Rightarrow R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega C_4 R_2 R_3 R_4$$

$$R_1 R_4 = R_2 R_3 \quad | \quad \omega L_1 R_4 = \omega C_4 R_2 R_3 R_4$$

$$\Rightarrow \boxed{R_1 = \frac{R_2 R_3}{R_4}} \quad | \quad \Rightarrow \boxed{L_1 = R_2 R_3 C_4}$$

$$Z_1 = R_1 + j\omega L_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 \parallel C_4$$

$$= R_4 \parallel \frac{1}{j\omega C_4}$$


$$= \frac{R_4}{1 + j\omega C_4 R_4}$$

Quality factor $\rightarrow Q = \frac{\omega L}{R} = \frac{\omega L_1}{R_1} = \frac{\omega R_2 R_3 R_4}{R_3 R_2} = \omega C_4 R_4$

ex.

$Q = 100\% \rightarrow$ indicates 100% inductive in nature.

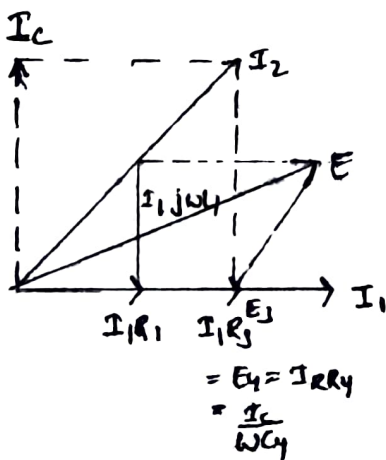$Q = 60\% \rightarrow$ indicates 60% inductive & 40% resistive.



$$= E_4 = I_2 R_4$$

$$= \frac{I_2}{\omega C_4}$$

Adv :- $\rightarrow$ frequency independent

$\rightarrow$ Simple expression


$\rightarrow$ wide range of power and audio freq

Disadv :- $\rightarrow$ limited to low Q inductances.

$(1 < Q < 10) \rightarrow$ required a variable standard capacitance, which can be very expensive.

Hay's Bridge :-

→ modification of maxwell's bridge.

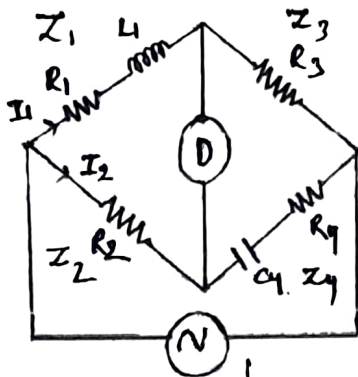

$L_1 \rightarrow$ unknown inductances
 $R_1 \rightarrow$ resistance of L_1
 $R_2, R_3, R_4 \rightarrow$ non inductive resistance
 $C_4 \rightarrow$ Standard capacitance.

At balanced condition;

$$Z_1 = R_1 + j\omega L_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = C_4 + R_4 = \frac{1}{j\omega C_4} + R_4$$

$$= \frac{1 + j\omega C_4 R_4}{j\omega C_4}$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow (R_1 + j\omega L_1) \left(R_4 + \frac{1}{j\omega C_4} \right) = R_2 R_3$$

$$\Rightarrow (R_1 + j\omega L_1) \left(\frac{1 + j\omega C_4 R_4}{j\omega C_4} \right) = R_2 R_3$$

$$\Rightarrow (R_1 + j\omega L_1) (1 + j\omega C_4 R_4) = j\omega C_4 R_2 R_3$$

$$\Rightarrow R_1 + j\omega R_1 R_4 C_4 + j\omega L_1 + (-\omega^2 L_1 R_4 C_4) = R_2 R_3 j\omega C_4$$

$$\Rightarrow (R_1 - \omega^2 L_1 R_4 C_4) + j\omega (L_1 + R_1 R_4 C_4) = j\omega R_2 R_3 C_4$$

by comparing :-

$$R_1 - \omega^2 L_1 R_4 C_4 = 0$$

$$R_1 = \omega^2 L_1 R_4 C_4$$

$$\Rightarrow R_1 = \omega^2 R_4 C_4 \left(\frac{R_2 R_3 R_4}{1 + \omega^2 R_4^2 C_4^2} \right)$$

$$R_1 = \frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \omega^2 R_4^2 C_4^2}$$

$$L_1 + R_1 R_4 C_4 = R_2 R_3 C_4$$

$$L_1 = R_2 R_3 C_4 - R_1 R_4 C_4$$

$$L_1 = R_2 R_3 C_4 - (\omega^2 L_1 R_4 C_4) R_4 C_4$$

$$L_1 = R_2 R_3 C_4 - \omega^2 L_1 R_4^2 C_4^2$$

$$R_2 R_3 R_4 = L_1 + \omega^2 L_1 R_4^2 C_4^2$$

$$R_2 R_3 R_4 = L_1 (1 + \omega^2 R_4^2 C_4^2)$$

$$L_1 = \frac{R_2 R_3 R_4}{1 + \omega^2 R_4^2 C_4^2}$$

Quality factor $Q = \frac{\omega L_1}{R_1}$

$$= \frac{\omega \left(\frac{R_2 R_3 R_4}{1 + \omega^2 R_4^2 C_4^2} \right)}{\frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \omega^2 R_4^2 C_4^2}} = \frac{1}{\omega C_4 R_4}$$

$$Q = \frac{1}{\omega C_4 R_4}$$

$$R_1 = \frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \omega^2 R_4^2 C_4^2} \quad \left| \quad L_1 = \frac{R_2 R_3 R_4}{1 + \omega^2 R_4^2 C_4^2} \right.$$


$$= \frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \left(\frac{1}{Q} \right)^2} \quad \left| \quad = \frac{R_2 R_3 R_4}{1 + \left(\frac{1}{Q} \right)^2} \right.$$

for higher $Q \gg 10$

$$R_1 = \omega^2 R_2 R_3 R_4 C_4^2$$

$$L_1 = R_2 R_3 C_4$$

OWEN's Bridge :-

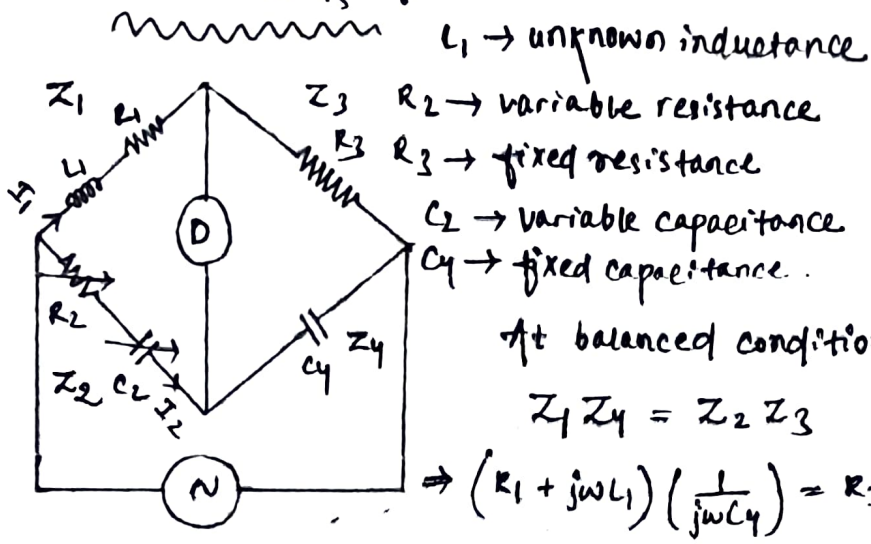

At balanced condition ;

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow (R_1 + j\omega L_1) \left(\frac{1}{j\omega C_4} \right) = R_3 \left(R_2 + \frac{1}{j\omega C_2} \right)$$

$$\Rightarrow \left(\frac{R_1 + j\omega L_1}{j\omega C_4} \right) = R_3 \left(\frac{R_2 j\omega C_2 + 1}{j\omega C_2} \right)$$

$$\Rightarrow (R_1 + j\omega L_1) C_2 = (R_3 + R_2 R_3 j\omega C_2) C_4$$

$$\Rightarrow R_1 C_2 + j\omega L_1 C_2 = R_3 C_4 + j\omega R_2 R_3 C_2 C_4$$

So by comparing ;

$$R_1 = R_3 \cdot \frac{C_4}{C_2}$$


$$L_1 = R_2 R_3 C_4$$

$$Q = \frac{\omega L_1}{R_1} = \frac{\omega R_2 R_3 C_4}{R_3 \frac{C_4}{C_2}}$$


(quality factor)

$$Q = \omega R_2 C_2$$

phasor diagram :-

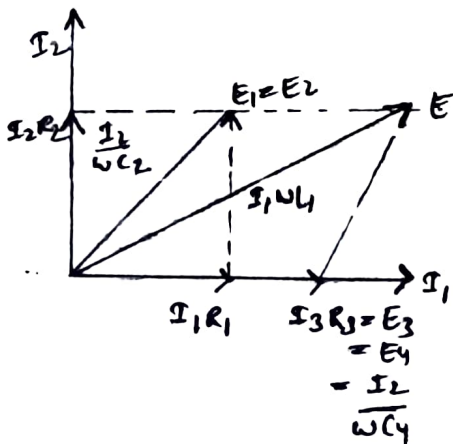

Schering's Bridge :-

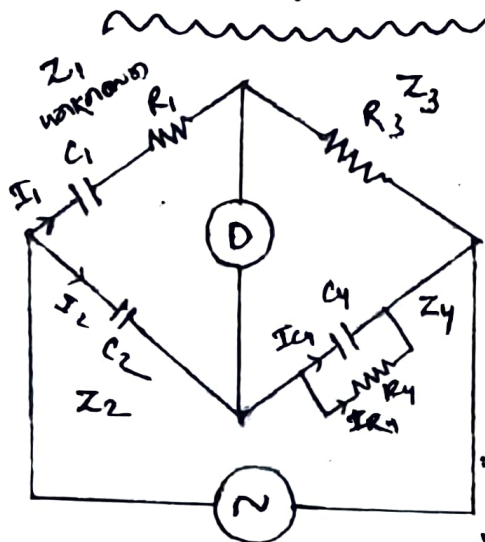

At balanced condition ;

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow \left(\frac{1}{j\omega C_1} + R_1 \right) (R_4 \parallel C_4) = (C_2) R_3$$

$$\Rightarrow \left(\frac{1 + j\omega C_1 R_1}{j\omega C_1} \right) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right) = \frac{R_3}{j\omega C_2}$$

$$\Rightarrow (1 + j\omega C_1 R_1) R_4 C_2 = C_2 R_3 (1 + j\omega C_4 R_4)$$

$$\Rightarrow R_4 C_2 + j\omega C_1 C_2 R_1 R_4 = C_2 R_3 + j\omega C_1 C_2 R_3 R_4$$

So, by comparing ;


$$C_1 = C_2 \frac{R_4}{R_3}$$

$$R_1 = R_3 \frac{C_4}{C_2}$$

Dissipation factor = $\frac{R}{X_C} = \omega C_1 R_1 = \omega R_3 \frac{R_4}{R_3} \cdot \frac{C_4}{C_2}$

$$\Rightarrow \boxed{D.F = \omega R_4 C_4}$$


phasor diagram :-

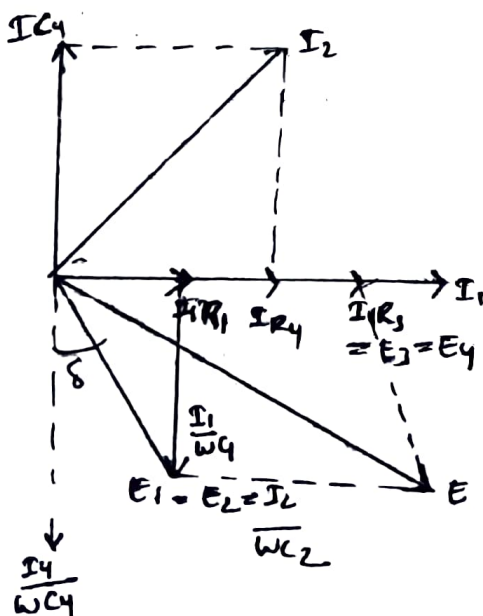

Measurement of high resistance by loss of charge method.

(high $R \rightarrow$ greater than $100\text{K}\Omega / 0.1\text{M}\Omega$)

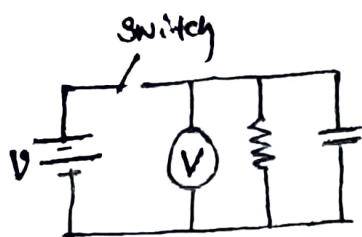→ unknown resistance is connected in parallel with a capacitor & a electrostatic voltmeter.




→ the capacitor is initially charged to some suitable voltage by means of a battery of voltage supply 'V' & then allowed to discharge through unknown resistance.

→ The terminal voltage is observed during discharge

$$V = V_0 \exp(-t/CR)$$

$\nwarrow$ emf of battery $\downarrow$ voltmeter reading

$$\frac{V}{V_0} = \exp(-t/CR)$$

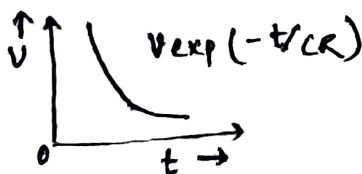

→ Insulation resistance :-

$$R = \frac{-t}{C \log_e \frac{V}{V_0}}$$

$$R = 0.4343 t / C \log \frac{V}{V_0}$$


→ If the resistance R is very large $\Rightarrow$ the process becomes time consuming $\Rightarrow$ errors.

→ Therefore difference b/w the voltages $V - v$ is calculated.

$$R = \frac{0.4343 t}{C \log_{10} \frac{V}{V-v}}$$

v = small difference b/w $V - v$

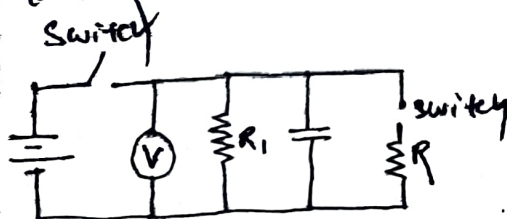* Loss of charge method measures high resistance but it requires a capacitor of a very high leakage resistance as compared to unknown resistance



R_1 is the leakage resistance of the capacitor

R' be the equivalent resistance of R & R_1 .


$$R' = \frac{R \times R_1}{R + R_1}$$

* discharge equation of capacitor :-

$$R' = \frac{0.4343 t}{C \log_{10} \frac{V}{V-v}}$$

$$R_1 = \frac{0.4343 t}{C \log \frac{V}{v}}$$

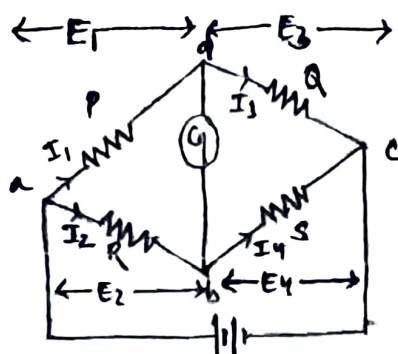Measurement of medium resistance (1-100 Ω) by Wheatstone Bridge method



P, Q $\rightarrow$ known resistances

R $\rightarrow$ unknown

S (bc) $\rightarrow$ Standard resistance

G $\rightarrow$ galvanometer.

Working principle - Null deflection principle

$\rightarrow$ We vary a parameter until the detector (G) shows zero & then we use mathematical relation b/w unknown and known resistances.

$\rightarrow$ Here standard resistance is varied in order to obtain null deflection in G.

$\rightarrow$ Null deflection implies no current is flowing b/w point b & d branch. They are at same potential. ($V_b = V_d$)

$$I_1 = I_3 \text{ \& } I_2 = I_4$$

$$E_1 = E_2 \text{ \& } E_3 = E_4$$

$$E_1 = E_2$$

$$\Rightarrow I_1 P = I_2 R \text{ --- (1)}$$

$$I_1 = I_3 = \frac{E}{P+Q}, \quad I_2 = I_4 = \frac{E}{R+S}$$

Putting the values of I_1 & I_2 in (1);

$$\frac{E}{P+Q} \cdot P = \frac{E}{R+S} \cdot R$$

$$\Rightarrow \frac{P}{P+Q} = \frac{R}{R+S}$$

$$\Rightarrow P(R+S) = R(P+Q)$$

$$\Rightarrow PR + PS = RP + RQ$$

$$\Rightarrow PS = RQ$$

$$\Rightarrow \frac{P}{Q} = \frac{R}{S}$$

$$\Rightarrow \boxed{R = \frac{P}{Q} S} \quad \text{Balance equation of wheatstone bridge.}$$

* Under unbalanced conditions, a small current will flow through the galvanometer.

By thevenin equivalent -

$$I_g = \frac{E_{th}}{R_{th} + R_g}$$

I_g = galvanometer current


R_g = galvanometer resistance.

E_{th} = Thevenin equivalent voltage

R_{th} = Thevenin equivalent resistance.

Measurement of low resistance by Kelvin's Double bridge method.

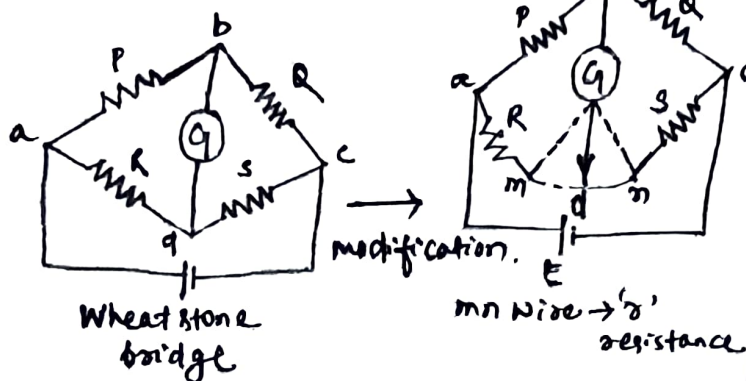low resistance $\rightarrow (0 \text{ to } 1 \Omega)$



$$\frac{P}{Q} = \frac{R}{S}$$

$R \rightarrow$ unknown

at point n: $S+x$
at point m: $R+x$

$$R = \frac{P}{Q} (S+x) \quad R+x = \frac{P}{Q} \cdot S$$

(low resistance)

When galvanometer is connected to point 'd' 'x' is divided into x_1 & x_2

$$\text{such that } \frac{x_1}{x_2} = \frac{P}{Q}$$

$$R+x_1 = \frac{P}{Q} (S+x_2) \quad \text{--- (1)}$$

$$\frac{x_1}{x_2} = \frac{P}{Q} \quad \text{--- (2)}$$

Adding 1 both side ;

$$\frac{x_1}{x_2} + 1 = \frac{P}{Q} + 1$$

$$\Rightarrow \frac{x_1+x_2}{x_2} = \frac{P+Q}{Q}$$

$$\Rightarrow \frac{x_2}{x_1+x_2} = \frac{Q}{P+Q}$$

$$\Rightarrow x_2 = \frac{Q}{P+Q} (x_1+x_2)$$

$$\Rightarrow x_2 = \frac{Q}{P+Q} (x)$$

$$\frac{x_2}{x_1} = \frac{Q}{P}$$

Adding 1 both side ;

$$\frac{x_2}{x_1} + 1 = \frac{Q}{P} + 1$$

$$\Rightarrow \frac{x_2+x_1}{x_1} = \frac{Q+P}{P}$$

$$\Rightarrow x_1 = \frac{P}{P+Q} (x_1+x_2)$$

$$\Rightarrow x_1 = \frac{P}{P+Q} (x)$$

Putting the values of x_1 & x_2 in (1) ;

$$R + \frac{P}{P+Q} x = \frac{P}{Q} \left(S + \frac{Q}{P+Q} x \right)$$

$$\Rightarrow R + \frac{Px}{P+Q} = \frac{PS}{Q} + \frac{PQx}{Q(P+Q)}$$

$$\Rightarrow \boxed{R = \frac{P}{Q} S}$$

from this expression ;
we conclude that , if

we making galvanometer connections in the bridge at a point such that

$\frac{x_1}{x_2} = \frac{P}{Q}$, the resistance of the connecting lead will have no effect in the circuit .


$\rightarrow$ It has a second set of ratio arms, hence the name Kelvin double bridge.

Construction (see next page fig)

$\rightarrow$ First set of ratio arms P & Q.

$\rightarrow$ Second set of ratio arms p and q.

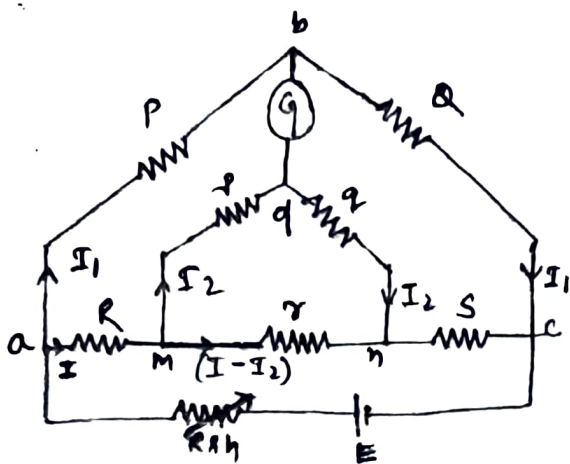$\rightarrow$ Galvanometer is connected in between .



Principle :-

ratio of $\frac{P}{Q}$ is made equal to $\frac{P}{Q}$, under balance conditions there is no current through the galvanometer which means voltage drop between Eab is equal to Eamd & $E_{cb} = E_{cd}$

Voltage across P = Voltage across R + voltage across r

$$V_P = V_R + V_r$$

$$\Rightarrow I_1 P = I R + I_2 r \quad \text{--- (1)}$$

Similarly;

$$V_Q = V_S + V_q$$

$$\Rightarrow I_1 Q = I S + I_2 q \quad \text{--- (2)}$$

'r' & 'q' is in parallel with p+q.
So, $V(r) = V(p+q)$

$$\Rightarrow (I - I_2) r = I_2 (p + q)$$

$$\Rightarrow I r - I_2 r = I_2 p + I_2 q$$

$$\Rightarrow I_2 = \frac{I r}{p + q + r}$$

Substituting the value of I_2 in eq (1) & (2);

$$I_1 P = I R + \left(\frac{I r}{p + q + r} \right) P \quad \text{--- (3)}$$

$$I_1 Q = I S + \left(\frac{I r}{p + q + r} \right) Q \quad \text{--- (4)}$$

Dividing (3) & (4);

$$\frac{P}{Q} = \frac{R + \frac{P r}{p + q + r}}{S + \frac{Q r}{p + q + r}}$$

$$\Rightarrow \frac{P}{Q} \left(S + \frac{Q r}{p + q + r} \right) = R + \frac{P r}{p + q + r}$$

$$\Rightarrow R = \frac{P}{Q} \left(S + \frac{Q r}{p + q + r} \right) - \frac{P r}{p + q + r}$$

$$\Rightarrow R = \frac{P S}{Q} + \frac{Q r}{p + q + r} \left(\frac{1}{Q} - \frac{1}{Q} \right)$$

$$\Rightarrow \boxed{R = \frac{P S}{Q}} \quad \text{as } \frac{r}{Q} = \frac{r}{q}$$

$$\Rightarrow \boxed{\frac{P}{Q} = \frac{R}{S}}$$


This is the required equation.

Wagner Earthing Device

Definition: The Wagner earthing device is used for removing the earth capacitance from the bridges. It is a type of voltage divider circuit used to reduce the error which occurs because of stray capacitance. The Wagner Earth device provides high accuracy to the bridge.

At high frequency, stray capacitance is induced between the bridge elements, ground and between the arms of the bridge. This stray element causes the error in the measurement. One of the ways of controlling these capacitances is to enclose the bridge elements into the shield. Another way of eliminating these stray capacitance is to place the Wagner Earth device between the elements of the bridge.

Construction of Wagner Earthing Device

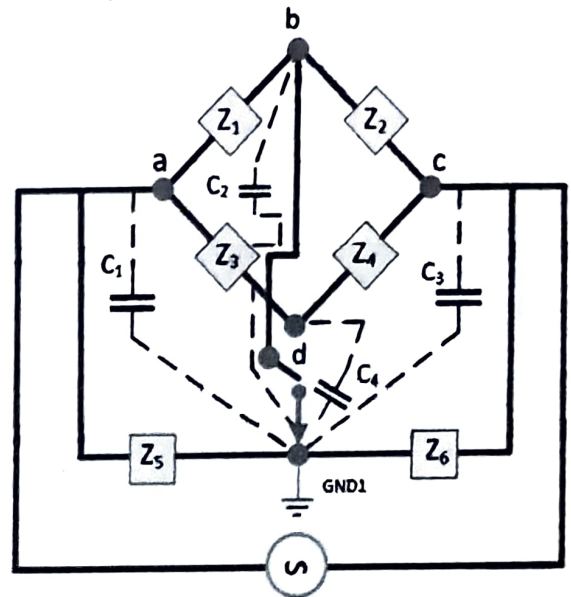

Wagner Earth Device

- The circuit diagram of the Wagner Earth Device is shown in the figure below. Consider the Z_1 , Z_2 , Z_3 , and Z_4 are the impedances arm of the bridge. The Z_5 and the Z_6 are the two variable impedances of the Wagner Earth Device. The centre point of the Wagner earth device is earthed. The impedance of Wagner device arms is similar to the arms of the bridge. The impedance of the arm consists the resistance and capacitances.
- The Wagner impedance placed in such a way so that they make the bridge balance with Z_1 , Z_3 and Z_2 , Z_4 . The C_1 , C_2 , C_3 and C_4 show the stray capacitances of the bridges. The D is the detector of the bridge.
- The bridge comes in the balance condition by adjusting the impedances of arms Z_1 and Z_4 . The stray capacitance prevents bridge to comes in the balanced condition. When the S is not thrown on 'e' then the D is connected between the point p and q . But when S is thrown on 'e' then the detector D is connected between the terminal b and earth.
- The impedance Z_4 and Z_5 are adjusted until the minimum sound is obtained. The headphones again connected between the point b and d for obtaining the minimum sound. The headphones are reconnected between the point b and d , Z_4 and Z_5 are adjusted for obtaining the minimum sound. The process is continuously repeated for obtaining the silent sound.
- The point b , d , and e all are in the same potential. And the capacitance C_1 , C_2 , C_3 , C_4 all are eliminated from the bridge circuit along with the impedances Z_5 and Z_6 .

Adv- eliminates stray capacitance charging effect .

DisAdv- Time consuming.

PYQ'S ASKED IN MID & END SEMESTER EXAMINATIONS

MODULE III

2 MARKERS

- 1) Derive the balance condition of AC bridges.
- 2) What is Wagner's earthing device ?

4 MARKERS

- 1) Draw the phasor diagram and obtain the unknown inductance by maxwell inductance method.
- 2) Explain and derive expression of measuring unknown resistance by using wheatstone bridge.
- 3) Find out the expression of unknown capacitance by schering bridge.
- 4) Explain double bridge method of measuring low resistance .