

Total No. of Questions : 4]

PE-3043

SEAT No. :

[Total No. of Pages : 2

[6502]-2

F. Y. B.Sc. (Computer Science)

ELECTRONICS

ELC-101-T: Principles of Analog Electronics
(Rev. 2024) (Semester - I)

Time : 2 Hours]

[Max. Marks : 30

Instructions to the candidates :

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Draw neat and labelled diagram wherever necessary.
- 4) Use of scientific calculator are allowed.

Q1) Answer the following questions (any 5).

[5 × 1 = 5]

- a) What do you mean by doping?
- b) Draw symbol of PNP and NPN transistor.
- c) What is relation between '3' currents of transistor?
- d) Give the material used for making crystal oscillator.
- e) What is accuracy with respect to DAC?
- f) What is difference between active and passive sensor?
- g) Define range with respect to sensors.

P.T.O.

Q2) Answer the following questions (any 5) :

[5 × 2 = 10]

- Define step angle of stepper motor. Find number of steps for one rotation if step angle is 36° .
- Derive relation of α in terms of β .
- Explain working principle of zener diode in brief.
- Explain the action of pn-junction diode when forward bias is applied to it.
- Define oscillator. State Barkhausen criteria for sustained oscillations.
- Find output voltage of R-2R ladder type DAC if binary input is 1010 and $V_{ref} = 12V$.
- Explain working principle of thermistor.

Q3) Answer the following questions (any 2) :

[2 × 5 = 10]

- What is the need of ADC and DAC in instrumentation system. Explain any three parameters of ADC.
- Give atleast 5 points to distinguish between CC, CB and CE configurations.
- Write any 5 ideal characteristics of op-amp.

Q4) Answer the following questions (any 2) :

[2 × 2½ = 5]

- What is dark current with respect to photodiode. Draw symbol of photodiode and give its two applications.
- Draw and explain block diagram of instrumentation system.
- Explain the concept of virtual ground in op-amp.
- Draw circuit diagram of Wein bridge oscillator and find frequency of it. If $R=5k\Omega$ and $C=0.01\mu F$

