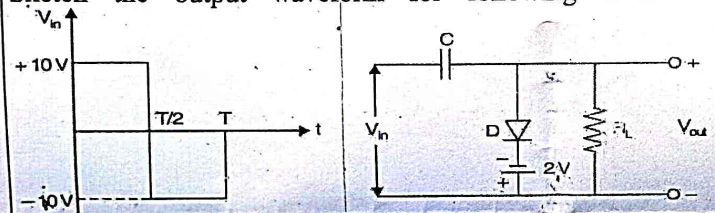
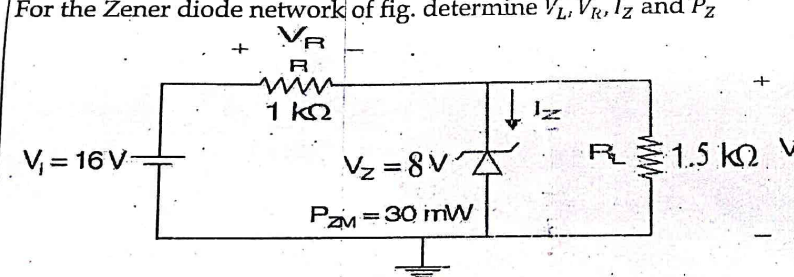
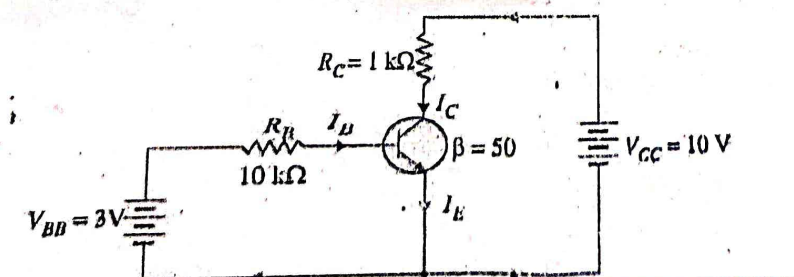


**B. TECH. ECE & ECE-IoT**  
**Year: I, Semester: I**  
**MINOR TEST (EXAMINATION): 2024-2025**  
**ELECTRONIC COMPONENT TESTING AND MEASUREMENT**

Time: 2 Hr.

Max Marks: 20

Note: Answer all questions.

Q1.	Attempt any Two parts of the following.	Marks	CO	BL	PO	PI Code
a)	Explain the construction and working of a p-n junction diode with V-I characteristics.	4	CO1	1,2,3	1	1.3.1
b)	Draw and explain common emitter (CE) transistor configuration and give its input and output characteristics. Also define the current gain ( $\beta$ ) of CE and derive the equation for collector current $I_C$ .	4	CO1	1,2	1	1.3.1
c)	I. Define Stability factors: S, S' and S''. II. The reverse saturation current flowing in a certain PN-junction diode at room temperature is $2 \times 10^{-7}$ A. Calculate the current flowing, when 0.1 V forward bias is applied.	4	CO2	1,2	1	1.3.1
Q2.	Attempt any Two parts of the following					
a)	Explain the working of bridge rectifier with proper diagrams.	3	CO1	1,2,3	1	1.3.1
b)	Sketch the output waveform for following circuit in Figure.	3	CO2	1,2	1	1.3.1
						
c)	For the Zener diode network of fig. determine $V_L$ , $V_R$ , $I_Z$ and $P_Z$	3	CO3	1,2,3,4	1	1.3.1
						
Q3.	Attempt any Two parts of the following					
a)	Explain the construction and working principle of npn transistor. Why is it called Bipolar?	3	CO1	1,2,3,4	1	1.3.1
b)	With a neat circuit diagram and equations, explain the Fixed Bias of BJT with the stability factor (S).	3	CO2	1,2,3,4	1	1.3.1
c)	Determine the dc bias voltage $V_{CE}$ and the current $I_C$ for the following configuration. Assume $V_{CE(sat)} = 0.2V$ .	3	CO3	1,2,3,4	1	1.3.1
						

**B. Tech. ECE & ECE-IoT**  
**Year: I, Semester: I**  
**Major Examination: 2024-2025**

**ELECTRONIC COMPONENT TESTING AND MEASUREMENT**

Time: 3 Hrs.

Max Marks: 50

Note: Attempt ALL questions. ALL questions carry equal marks.

Q1.	Attempt any <b>Five parts</b> of the following.	Marks	CO	BI.	PO	PI Code
a)	What is depletion layer and junction potential in an unbiased p-n junction?	2	CO1	1.2.3	1.2.3	1.3.1
b)	Explain the two reverse breakdown mechanisms in a junction diode.	2	CO2	1.2.3	1.2.3	1.3.1
c)	Explain the clipper circuit with suitable diagram.	2	CO1	1.2.3	1.2.3	1.3.1
d)	Explain the working of LED.	2	CO2	1.2.3	1.2.3	1.3.1
e)	What is base width modulation or early effect in BJT?	2	CO1	1.2.3	1.2.3	1.3.1
f)	What is the difference between $I_{CBO}$ and $I_{CEO}$ in a BJT?	2	CO2	1.2.3	1.2.3	1.3.1
g)	State the significance of operating point in Transistor biasing.	2	CO2	1.2.3	1.2.3	1.3.1
<b>Q2.</b>	Attempt any <b>Two parts</b> of the following					
a)	Differentiate between a JFET and a bipolar transistor. Further, explain the construction and working of a n-channel JFET with illustrative diagrams.	5	CO1	1.2.3	1.2.3	1.3.1
b)	Define different JFET parameters and derive the relationship between them.	5	CO2	1.2.3	1.2.3	1.3.1
c)	i. Differentiate between the characteristics of JFETs and D-MOSFETs.	5	CO2	1.2.3	1.2.3	1.3.1
	ii. A JFET has a drain current of 5 mA. If $I_{DSS} = 10$ mA and $V_{GS(off)} = -6V$ , find the value of $V_{GS}$ .					
<b>Q3.</b>	Attempt any <b>Two parts</b> of the following.					
a)	What is depletion-type MOSFET? Explain the working and operation of n-channel depletion-type MOSFET with diagrams and characteristics curves.	5	CO3	1.2.3	1.2.3	1.3.1
b)	What is the basic difference between D-MOSFET and E-MOSFET. Further explain the working of n-channel enhancement-type MOSFET with diagrams and characteristics curves.	5	CO3	1.2.3	1.2.3	1.3.1
c)	i. For a certain D-MOSFET, $I_{DSS} = 10$ mA and $V_{GS(off)} = -8V$ . a. Is this a n-channel or p-channel b. Calculate $I_D$ at $V_{GS} = -3V$ c. Calculate $I_D$ at $V_{GS} = +3V$	5	CO3	1.2.3	1.2.3	1.3.1
	ii. The datasheet for an E-MOSFET gives $I_{D(on)} = 500$ mA at $V_{GS} = 10V$ and $V_T = 1V$ . Determine the drain current for $V_{GS} = 5V$ .					

Q4.	Attempt any Two parts of the following.									
a)	What is an operational amplifier (Op-Amp)? Draw and explain the block diagram of Op-Amp.	5	CO3	1,2,3	1,2,3	1.3.1				
b)	An ideal op-amp is used in inverting mode with $R_1 = 1k\Omega$ , $R_f = 15k\Omega$ and $V_{CC} = \pm 15V$ . Calculate the output voltage for the following i/p i) $V_{in} = 250mV$ ii) $V_{in} = -300mV$ iii) $V_{in} = -2V$ .	5	CO3, CO4	1,2,3	1,2,3	1.3.1				
c)	Draw and explain the block diagram of cathode ray oscilloscope (CRO).	5	CO6	1,2,3	1,2,3	1.3.1				
Q5.	Attempt any Two parts of the following.									
a)	List and explain different characteristics of an ideal op-amp.	5	CO5	1,2,3	1,2,3	1.3.1				
b)	In the circuit shown in Figure, assume that the op-amp is ideal. If the gain $v_o/v_{in}$ is $-12$ , find the value of $R$ .	5	CO5	1,2,3	2,3,4	1.3.1				
c)	Compare DSO with a Cathode Ray Oscilloscope (CRO). Further draw and label the block diagram of a Digital Storage Oscilloscope (DSO). Explain the function of each block.	5	CO6	1,2,3	2,3,4	1.3.1				

BL – Bloom's Taxonomy Levels (1- Remembering, 2- Understanding, 3 – Applying, 4 – Analysing, 5 – Evaluating, 6 - Creating)

CO – Course Outcomes

PO – Program Outcomes

PI Code – Performance Indicator Code