

Subject Code
BEC-210


B. TECH.
Year: 2nd, Semester: III
MINOR TEST (EXAMINATION): 2025-26
Electronic Devices & Circuits Theory

Time: 2 Hr.

Note: Answer all questions

Max. Marks: 30

Q1.	Attempt any Three parts of the following. Q.1 (a) is compulsory. (Unit-1 & Unit-2)	Marks	CO	BL	PO	PI Code
a)	With the help of a circuit diagram, explain the collector-to-base bias method. How does it improve stability compared to fixed bias method?	4	1	2		
b)	An N-channel JFET has $I_{DSS} = 2 \text{ mA}$ and $V_p = -4 \text{ V}$. Calculate its drain current and transconductance for an applied gate-to-source voltage of -2V .	3	2	3		
c)	With the help of suitable diagram, explain the input and output characteristics of Common Emitter configuration.	3	1	2		
d)	Explain the operation of NMOS with drain and transfer characteristics.	3	2	2		
Q2.	Attempt any Three parts of the following. Q.2 (a) is compulsory. (Unit-1)					
a)	Explain the terms stability factor. Why is it important? Derive its expression for voltage divider bias in npn transistor.	4	1	3		
b)	Discuss the differences between BJT and FET devices. Highlight the importance of FET devices.	3	1	3		
c)	In amplifier shown, transistor has $h_{fe} = 75$, $h_{ie} = 2.5\text{k}\Omega$, $h_{re} = 0$ and $h_{oc} = 20 \mu\Omega$. Calculate current gain, voltage gain input impedance.	3	1	2		

 


	d)	Derive the relations among α , β , and γ . Also, write output current equations in each configuration.	3	1	2		
Q3.	Attempt any Three parts of the following. Q.3 (a) is compulsory. (Unit-2)						
	a)	Draw the drain and transfer characteristics of N-channel JFET. Also, explain the condition of pinch-off.	4	2	2		
	b)	Explain the self bias scheme for FET.	3	2	2		
	c)	In the circuit diagram shown below, a JFET has values of $V_{GS}(\text{off}) = -7\text{ V}$ and $I_{DSS} = 14\text{ mA}$. Determine the values of V_{GS} , I_D and V_{DS} .	3	2	3		
	d)	For the circuit shown below, find V_{DS} and V_{GS} with zero input signal applied.	3	2	3		

BL – Bloom's Taxonomy Levels (1- Remembering, 2- Understanding, 3 – Applying, 4 – Analyzing, 5 –Evaluating, 6 - Creating)
CO – Course Outcomes
PO – Program Outcomes
PI Code – Performance Indicator Code

Time: 3 Hr.

Note: Attempt All questions.

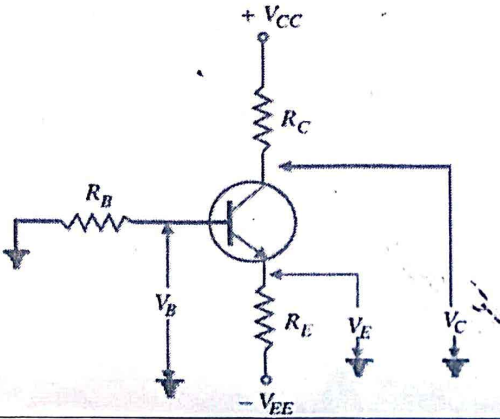Q1	Attempt any five parts of the following. (Unit I and II)	Marks	CO	BL	PO	PI Code
a)	Discuss the hybrid parameter model of <i>npn</i> transistor.	2	1	2	1	1.3.1
b)	Explain Darlington pair with neat and clean diagram.	2	1	2	1	1.3.1
c)	From the given figure, find (i) emitter voltage (ii) base voltage (iii) collector voltage w.r.t. ground.	2	1	3	1	1.3.1
						
d)	Derive the drain current equation for n-channel MOSFET using GCA method.	2	2	2,3	1	1.3.1
e)	Explain the operation of voltage divider based n-channel MOSFET amplifier.	2	2	2,3	1	1.3.1
f)	A JFET has a gate current of 2.5 nA and the reverse gate voltage is 10 V. What is the input resistance of the JFET?	2	2	3	1	1.3.1
g)	Mention the features of BJT, JFET, and MOSFET devices.	2	2	2	1	1.3.1
Q2.	Attempt any two parts of the following. (Unit III only)					
a)	Discuss the negative and positive feedback amplifiers and their advantages and disadvantages in detail.	5	3	2	1	1.3.1
b)	Determine the voltage gain, input impedance, and output impedance with feedback for current series configuration having $A = -100$, $R_i = 10\text{k}\Omega$, $R_o = 20\text{k}\Omega$ for feedback factor of -0.5.	5	3	3	1	1.3.1
c)	Discuss Transconductance feedback amplifier. Also, compare the input and output impedances of different feedback amplifiers.	5	3	2,3	1	1.3.1
Q3.	Attempt any two parts of the following. (Unit III only)					
a)	Explain voltage series feedback amplifier with the impact on feedback gain, input impedance, output impedance.	5	3	2,3	1	1.3.1
b)	Draw the transistor level diagram of voltage shunt amplifier and explain its operation.	5	3	2	1	1.3.1
c)	Draw and explain the operation of FET amplifier stage with voltage series feedback.	5	3	2,3	1	1.3.1
Q4.	Attempt any two parts of the following. (Unit IV only)					
a)	What are the conditions for sustained oscillations? Highlight the features of oscillators.	5	4	2	1	1.3.1
b)	Draw the circuit and explain the operation of Hartley Oscillator. Also, determine the expression for frequency of oscillation.	5	4	2,3	1	1.3.1
c)	What do you mean by tuned oscillator? Explain in detail.	5	4	2	1	1.3.1
Q5.	Attempt any two parts of the following. (Unit IV only)					
a)	Discuss the operation of Wein Bridge oscillator neat and clean diagram. Also, determine its frequency of oscillation.	5	4	2,3	1	1.3.1

b)	Describe the working of crystal oscillator with diagram. Also explain the operating modes of the crystal oscillator.	5	4	2,3	1	13.1
c)	Explain the operation of RC phase shift oscillator. A phase shift oscillator uses 5 pF capacitors. Find the value of R to produce a frequency of 800 kHz.	5	4	3	1	13.1
