

ECE 101

B. Tech. Ist SEMESTER EXAMINATION, 2025-26

Bachelor of Technology

(ECE & IT)

Basic Electronics Engineering

Time : Three Hours]

[Maximum Marks : 75

Note: There are **three** sections (A, B and C) and candidate has to attempt questions from all sections. Marks are indicated against each section.

Section-A

1. Attempt all parts of the following : $5 \times 3 = 15$
- (a) What do you mean by the depletion region in a P-N junction diode ?
 - (b) What is a semiconductor ? Draw its energy band-diagram and give two examples.
 - (c) Find the current gain α in CB configuration of a BJT if $\beta = 101$.
 - (d) Give the definitions for slew rate and CMMR of an operational amplifier.
 - (e) Define modulation index.

Section-B

Note: Attempt all questions :

4×5=20


2. (a) Explain the V-I characteristics of a P-N junction diode under forward and reverse bias condition.

Or

- (b) Describe zener and avalanche breakdown mechanism in a semiconductor diode.
3. (a) What is meant by pinch-off voltage in a JFET? Explain it using a characteristic curve.

Or

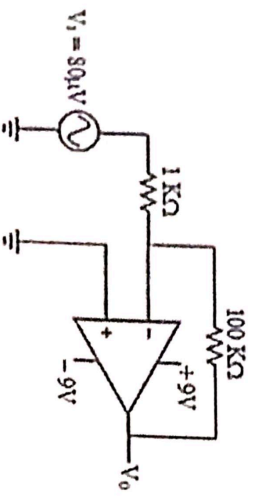- (b) Explain the construction and working of depletion type MOSFET with a diagram.
4. (a) Find the output voltage for the given circuit.



Or

- (b) Draw and discuss the integrator circuit using op-amp.

5. (a) Define the term modulation and demodulation in communication system. Also classify the different modulation scheme.

Or

- (b) An AM transmitter outputs 8KW without modulation and 10KW when modulated. Find the modulation index.

Section-C

Note: Answer any two questions of the following : 2×20=40

6.

- (a) Explain the diode capacitance. Also discuss its types in detail.
- (b) Explain the construction and working principle of light emitting Diode (LED) in detail.

7. (a) Draw a BJT in common-emitter mode and explain its operation along with input and output characteristics.

- (b) Explain the construction of n-channel JFET and draw its transfer and drain characteristics.

8. (a) What is an operational amplifier ? Draw its block diagram. Write the characteristics of an ideal operational amplifier.
- (b) What is an inverting and non-inverting op-amp ? Derive their expression for voltage gain.
9. (a) Illustrate the block diagram of a CRO and explain the function of each block.
- (b) (i) Discuss the element of communication system with the help of block diagram.
- (ii) An Am radio transmitter radiates 20KW power when modulation percentage is 60% calculate the carrier power.

••••