

ASSUMPTION:

- Short Line.
- Voltage drop at the load:

Case 1: without cap bank (SW off)

$$V_{\text{drop}_1} = I_R \cdot R + I_X \cdot (j \cdot X_L)$$

Case 2: with cap bank connected (SW on)

$$V_{\text{drop}_2} = I_R \cdot R + I_X \cdot (j \cdot X_L) - I_C \cdot X_L$$

The difference between Case 1 & Case 2 is the voltage drop

$$\Delta V = V_{r_1} - V_{r_2} = I_C \cdot X_L$$

Example:



- $V_s := 230 \text{ kV}$ System voltage
- $R := 5 \ \Omega$ Feeder resistance
- $X_L := 15 \cdot j \ \Omega$ Feeder Inductive reactance
- $S_C := 100 \text{ kVAr}$ Capacitor bank size
- I_R = Real component of the current
- I_X = Reactive inductive component of current (Laging voltage by 90°)
- I_C = Reactive capacitive component of current (leading the voltage by 90°)

Let $i := 1..5$ $I_{C_i} := \frac{S_C \cdot i}{\sqrt{3} \cdot V_s} \text{ kA}$

Voltage rise: $\Delta V_i := I_{C_i} \cdot |X_L| \text{ kV}$

$$\Delta V_i =$$

3.765
7.531
11.296
15.061
18.827

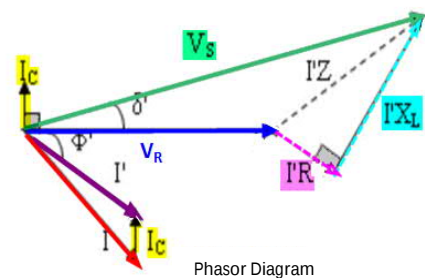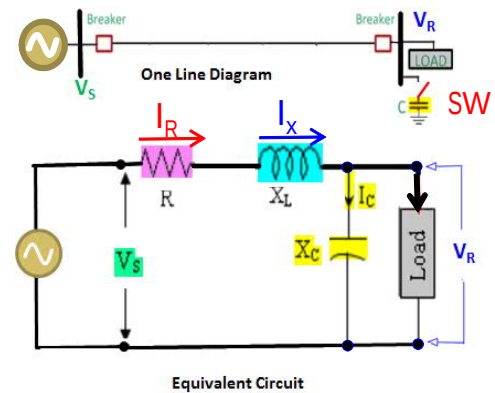

NOTES:

I = current without any capacitor connected.
 I' = current with the shunt capacitor connected.
 $I' = I + I_C$
 without capacitor bank $I_C = 0$ & $I' = I$.

