
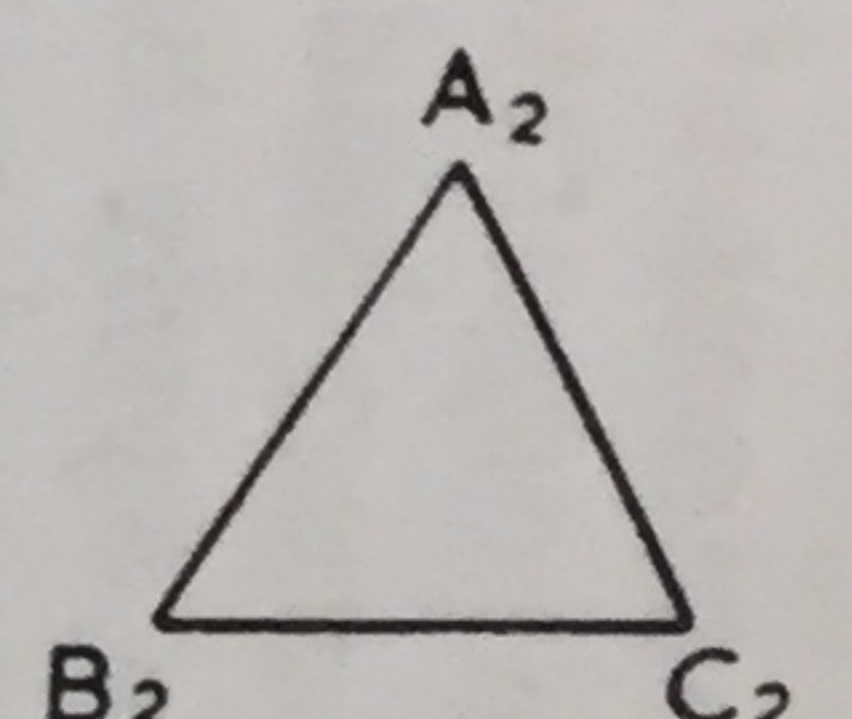
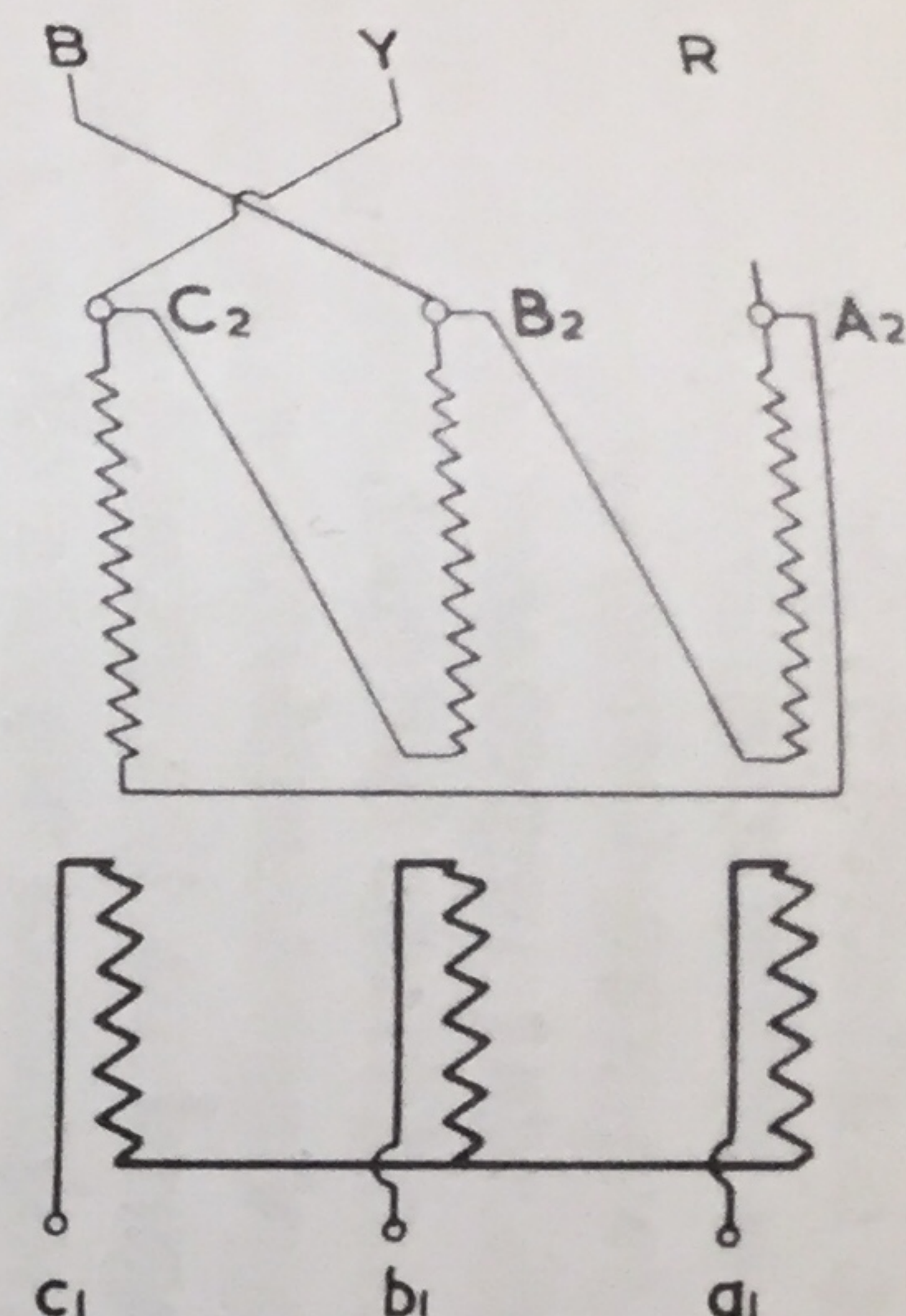
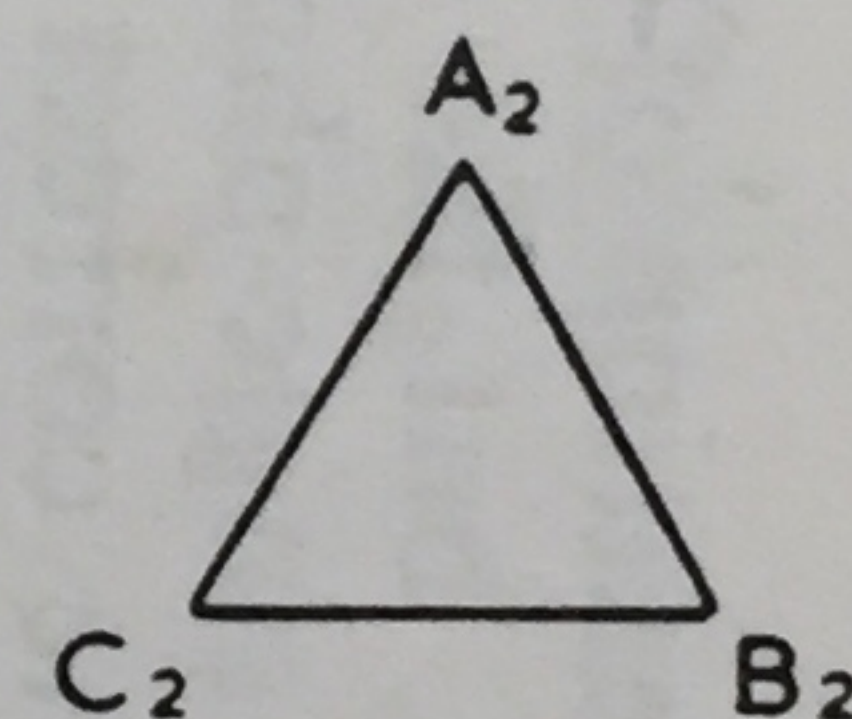
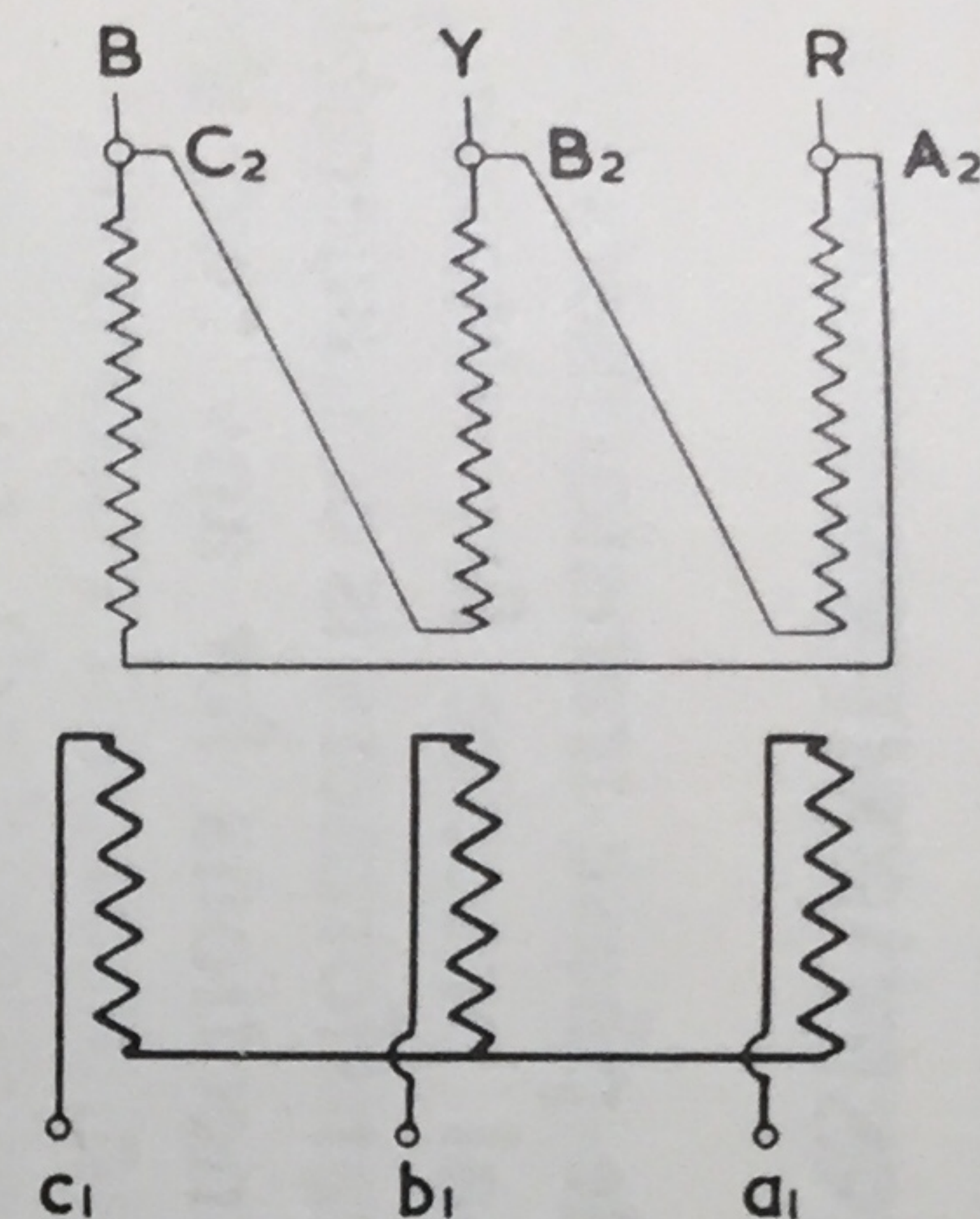
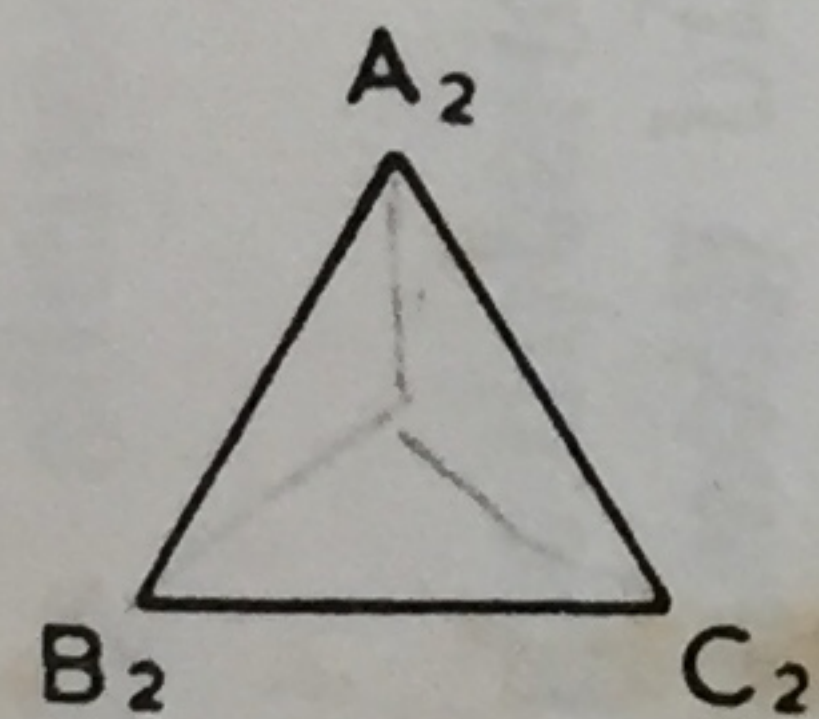
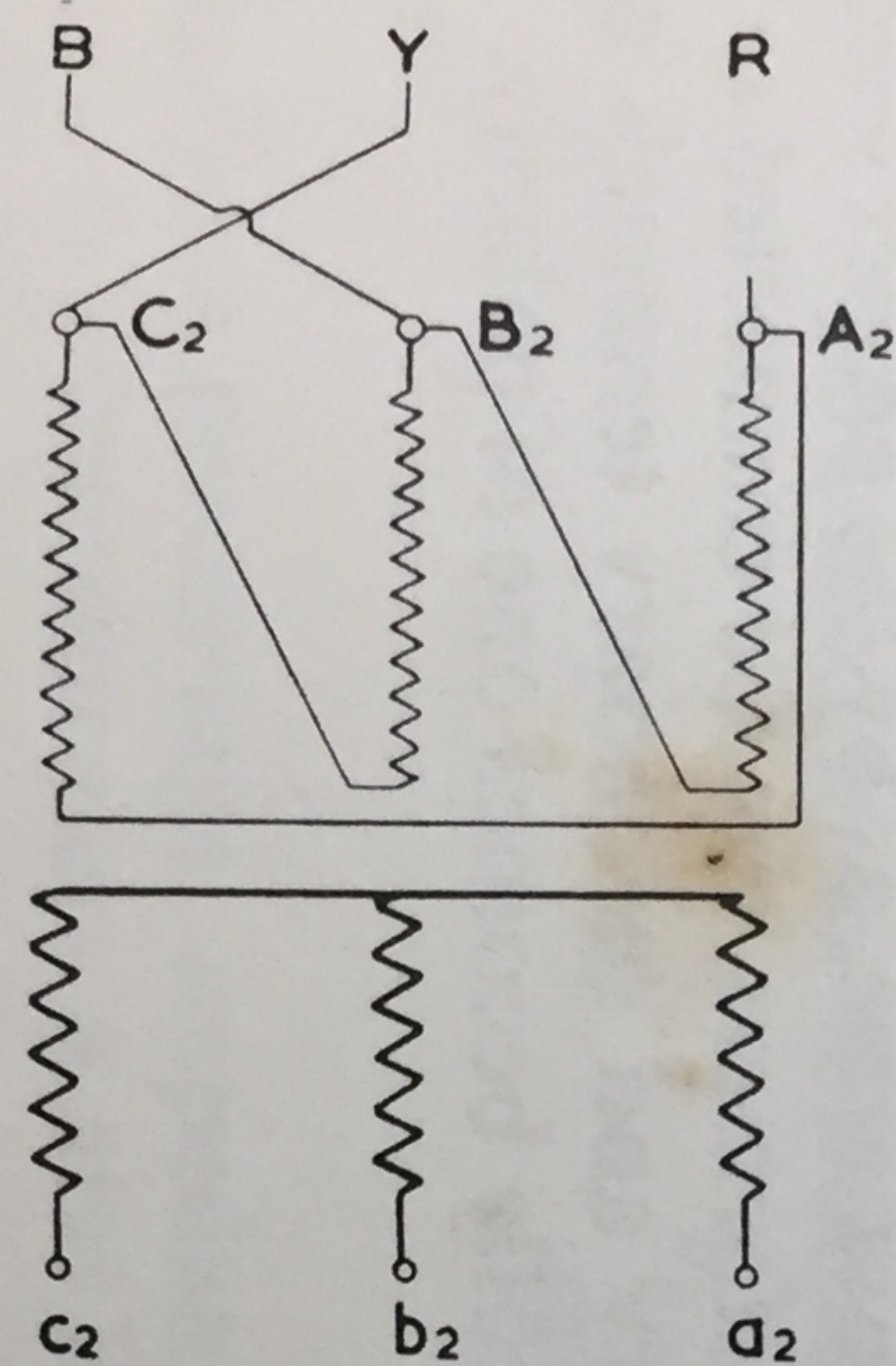
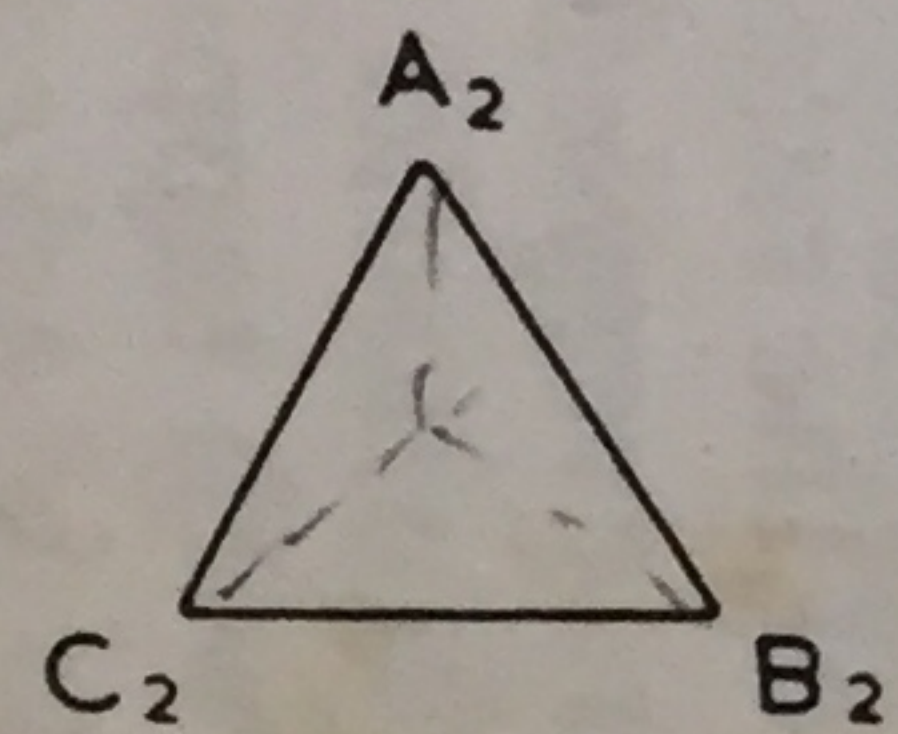


The supply phase sequence is *RYB* in each case and the conventional counter-clockwise phasor rotation is observed

UPPLY

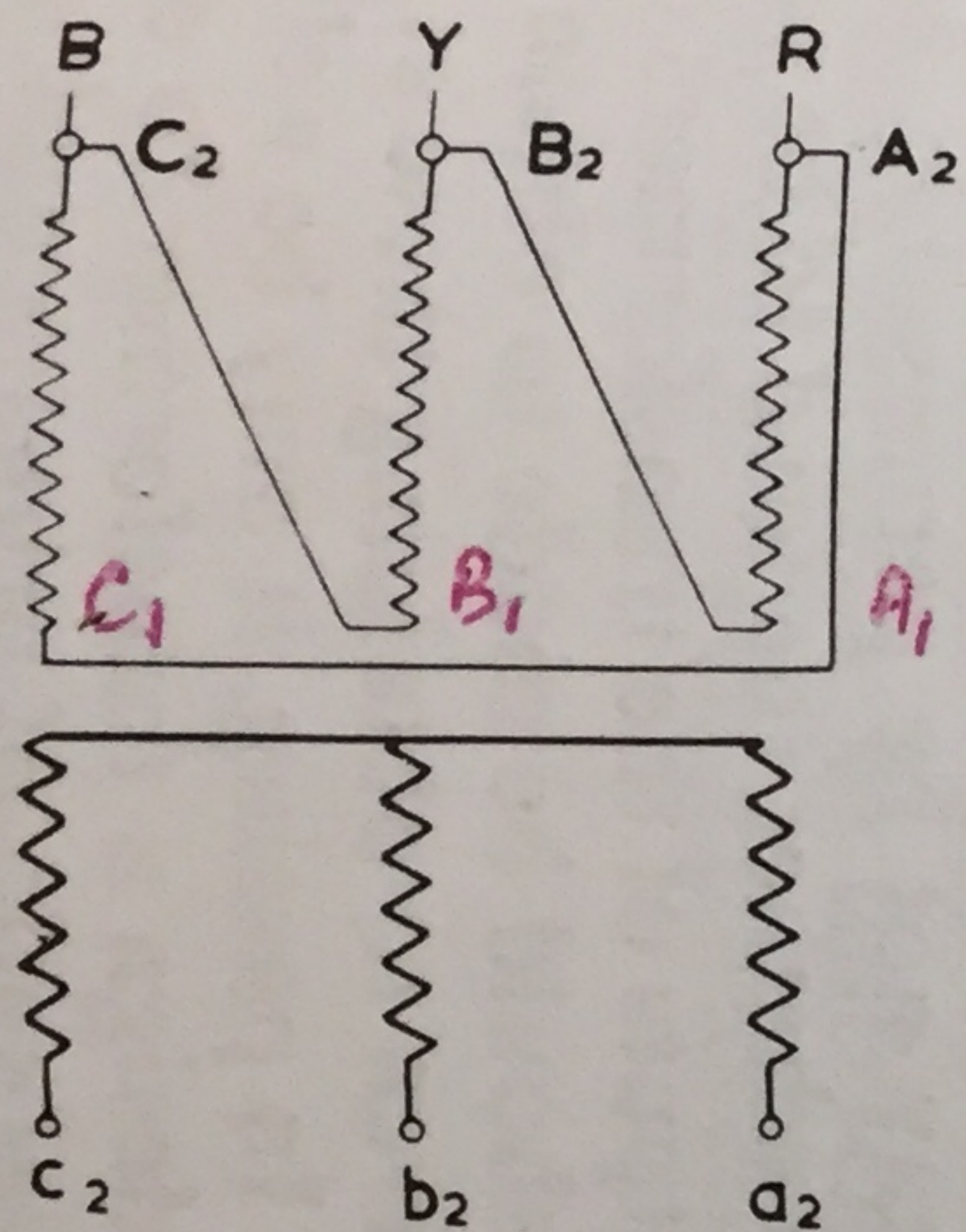

(a) Standard polarity, standard phase sequence

(b) Reverse polarity, reverse phase sequence

(c) Reverse polarity, standard phase sequence

(d) Standard polarity, reverse phase sequence

Fig. 18.12 Diagrams showing four examples of a three-phase delta/star connected transformer having differing polarity and phase sequence conditions