# SPACE WAR GUN KIT

## MODEL K-10



# **Elenco Electronics, Inc.**

#### PARTS LIST

LED

Switch

TOUL

Contact Elenco Electronics (address/phone/e-mail is at the back of this manual) if any parts are missing or damaged. **DO NOT** contact your place of purchase as they will not be able to help you.

			RESIS	TORS				
Qty	Symbol	Description	Col	or Code Part #				
□1	R5	47Ω 5% 1/4W	yello	w-violet-black-gold 124700				
□2	R1, R2	100Ω 5% 1/4W	brov	vn-black-brown-gold 131000				
□1	R6	560Ω 5% 1/4W	gree	en-blue-brown-gold 135600				
□1	R3	1kΩ 5% 1/4W	brov	vn-black-red-gold 141000				
□1	R4	56kΩ 5% 1/4W	gree	en-blue-orange-gold 155600				
□ 1	P1	Trim Pot 50k $\Omega$	5	191552				
		CAPACITORS						
Otv	Symbol	Description	Part #	IDENTIFYING RESISTOR VALUES				
	$C_2 C_3$	01µE Discap (103)	241031	Use the following information as a guide in properly				
□ <u>∠</u>	C1	220uE Electrolytic	282244	identifying the value of resistors.				
	01		202244					
_	S	EMICONDUCTORS	1 III Digit Brid Digit Red Digit					
Qty	Symbol	Description	Part #	Color Degl Color Degl Color Co				
□1	IC1	LM556 Integrated Circuit	330556	Brown 1 Brown 1 Genom 10 Gold 9754 Red 2 Red 7 2 Red 120 Brown 975				
	D1	LED (Light Emitting Diode) Red	350002					
⊔1	D2	LED (Light Emitting Diode) Green	350010					
		MISCELLANEOUS						
Qtv	Symbol	Description	Part #					
□ 1	- <b>,</b>	PC Board	518010	Banda				
□1	S1	Switch Push Button	540001					
□1	S2	Switch Slide	541102	XX Zitarana				
□1		Solder Roll 24"	551124	<u>N/Z</u>				
□1	B1	Battery Snap 9V	590098					
□1	SPK1	Speaker 8Ω	590102					
□1		IC Socket 14-pin	664014					
□2		Wire 4" Blue	814620					
				IDENTIFYING CAPACITOR VALUES				
PAR	TS IDEN	TIFICATION		Capacitors will be identified by their capacitance value in pF (picofarads), nF (nanofarads), or uF (microfarads).				
	Resistor	Transistor Integrated	Circuit	Most capacitors will have their actual value printed on				
				them. Some capacitors may have their value printed in the				
				following manner. Second Digit - Multiplier				
	Battery Snap			First Digit				
	6			1 B=1				
Trin	Pot Spea			1 1				
			The above value is $10 \times 1,000 = 10,000$ pF or $.01\mu$ F					
1 0	5 N I //			The letter K indicates a tolerance of +10%				

The letter J indicates a tolerance of  $\pm 5\%$ 

Multiplier	For the No.	0	1	2	3	4	5	8	9
wultiplier	Multiply By	1	10	100	1k	10k	100k	.01	0.1

Note: The letter "R" may be used at times to signify a decimal point; as in 3R3 = 3.3

I

IC Socket

Electrolytic Discap

**Push Button** 

#### **CIRCUIT OPERATION**

Figure 1 shows the circuit of the Space War Gun. It consists of two 555 integrated circuits (IC) packaged in one IC 556. A 555 timer is well known for its ability to operate as an astable multivibrator oscillator. This oscillator can put out a square wave or pulses depending on the value of the resistors. The first 555A IC oscillates at about 2000 cycles per second. The 555A IC drives the 555B IC to give the weird space sounds.



#### THE 555 IC TIMER

Let's study the right side of Figure 1 which shows the 555B circuit. Resistor R3, R4 and capacitor C3 control the frequency of oscillation of this circuit. Capacitor C3 charges through resistors R3 and R4, but discharges through resistor R4 and the IC. Since the value of R3 and R4 are  $1k\Omega$  and  $56k\Omega$  respectively, their total value equals  $57k\Omega$ . Thus, C3 charges through  $57k\Omega$  and discharges through  $56k\Omega$ . The charge and discharge time is about equal. The output at pin 5 will be a square wave as shown in Figure 2. The frequency of oscillation will be around 2,000 cycles per second. If a speaker is connected to output pin 5, we will hear the 2,000 cycle tone. When the two LEDs are connected to this output, they will light whenever the output goes positive. Resistor R6 is added to limit the current in the LEDs. Resistor R5 is added to limit the current in the speaker.



The operation of the 555A IC differs quite a bit from the 555B IC. Note the value of the capacitor C1, it is  $220\mu$ F or 22,000 times bigger than the .01 $\mu$ F used in the 555B. This means that the frequency of oscillation will be much lower. Also, resistor P1 is made a 50,000 $\Omega$  variable. Resistor R2 is only 100 $\Omega$ . Thus, the charge time on capacitor C1 is through the 100 $\Omega$ . With the pot at the maximum position, the charge to discharge will be

500:1. Figure 3A shows the pulse as it appears in the output in 9. Figure 3B shows the voltage across capacitor C1. By varying the value of P1, the distance between the pulses will be made shorter of the frequency will be increased. At the minimum position, the charge time will be twice the discharge time ( $200\Omega$  versus  $100\Omega$ ). Thus, varying P1 will change the frequency between .1 cycles to 45 cycles. This change in frequency adds to the effects of the Space War Gun.



#### **VOLTAGE CONTROLLED OSCILLATOR (VCO)**

The 555 timer is designed to allow the output frequency to be varied by changing the DC voltage. If we raise the voltage at the 555B input pin 3, the output will decrease in frequency. In the Space Gun design, the VCO of the 555B is connected to the voltage across capacitor C1. This voltage is sawtooth in shape as shown in Figure 3B. As this voltage increases, the pitch-frequency of the 555B timer is constantly changing at a rate determined by the voltage amplitude of the 555A timer.

#### CONSTRUCTION

#### Introduction

The most important factor in assembling your K-10 Space War Gun Kit is good soldering techniques. Using the proper soldering iron is of prime importance. A small pencil type soldering iron of 25 - 40 watts is recommended. The tip of the iron must be kept clean at all times and well tinned.

#### **Safety Procedures**

- Wear eye protection when soldering.
- Locate soldering iron in an area where you do not have to go around it or reach over it.
- **Do not hold solder in your mouth.** Solder contains lead and is a toxic substance. Wash your hands thoroughly after handling solder.
- Be sure that there is adequate ventilation present.

#### **Assemble Components**

In all of the following assembly steps, the components must be installed on the top side of the PC board unless otherwise indicated. The top legend shows where each component goes. The leads pass through the corresponding holes in the board and are soldered on the foil side.

Use only rosin core solder of 63/37 alloy.

#### DO NOT USE ACID CORE SOLDER!

#### What Good Soldering Looks Like

A good solder connection should be bright, shiny, smooth, and uniformly flowed over all surfaces.

- Solder all components from the copper foil side only. Push the soldering iron tip against both the lead and the circuit board foil.
- Apply a small amount of solder to the iron tip. This allows the heat to leave the iron and onto the foil. Immediately apply solder to the opposite side of the connection, away from the iron. Allow the heated component and the circuit foil to melt the solder.
- Allow the solder to flow around the connection. Then, remove the solder and the iron and let the connection cool. The solder should have flowed smoothly and not lump around the wire lead.
- 4. Here is what a good solder connection looks like.









#### **Types of Poor Soldering Connections**

- 1. **Insufficient heat** the solder will not flow onto the lead as shown.
- 2. **Insufficient solder** let the solder flow over the connection until it is covered. Use just enough solder to cover the connection.
- Rosin Soldering iron positioned incorrectly.



- Excessive solder could make connections that you did not intend to between adjacent foil areas or terminals.
- Solder bridges occur when solder runs between circuit paths and creates a short circuit. This is usually caused by using too much solder. To correct this, simply drag your soldering iron across the solder bridge as shown.





#### ASSEMBLE COMPONENTS TO THE PC BOARD



#### **COMPONENT CHECK**

- 1. Be sure that all components have been mounted in their correct places.
- 2. Make sure that C1, the electrolytic capacitor is mounted correctly. The negative lead should be in the hole as shown on the top legend.
- 3. Have LEDs D1 and D2 been installed correctly? The flat side of their bodies should be in the same direction as marked on the top legend. If the LEDs are in backwards, they will not light.
- 4. Pay close attention to the red and black wires of the battery snap. The red wire should be installed in the positive (+) hole and the black wire in the negative (--) hole. Snap in a fresh 9-volt battery.

#### TROUBLESHOOTING

Contact Elenco Electronics if you have any problems. DO NOT contact your place of purchase as they will not be able to help you.

- 1. One of the most frequently occurring problems is poor solder connections. Tug slightly on all parts to make sure that they are indeed soldered.
- 2. All solder connections should be shiny. Resolder any that are not.
- 3. Solder should flow into a smooth puddle rather than a round ball. Resolder any connection that has formed into a ball.
- 4. Have any solder bridges formed? A solder bridge may occur if you accidentally touch an adjacent foil by using too much solder or by dragging the soldering iron across adjacent foils. Break the bridge with your soldering iron.

#### R3 **P1** 1kΩ 4 10 14 $50k\Omega$ 1 SPK1 S1 R4 R1 $56k\Omega$ 100Ω 13 2 IC1 R5 556 47Ω 6 S2 R2 100Ω 5 12 8 R6 560Ω 3 9 D1 7 11 B1 .01µF .01µF D2 220µF C1 C3 C2 -5-

#### SCHEMATIC DIAGRAM

### QUIZ

- 1. The Space War Gun has two \_\_\_\_\_\_ oscillators.
- 2. Capacitor C3 and resistors R3 and R4 controls the \_\_\_\_\_\_ of oscillation.
- 3. The charge time of capacitor C3 is through resistors \_\_\_\_\_ and \_\_\_\_\_.
- The discharge of capacitor C3 is through resistor \_\_\_\_\_ and the \_\_\_\_\_.
- 5. The 555B timer operates at a \_\_\_\_\_\_ frequency than the 555A timer.
- 6. Increasing the value of capacitor C2 will the frequency of oscillation.
- 7. Increasing the voltage of VCO pin 3 of the 555B timer will the frequency of oscillation.
- 8. VCO stands for \_\_\_\_\_\_
- 9. In the Space War Gun design, the 555A timer controls the frequency of the \_\_\_\_\_\_ timer.
- 10. Resistor R6 is added to \_\_\_\_\_\_ the current in the LEDs.

Answers: 1. astable multivibrator; 2. frequency; 3. R3, R4; 4. R4, IC; 5. higher; 6. lower; 7. decreases; 8. voltage controlled oscillator; 9. 555B; 10. limit



## **Stereo Cassette Player Kit**

Easy-to-build kit teaches you basic mechanical and electronic circuits. You will

have fun building this kit and learn how a tape player works. Lesson manual

teaches magnetic recording and audio amplifier theory, speed control, mechanical switching, and much more. Comes complete with all parts including Stereo Head

Phones. Clear plastic case allows you to show your friends your accomplishments.



Requires two (2) "AA" batteries (not included).

with Training Course Model AK-200

**Build This Great Kit and** Learn How Cassette Players Work

- Transparent Case High Resolution
  - Belt Clip

Includes Headphones



Simple and fun to build, compact, portable, and adds safety to your home or office. Learn the basics of motion detector technology while building this motion detector kit that uses a pyroelectric infrared sensor. Comes complete with all parts, PC board, case, schematic, and extensive training manual. Requires one (1) 9V battery (not included).

Uses: • Sentry

#### Burglar Alarm Message Minder Room Detector

#### **Telephone Kit** Model AK-700

#### with Training Course

The AK-700 is a push button electronic telephone. It is equipped with the following features: Pulse/tone dialing, automatic redial, a ringer turn off switch, 4 neon bulbs for visual indication of telephone ringing, clear seethrough case to show the total inner workings of the phone. Sectionalized construction and testing makes construction easy. Wall mounting cradle included.



Strobe Light Kit with Training Course Model AK-520

This deluxe strobe light makes learning fun and easy. You will have fun building this kit and learn how strobe lights work. Comes complete with all components and lesson manual. Kit uses high energy xenon flash tube. Learn about transistors, oscillators, step-up transformers, trigger circuits, flash tubes. and more! Easv-to-follow instructions include lesson manual and self-test. Requires two (2) "C" batteries (not included).



### Super Sensor Motion Detector Kit with Training Course Model AK-510

