

## LevNet RF<sup>™</sup> Controlling Multiple Wired LED Dimmers from One 0-10V Wireless Dimmer

| Product: | LevNet RF Energy Harvesting with Wireless |
|----------|---|
|          | Protocol Solutions (WSS0S, WSD0x)         |

Article ID: 09132012-JE/TB-01

Date: September 13, 2012

**Summary:** This article outlines how and why to use one 0-10V dimmer to control multiple wired LED dimmers.

### Information: Application Explanation:

In many applications, running control wires from a LED dimmer to the control switch is difficult and costly. LevNet RF Energy Harvesting with Wireless Protocol switches and a 0-10V dimmer simplify installation by eliminating the need to run wires and alleviating placement concerns.

#### To program for switching signs from an existing circuit, perform the following:

A Wireless Switch (WSS0S-D0W) is used to raise and lower the output of the 0-10V dimmer. This 0-10V output is then wired to the control input of the Wired LED Dimmer. The Wired LED Dimmer dims the LEDs according to the percent of the 0-10V input signal (5V is 5%).

#### Refer to Figure 1 on page 2 for diagram instructions.

- 1. Link a Wireless Switch (WSS0S-D0W) to a 0-10V Dimmer (WSD01-001) in mode 1.
- 2. Wire the 0-10V Dimmer to the Wired LED Dimmers (WSD02-020) as shown in Figure 1.
- 3. Installation complete. The 0-10V Dimmer can control up to 8 Wired LED Dimmers.

# **Technical Article**





**Contact:** If you have any questions or concerns, please call LES technical support at (800) 959-6004.