

## Table of Contents


1. Introduction
2. Energy Bands of Solids
3. Energy Bands Classification
4. Hole
5. Intrinsic Semiconductor
6. Energy Band Diagram
7. Extrinsic Semiconductor
8. n-type Semiconductor
9. p-type Semiconductor
10. p-n Junction
11. Semiconductor Diode
12. Biasing of p-n Junction
13. I-V Characteristic of Diode
14. Application of Junction Diode as a Rectifier
15. Special Purpose p-n Junction Diodes
16. Photodiode
17. Light Emitting Diode
18. Solar Cell
19. Digital Electronics and Logic Gates
20. AND gate
21. NOT gate
22. NAND gate
23. NOR gate

## Introduction

### Overview

- Electronic circuits use devices controlling electron flow.
- Before transistors, vacuum tubes (diode, triode, tetrode, pentode) were used.
- Vacuum tubes are bulky, consume high power, operate at ~100 V, have limited life and low reliability.
- Modern solid-state semiconductors control charge carrier flow via junctions.
- Light, heat, or small voltage can change mobile charge carriers in semiconductors.
- CRT monitors replaced by LCD due to semiconductor development.
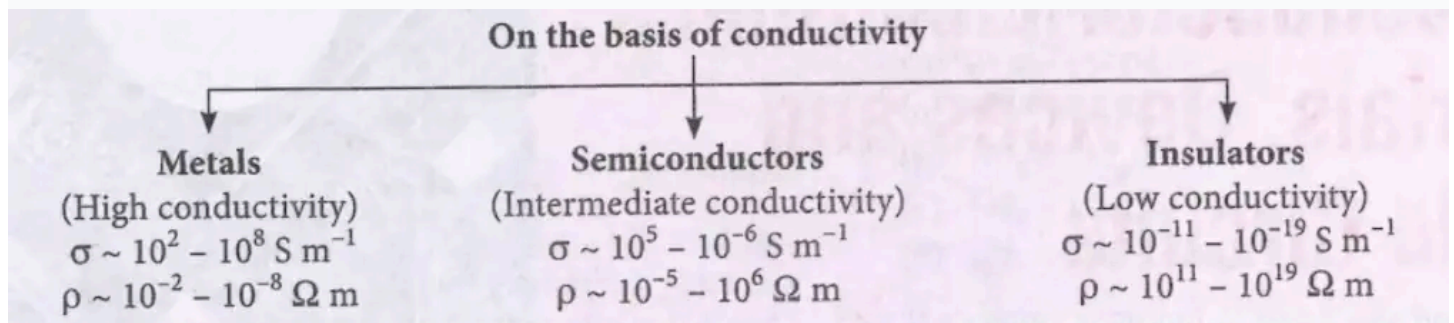
### Classification of Metals, Conductors and Semiconductors



- Materials classified by electrical conductivity: Metals, Semiconductors, Insulators.
- Conductivity ( $\sigma$ ) measures ease of electric current flow.
- Metals: High conductivity, electricity flows easily.
- Semiconductors: Medium conductivity, moderate current flow.
- Insulators: Very low conductivity, almost no current flow.
- Conductivity and resistivity ( $\rho$ ) are inversely related.

### Solved Examples

- **Ex 1:** Identify material type with conductivity  $10^7 \text{ S/m}$ .
  - Answer: Metal (high conductivity).
- **Ex 2:** Material with conductivity  $10^{-6} \text{ S/m}$  is?
  - Answer: Insulator (very low conductivity).

### Practice Set

- Q1: Which material has highest conductivity?
  - A. Semiconductor
  - B. Metal
  - C. Insulator
  - D. None
- Q2: Which material has conductivity around  $10^{-3} \text{ S/m}$ ?
  - A. Metal
  - B. Semiconductor
  - C. Insulator
  - D. Vacuum tube
- Q3: Resistivity  $\rho$  and conductivity  $\sigma$  relation is?
  - A.  $\rho = \sigma$
  - B.  $\rho = 1/\sigma$
  - C.  $\rho = \sigma^2$
  - D.  $\rho = \sqrt{\sigma}$

## Answer Key

- Q1: B - Metals have highest conductivity.
- Q2: B - Semiconductors have medium conductivity ( $\sim 10^{-3}$  S/m).
- Q3: B - Resistivity is inverse of conductivity:  $\rho = 1/\sigma$ .

## Memory Aids

- Metals: High  $\sigma$ , low  $\rho$ .
- Semiconductors: Moderate  $\sigma$ , moderate  $\rho$ .
- Insulators: Low  $\sigma$ , high  $\rho$ .

## Energy Bands of Solids

### Valence Band

- Contains valence electrons.
- Partially or fully filled.
- Electrons here do not conduct current.

### Conduction Band

- Electrons rarely present or partially filled.
- Contains free electrons contributing to current.

### Forbidden Energy Gap

- Energy gap between valence and conduction bands.
- No electrons present in this gap.
- Energy band gap formula:  $E_g = h\nu = \frac{hc}{\lambda}$
- Where  $h$  = Planck's constant,  $c$  = speed of light,  $\lambda$  = wavelength.
- Band gap depends on temperature.

### Fermi Energy

- Maximum energy of free electrons at 0 K.

## Solved Examples

- **Ex 1:** Calculate band gap if  $\lambda = 500$  nm.
  - $E_g = \frac{6.63 \times 10^{-34} \times 3 \times 10^8}{500 \times 10^{-9}} = 3.98 \times 10^{-19} \text{ J} = 2.49 \text{ eV}$

## Practice Set

- Q1: What is conduction band?
  - A. Filled with valence electrons
  - B. Empty or partially filled with free electrons

- C. Energy gap
- D. None
- Q2: Formula for energy band gap?
  - A.  $E_g = h\nu$
  - B.  $E_g = mc^2$
  - C.  $E_g = \frac{1}{2}mv^2$
  - D.  $E_g = \lambda c$
- Q3: Fermi energy is energy at?
  - A. Room temperature
  - B. Absolute zero
  - C. Melting point
  - D. Boiling point

### Answer Key

- Q1: B - Conduction band has free electrons.
- Q2: A - Band gap formula is  $E_g = h\nu$ .
- Q3: B - Fermi energy at 0 K.

### Memory Aids

- Band gap energy:  $E_g = \frac{hc}{\lambda}$ .
- Fermi energy max at 0 K.
- Conduction band = free electrons.

## Energy Bands Classification

### Metals



- Conduction band partially filled or overlaps valence band.
- No forbidden energy gap.


### Insulators

- Valence band fully filled, conduction band empty.
- Wide forbidden gap  $> 5$  eV.
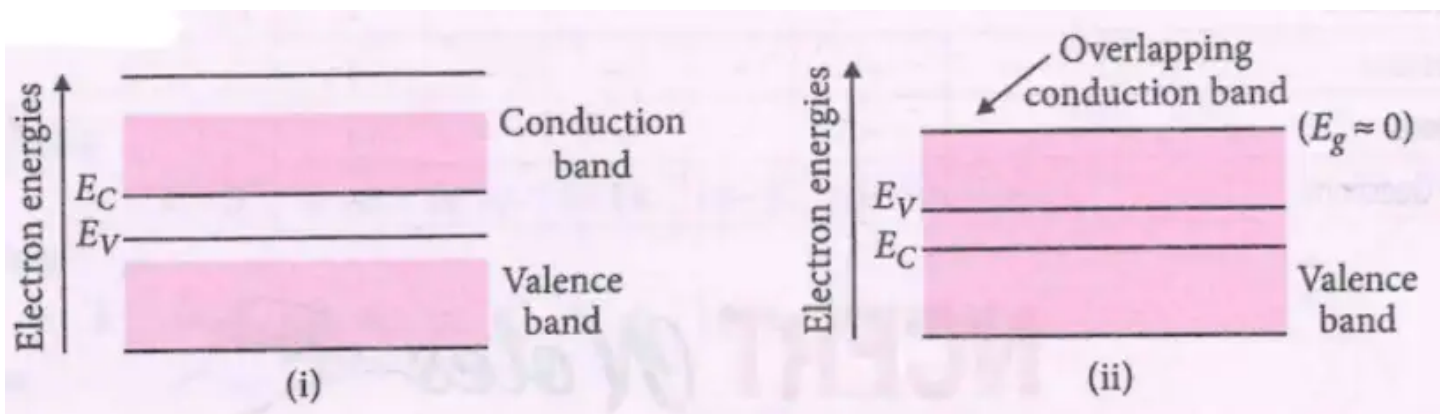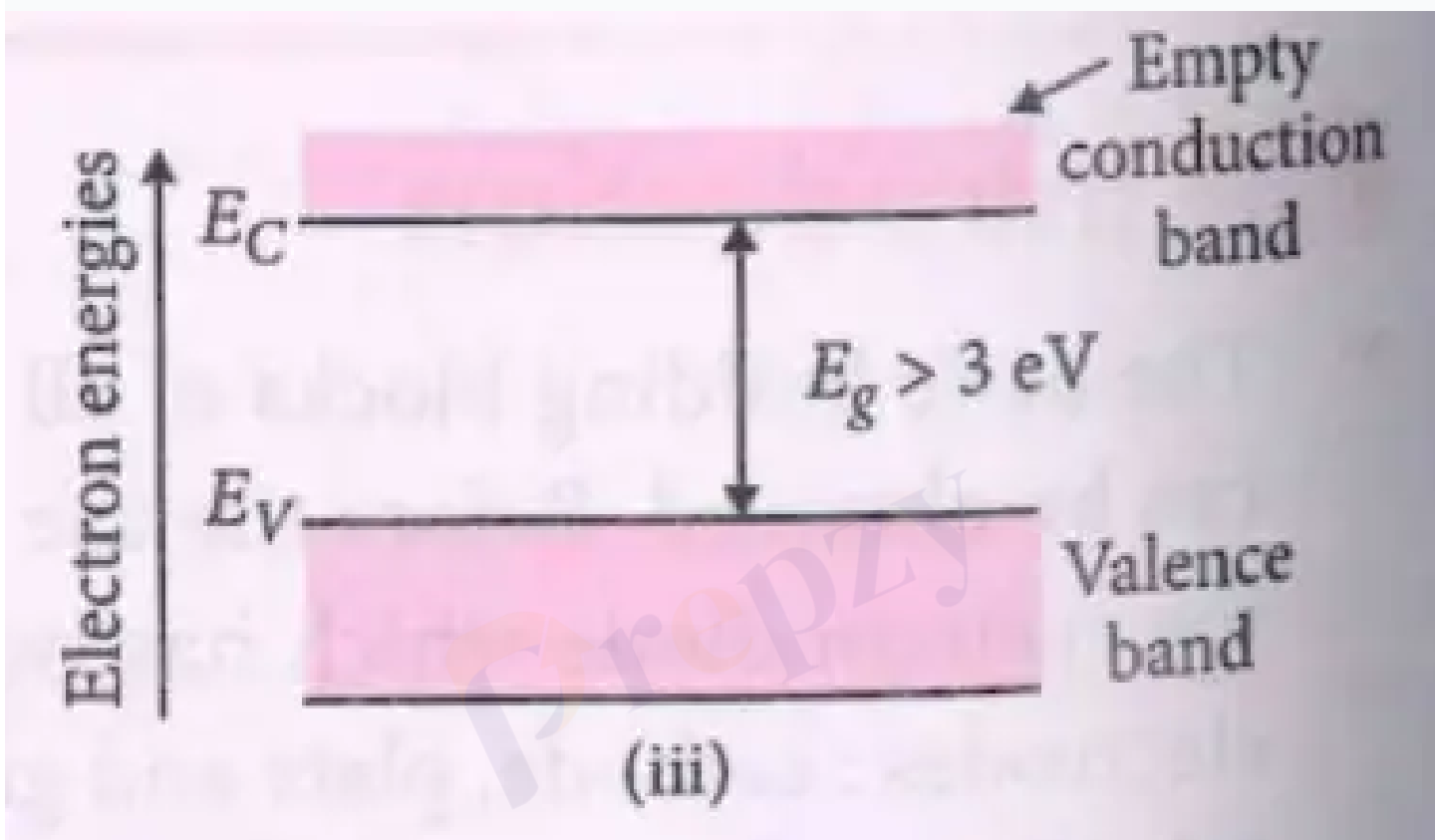
### Semiconductors

- Valence band full, conduction band empty.
- Small forbidden gap  $\sim 1$  eV (Si: 1.1 eV, Ge: 0.72 eV).
- At 0 K, behave as insulators.



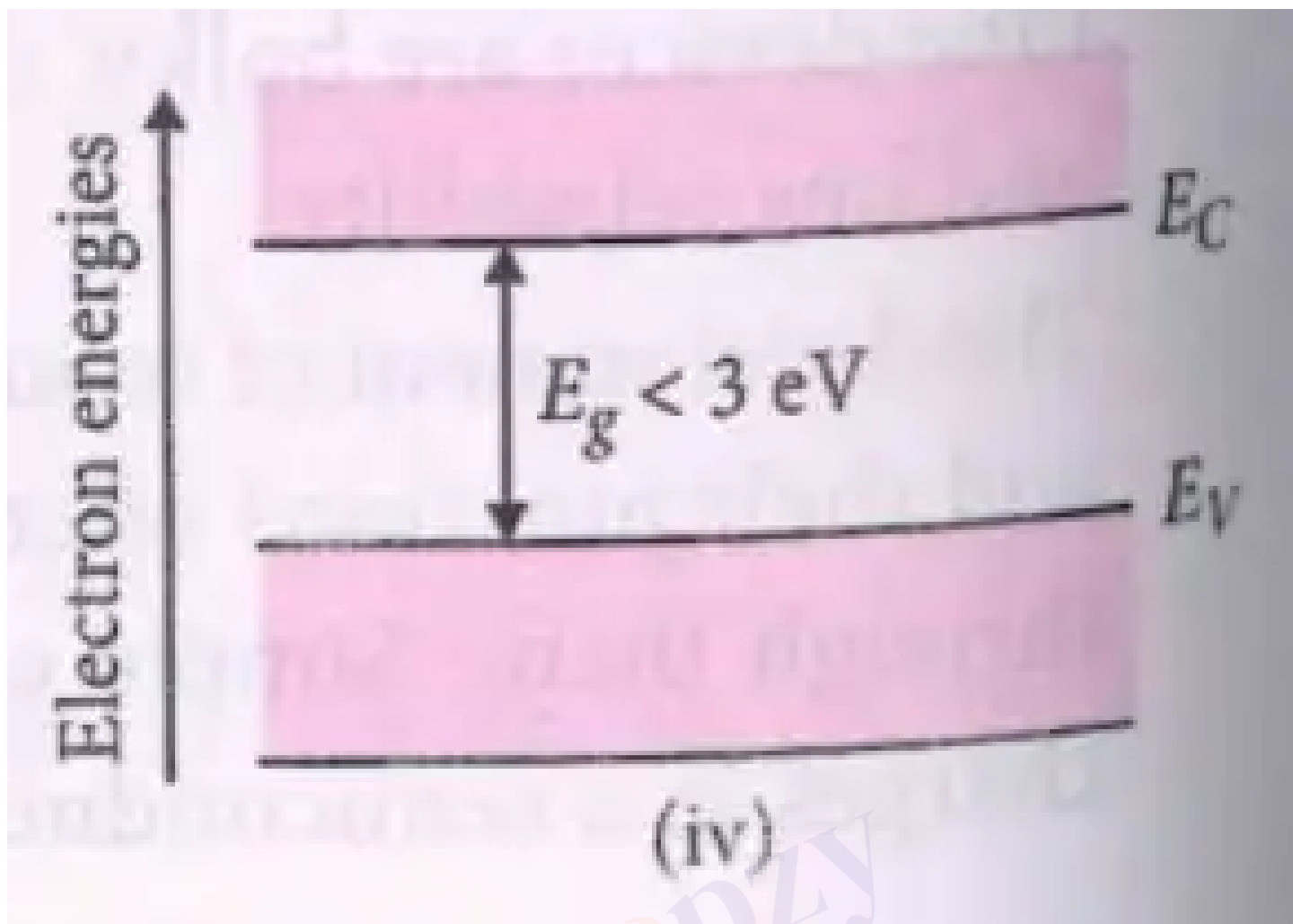

### Solved Examples

- **Ex 1:** Identify material with overlapping bands.
  - Answer: Metal.
- **Ex 2:** Material with band gap 1.1 eV?
  - Answer: Silicon (semiconductor).

### Practice Set

- Q1: Which has no band gap?
  - A. Metal
  - B. Semiconductor
  - C. Insulator
  - D. None
- Q2: Band gap of insulator is?
  - A.  $< 1 \text{ eV}$
  - B.  $\sim 1 \text{ eV}$
  - C.  $> 5 \text{ eV}$
  - D.  $0 \text{ eV}$
- Q3: Band gap of germanium?
  - A.  $0.72 \text{ eV}$
  - B.  $1.1 \text{ eV}$
  - C.  $5 \text{ eV}$
  - D.  $0 \text{ eV}$

## Answer Key

- Q1: A - Metals have overlapping bands, no gap.
- Q2: C - Insulators have band gap  $> 5$  eV.
- Q3: A - Germanium band gap is 0.72 eV.

## Memory Aids

- Metal: Overlapping bands, no gap.
- Insulator: Large gap  $> 5$  eV.
- Semiconductor: Small gap  $\sim 1$  eV.

## Hole

### Definition and Properties

- Positive charge carrier in semiconductors.
- Created when electron leaves covalent bond.
- Charge equal in magnitude to electron but positive.
- Mobility less than electron.

### Solved Examples

- **Ex 1:** What charge does a hole carry?
  - Answer: Positive charge equal to electron charge.

### Practice Set

- Q1: Hole is?
  - A. Negative charge carrier
  - B. Positive charge carrier
  - C. Neutral particle
  - D. Electron
- Q2: Hole mobility compared to electron is?
  - A. Greater
  - B. Equal
  - C. Smaller
  - D. Zero
- Q3: Hole is created when?
  - A. Electron breaks covalent bond
  - B. Electron recombines
  - C. Electron moves in conduction band
  - D. Electron is created

## Answer Key

- Q1: B - Hole carries positive charge.
- Q2: C - Hole mobility is smaller than electron.
- Q3: A - Hole created when electron leaves covalent bond.

## Memory Aids

- Hole = positive charge carrier.
- Mobility: electron > hole.
- Created by electron leaving bond.

## Intrinsic Semiconductor

### Definition and Examples

- Pure semiconductor without impurities is intrinsic semiconductor.
- Examples: Silicon (Si), Germanium (Ge).

### Carrier Concentration

- Electron density in conduction band,  $n_e$ .
- Hole density in valence band,  $n_h$ .
- Intrinsic carrier concentration,  $n_i$ .
- In intrinsic semiconductor,  $n_e = n_h = n_i$ .

### Current in Intrinsic Semiconductor

- Electrons and holes move in opposite directions under electric field.
- Total current,  $I = I_e + I_h$ , where  $I_e$  is electron current,  $I_h$  is hole current.
- Current formula:  $I = n_i e A (v_e + v_h)$ , where  $A$  is cross-sectional area,  $v_e, v_h$  are drift velocities.

### Conductivity and Resistivity


- Conductivity,  $\sigma = n_i e (\mu_e + \mu_h)$ , where  $\mu_e, \mu_h$  are mobilities of electrons and holes.
- Resistivity,  $\rho = \frac{1}{\sigma} = \frac{1}{en_i(\mu_e + \mu_h)}$ .

### Temperature Effect

- Increasing temperature increases electron-hole pair density.
- Conductivity increases with temperature.
- Resistivity decreases with temperature.
- Semiconductors have negative temperature coefficient of resistance.
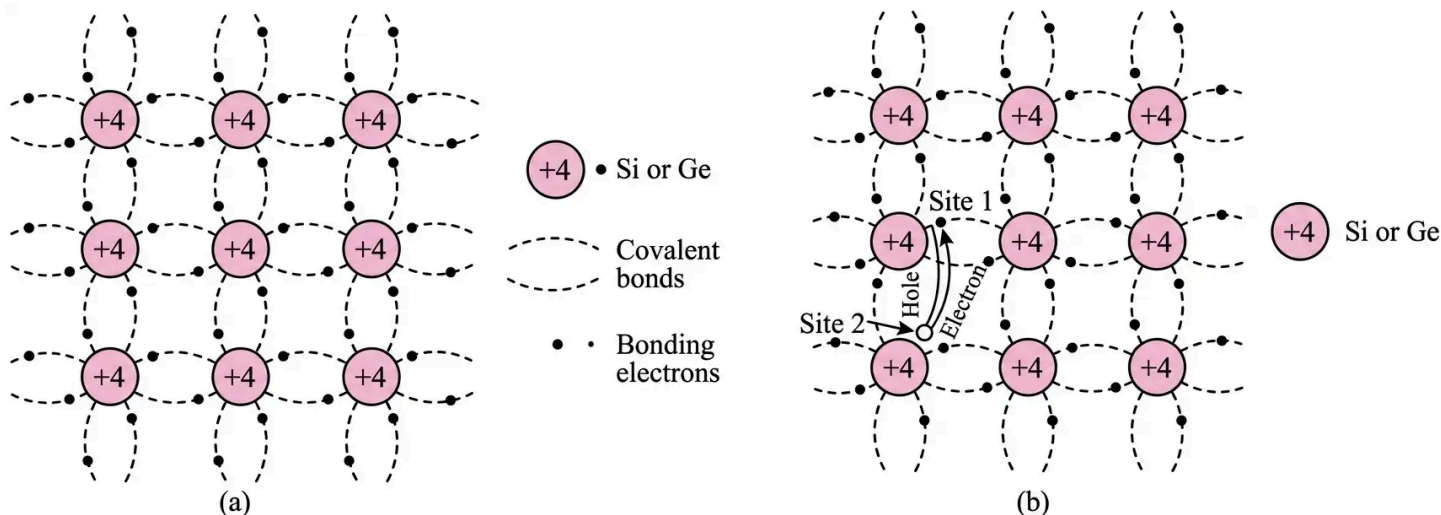
### Crystal Structure and Hole Motion

- Si or Ge atoms form covalent bonds with 4 neighbors (+4 core charge).
- At low temperature, all bonds intact.
- Electron movement creates holes that appear to move through the lattice.



### Solved Examples

- **Ex 1:** Calculate conductivity if  $n_i = 1 \times 10^{16} \text{ m}^{-3}$ ,  $\mu_e = 0.14 \text{ m}^2/\text{V}\cdot\text{s}$ ,  $\mu_h = 0.05 \text{ m}^2/\text{V}\cdot\text{s}$ , and  $e = 1.6 \times 10^{-19} \text{ C}$ .
  - $\sigma = n_i e (\mu_e + \mu_h) = 1 \times 10^{16} \times 1.6 \times 10^{-19} \times (0.14 + 0.05) = 3.04 \times 10^{-3} \text{ S/m}$ .
- **Ex 2:** Find resistivity  $\rho$  from above data.
  - $\rho = 1/\sigma = 1/3.04 \times 10^{-3} = 329.0 \text{ } \Omega\cdot\text{m}$ .

### Practice Set

- Q1: What is the relation between electron and hole densities in intrinsic semiconductor?
  - A)  $n_e > n_h$
  - B)  $n_e < n_h$
  - C)  $n_e = n_h = n_i$
  - D) None of these
- Q2: Conductivity  $\sigma$  of intrinsic semiconductor depends on?
  - A) Carrier concentration and mobility
  - B) Only carrier concentration
  - C) Only mobility
  - D) Temperature only
- Q3: If intrinsic carrier concentration doubles, what happens to conductivity?
  - A) Halves
  - B) Doubles
  - C) Quadruples
  - D) No change

### Answer Key

- Q1: C - Electron and hole densities are equal in intrinsic semiconductor.
- Q2: A - Conductivity depends on carrier concentration and their mobilities.
- Q3: C - Conductivity  $\sigma = n_i e (\mu_e + \mu_h)$ , doubling  $n_i$  doubles  $\sigma$ , so quadruples conductivity.


### Memory Aids

- Intrinsic: Pure, no impurities.
- $n_e = n_h = n_i$  always equal.
- Conductivity  $\sigma = n_i e (\mu_e + \mu_h)$ .
- Resistivity inversely proportional to conductivity.
- Conductivity increases with temperature.

## Energy Band Diagram
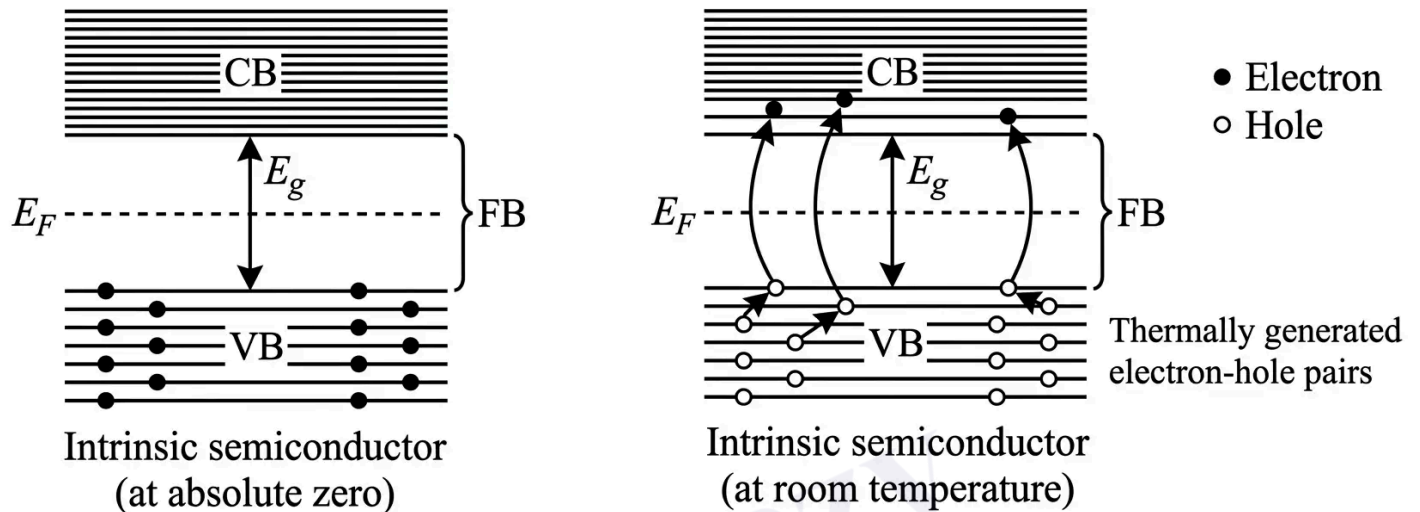
### Band Structure at Different Temperatures

- At  $T = 0$  K, valence band (VB) full, conduction band (CB) empty.
- Intrinsic semiconductor behaves like insulator at 0 K.
- At  $T > 0$  K, electrons gain thermal energy, jump from VB to CB.
- Equal number of holes created in VB.
- Electrons occupy lowest energy levels in CB.
- Number of electrons in CB equals number of holes in VB.



### Solved Examples

- **Ex 1:** At 0 K, what is the conductivity of intrinsic semiconductor?
  - Zero, as no free electrons in conduction band.
- **Ex 2:** Why does conductivity increase with temperature?
  - Thermal energy excites electrons to conduction band, increasing free carriers.

### Practice Set

- Q1: At 0 K, intrinsic semiconductor behaves as?
  - A) Conductor
  - B) Insulator
  - C) Semiconductor
  - D) Superconductor
- Q2: What causes holes in valence band?
  - A) Electron excitation to conduction band
  - B) Electron recombination
  - C) Impurity doping
  - D) None of these
- Q3: Number of electrons in conduction band equals?
  - A) Number of holes in valence band
  - B) Number of atoms
  - C) Number of impurities
  - D) Zero

## Answer Key

- Q1: B - At 0 K, no free electrons, acts as insulator.
- Q2: A - Holes created by electron excitation to conduction band.
- Q3: A - Electrons in CB equal holes in VB.


## Memory Aids

- At 0 K, no conduction.
- Thermal energy creates electron-hole pairs.
- Electron-hole pairs enable conductivity.

## Extrinsic Semiconductor
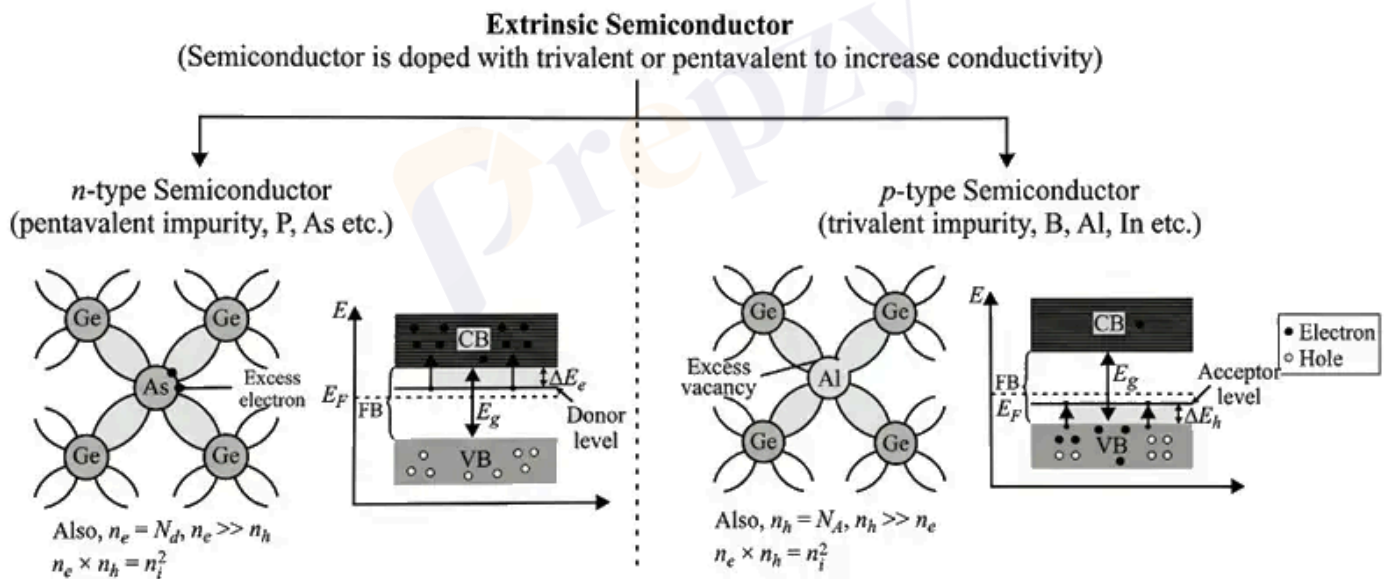
### Concepts

- Impure semiconductor with added impurities is called extrinsic semiconductor.
- Doping: Adding small amounts of impurities with different valency to pure semiconductor.
- Impurities increase mobile electrons or holes, enhancing conductivity.
- Two types: n-type (pentavalent impurities) and p-type (trivalent impurities).
- Energy bands affected by donor (n-type) or acceptor (p-type) levels.



## Solved Examples

- **Ex 1:** Calculate the effect of doping on conductivity if donor atoms increase free electrons by  $10^{15} \text{ cm}^{-3}$ .
- Step 1: Identify donor density  $N_d = 10^{15} \text{ cm}^{-3}$ .
- Step 2: Free electron concentration  $n_e \approx N_d = 10^{15} \text{ cm}^{-3}$ .
- Step 3: Conductivity increases proportionally to  $n_e$ .

## Practice Set

- **Q1:** What is doping in semiconductors?
  - A. Removing impurities
  - B. Adding impurities to increase conductivity

- C. Heating semiconductor
- D. Cooling semiconductor
- **Q2:** Which impurity type is used for n-type semiconductor?
  - A. Trivalent
  - B. Pentavalent
  - C. Tetravalent
  - D. Hexavalent
- **Q3:** In extrinsic semiconductors, what mainly increases conductivity?
  - A. Holes in n-type
  - B. Electrons in p-type
  - C. Electrons in n-type
  - D. Holes in intrinsic

### Answer Key

- **Q1:** B - Doping means adding impurities to increase conductivity.
- **Q2:** B - Pentavalent impurities create n-type semiconductors.
- **Q3:** C - Electrons are majority carriers in n-type, increasing conductivity.


### Memory Aids

- Doping = Adding impurities to increase charge carriers.
- n-type = Negative charge carriers (electrons) from pentavalent donors.
- p-type = Positive charge carriers (holes) from trivalent acceptors.

### n-type Semiconductor
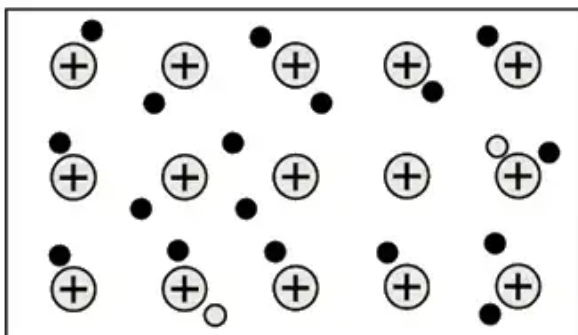
#### Concepts

- Pure Si or Ge (tetravalent) doped with group V pentavalent impurities (As, Sb, P).
- Donor atoms donate one free electron for conduction.
- Conduction due to electrons (negative charge carriers).
- Majority carriers: electrons; minority carriers: holes.
- Charge neutrality maintained.
- Electron concentration:  $n_e \approx N_d \gg n_h$ , where  $N_d$  = donor density.



#### Legends

- Free electron (negative charge)
- Hole (positive charge)
- ⊕ Immobile ion (positive charge)

### Solved Examples

- **Ex 1:** Find majority carrier concentration if donor density  $N_d = 5 \times 10^{16} \text{ cm}^{-3}$ .
- Step 1: Majority carrier concentration  $n_e \approx N_d = 5 \times 10^{16} \text{ cm}^{-3}$ .
- Step 2: Minority carrier concentration  $n_h$  is negligible.

## Practice Set

- **Q1:** What type of impurity is used in n-type semiconductor?
  - A. Trivalent
  - B. Pentavalent
  - C. Tetravalent
  - D. Divalent
- **Q2:** Majority carriers in n-type semiconductor are?
  - A. Holes
  - B. Electrons
  - C. Ions
  - D. Neutrons
- **Q3:** If donor density  $N_d = 10^{15} \text{ cm}^{-3}$ , what is electron concentration?
  - A.  $10^{14} \text{ cm}^{-3}$
  - B.  $10^{15} \text{ cm}^{-3}$
  - C.  $10^{16} \text{ cm}^{-3}$
  - D.  $10^{13} \text{ cm}^{-3}$

## Answer Key

- **Q1:** B - Pentavalent impurities are used in n-type doping.
- **Q2:** B - Electrons are majority carriers in n-type semiconductor.
- **Q3:** B - Electron concentration equals donor density  $N_d$ .


## Memory Aids

- n-type = Negative charge carriers (electrons).
- Donor atoms = Pentavalent impurities.
- Electron concentration  $n_e \approx N_d$ .

## p-type Semiconductor
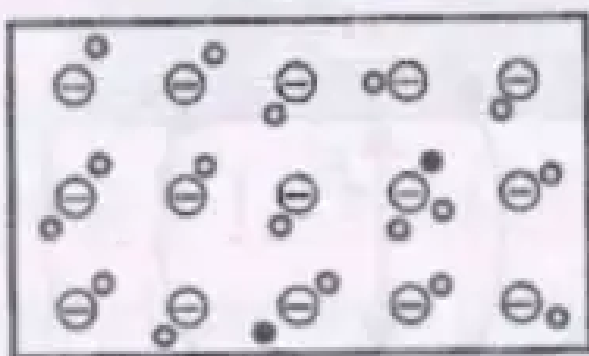
### Concepts

- Pure Si or Ge doped with group III trivalent impurities (Al, B, In).
- Acceptor atoms create holes (positive charge carriers).
- Conduction due to holes.
- Majority carriers: holes; minority carriers: electrons.
- Charge neutrality maintained.
- Hole concentration:  $n_h \approx N_a \gg n_e$ , where  $N_a$  = acceptor density.



- Ligends**
- Hole (positive charge)
  - Electron (negative charge)
  - ⊖ Immobile ion (negative charge)

## Solved Examples

- **Ex 1:** Calculate hole concentration if acceptor density  $N_a = 2 \times 10^{16} \text{ cm}^{-3}$ .
- Step 1: Hole concentration  $n_h \approx N_a = 2 \times 10^{16} \text{ cm}^{-3}$ .
- Step 2: Electron concentration  $n_e$  is negligible.

## Practice Set

- **Q1:** What type of impurity is used in p-type semiconductor?
  - A. Pentavalent
  - B. Trivalent
  - C. Tetravalent
  - D. Hexavalent
- **Q2:** Majority carriers in p-type semiconductor are?
  - A. Electrons
  - B. Holes
  - C. Ions
  - D. Neutrons
- **Q3:** If acceptor density  $N_a = 10^{15} \text{ cm}^{-3}$ , what is hole concentration?
  - A.  $10^{14} \text{ cm}^{-3}$
  - B.  $10^{15} \text{ cm}^{-3}$
  - C.  $10^{16} \text{ cm}^{-3}$
  - D.  $10^{13} \text{ cm}^{-3}$

## Answer Key

- **Q1:** B - Trivalent impurities are used in p-type doping.
- **Q2:** B - Holes are majority carriers in p-type semiconductor.
- **Q3:** B - Hole concentration equals acceptor density  $N_a$ .

## Memory Aids

- p-type = Positive charge carriers (holes).
- Acceptor atoms = Trivalent impurities.
- Hole concentration  $n_h \approx N_a$ .

## p-n Junction

### Formation and Charge Distribution


- Free electrons from n-type diffuse to p-type, filling holes.
- Positive charge layer forms on n-side; negative charge layer on p-side.
- Charge layers form quickly, stopping further carrier movement.
- Potential difference ( $V_o$ ) of 0.1–0.3 V (Ge: 0.3 V, Si: 0.7 V) forms as a barrier.
- Depletion layer: thin region with immobile charges around junction.

### Currents in p-n Junction

- **Diffusion current:** Holes diffuse  $p \rightarrow n$ ; electrons diffuse  $n \rightarrow p$  due to concentration difference.
- **Drift current:** Minority carriers move across barrier due to potential, creating drift current.
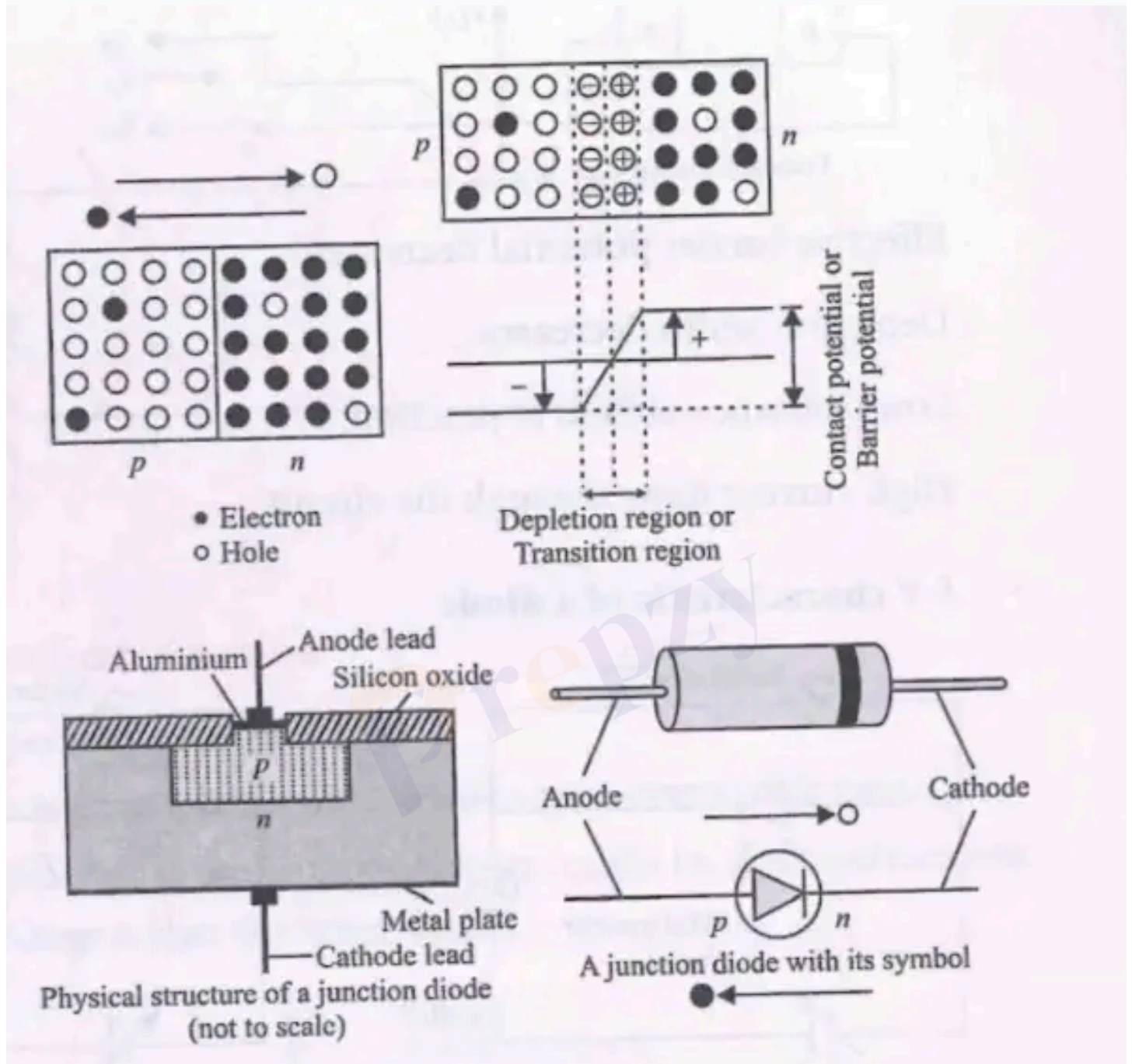
## Electric Field

- Electric field intensity,  $E = \frac{V}{d}$ , where  $V$  is potential barrier and  $d$  is depletion width.



## Solved Examples

- Ex 1:** Calculate electric field if  $V_0 = 0.7 \text{ V}$  and  $d = 2 \times 10^{-6} \text{ m}$ .
  - Use  $E = \frac{V}{d} = \frac{0.7}{2 \times 10^{-6}} = 3.5 \times 10^5 \text{ V/m}$ .

## Practice Set

- Q1: What is the typical potential barrier for silicon p-n junction?
  - A) 0.1 V
  - B) 0.3 V
  - C) 0.7 V

- D) 1.0 V
- Q2: Which current is due to minority carriers moving across the junction?
  - A) Diffusion current
  - B) Drift current
  - C) Both currents
  - D) None
- Q3: If the depletion width is  $1 \times 10^{-6}$  m and barrier potential is 0.3 V, what is the electric field intensity?
  - A)  $3 \times 10^5$  V/m
  - B)  $3 \times 10^4$  V/m
  - C)  $3 \times 10^6$  V/m
  - D)  $3 \times 10^3$  V/m

### Answer Key

- Q1: C - Silicon p-n junction barrier is typically 0.7 V.
- Q2: B - Drift current is due to minority carriers moving across the barrier.
- Q3: A -  $E = V/d = 0.3/1 \times 10^{-6} = 3 \times 10^5$  V/m.


### Memory Aids

- Potential barrier: Ge ~0.3 V, Si ~0.7 V.
- Diffusion current: majority carriers move due to concentration gradient.
- Drift current: minority carriers move due to electric field.
- Electric field:  $E = V/d$ .

## Semiconductor Diode
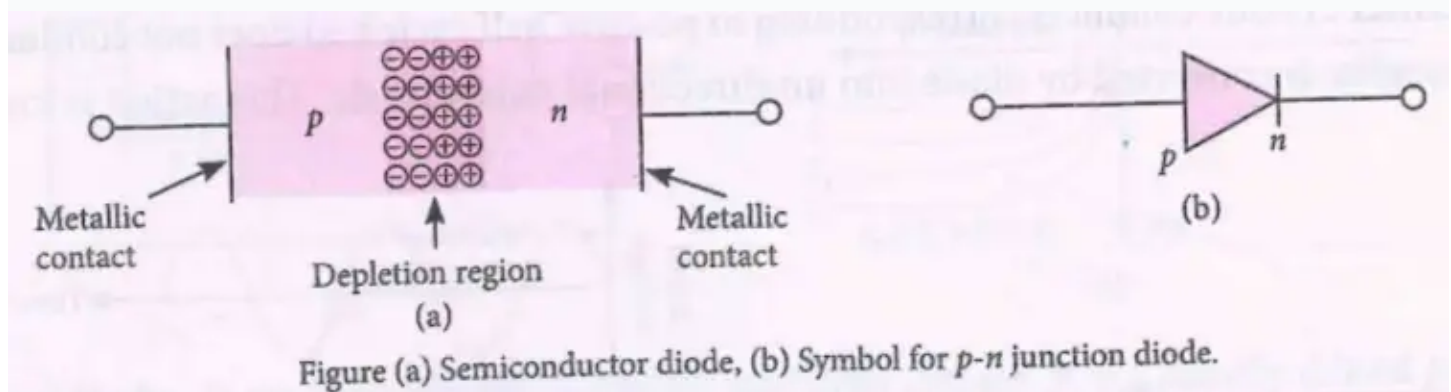
### Basic Concept

- A semiconductor diode is a p-n junction with metallic contacts for external voltage application.
- Current flows mainly from p-side to n-side under forward bias (arrow direction shows conventional current).
- Equilibrium barrier potential changes with applied external voltage  $V$ .



### Structure and Symbol

- Formed by joining p-type and n-type semiconductors.
- Depletion region at junction acts as a barrier to current.
- Metallic contacts connect diode to circuit.
- Symbol shows arrow indicating forward current direction.

## Solved Examples

### Ex 1

- Identify the direction of current flow in a given diode symbol: Current flows from p to n side (arrow direction).
- Apply external voltage to alter barrier potential and observe current change.

### Practice Set

- Q1: What does the arrow in a diode symbol indicate?
  - A) Electron flow direction
  - B) Conventional current direction
  - C) Voltage polarity
  - D) Depletion region width
- Q2: What forms the depletion region in a semiconductor diode?
  - A) Metallic contacts
  - B) Junction of p and n regions
  - C) External voltage
  - D) Battery connection
- Q3: Applying forward bias to a diode does what to the barrier potential?
  - A) Increases it
  - B) Decreases it
  - C) No change
  - D) Removes it completely

### Answer Key


- Q1: B - Arrow shows conventional current flow direction under forward bias.
- Q2: B - Depletion region forms at the p-n junction.
- Q3: B - Forward bias reduces the barrier potential allowing current flow.

### Memory Aids

- Arrow in diode symbol = conventional current direction.
- Depletion region = barrier to current at p-n junction.
- Forward bias lowers barrier potential, enabling conduction.


## Biasing of p-n Junction

### Unbiased Junction

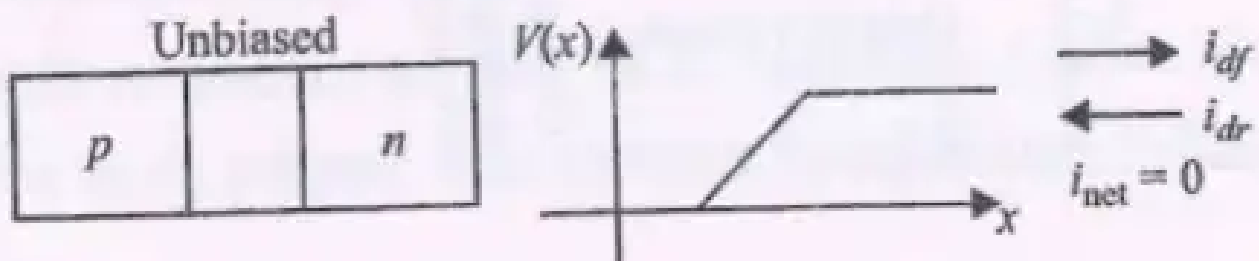


- No external voltage applied.
- Built-in electric field exists due to voltage rise from p to n side.
- Diffusion current  $i_{df}$  and drift current  $i_{dr}$  balance each other.
- Net current  $i_{net} = 0$ .

### Forward Bias

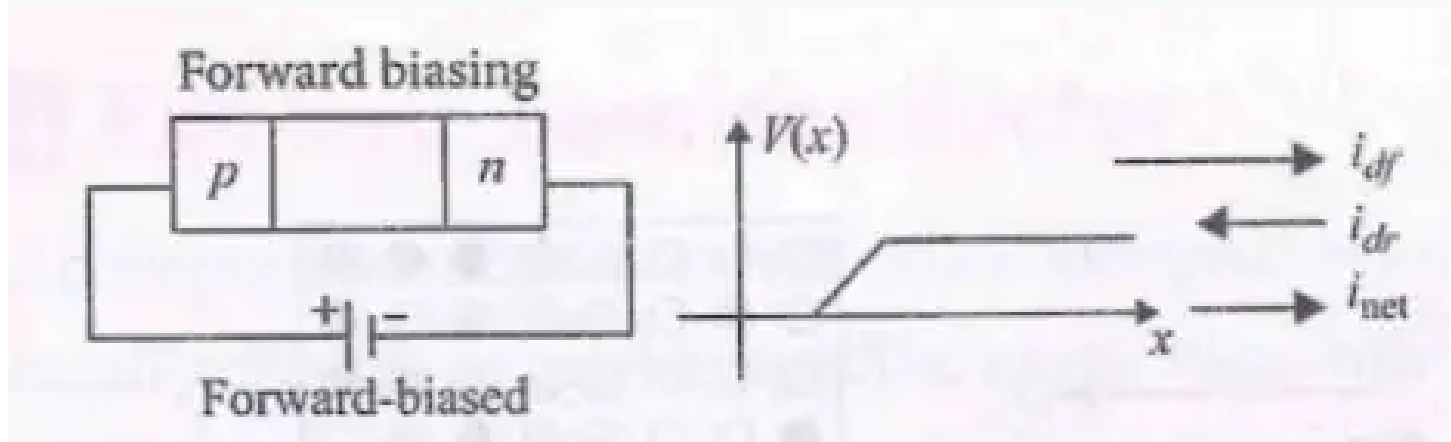

- Positive terminal connected to p-side, negative to n-side.
- Barrier potential decreases, depletion width narrows.
- Low resistance at junction, high current flows.
- Net current  $i_{net}$  flows forward.

### Reverse Bias

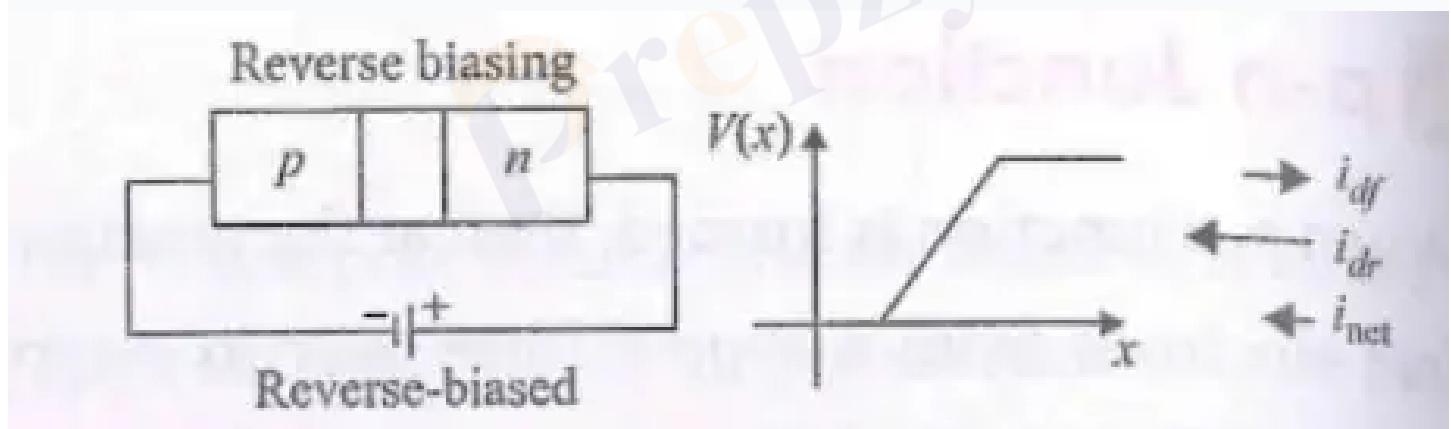

- Positive terminal connected to n-side, negative to p-side.
- Barrier potential increases, depletion width widens.
- High resistance at junction, very low current (leakage current) flows.
- Net current  $i_{net} \approx 0$ , blocks current flow.

### Solved Examples

#### Ex 1

- Determine the effect of forward bias on depletion width: It decreases.
- Determine the effect of reverse bias on barrier potential: It increases.

## Practice Set

- Q1: What happens to the depletion width under forward bias?
  - A) Increases
  - B) Decreases
  - C) No change
  - D) Becomes zero
- Q2: Under reverse bias, the current through the diode is:
  - A) High
  - B) Zero
  - C) Very low (leakage)
  - D) Same as forward bias
- Q3: In reverse bias, the barrier potential:
  - A) Decreases
  - B) Increases
  - C) Remains constant
  - D) Is zero

## Answer Key


- Q1: B - Forward bias narrows the depletion region.
- Q2: C - Reverse bias allows only a tiny leakage current.
- Q3: B - Barrier potential increases under reverse bias.

## Memory Aids

- Forward bias = barrier down, depletion narrows, current flows.
- Reverse bias = barrier up, depletion widens, current blocked.
- Net current zero when unbiased.

## I-V Characteristic of Diode

### Measurement Setup

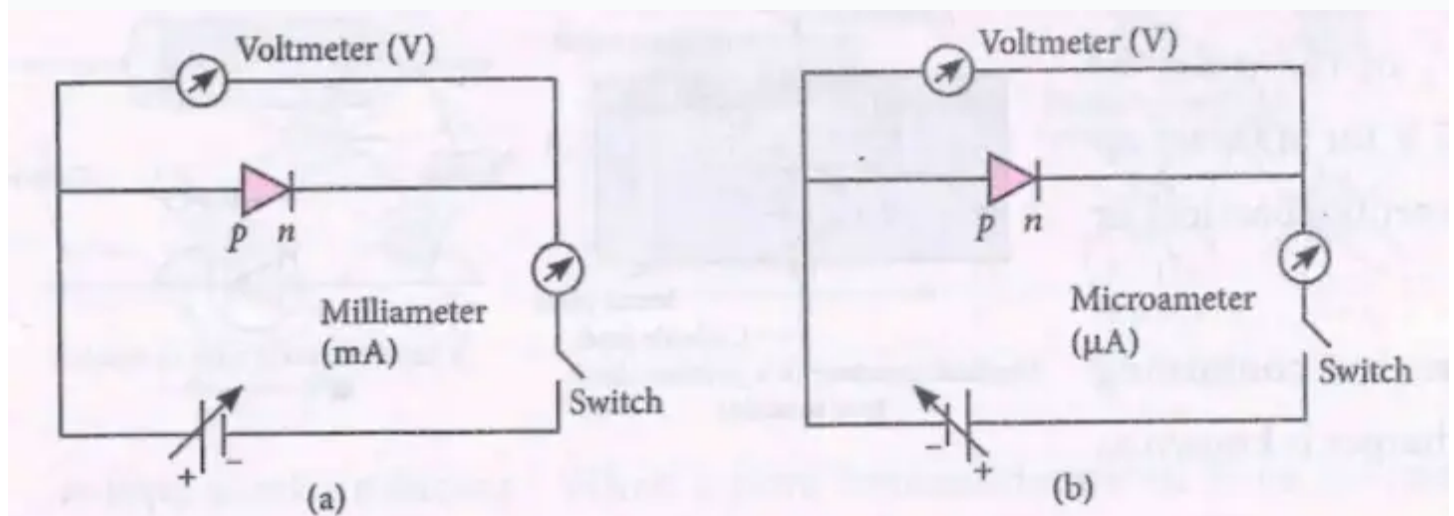


- Diode connected with battery, voltmeter, and current meter (milliammeter or microammeter).
- Switch controls circuit ON/OFF.
- Milliammeter measures higher currents; microammeter measures very low currents.

## Current Equation

- Current through diode:  $I = I_0 \left[ e^{\frac{eV}{nkT}} - 1 \right]$
- Where  $n = 1$  for Ge,  $n = 2$  for Si.
- $I_0$  is the reverse saturation current.
- Dynamic resistance:  $r_d = \frac{\Delta V}{\Delta I}$
- Static (dc) resistance:  $r_{dc} = \frac{V}{I}$

## Zener Diode Characteristics

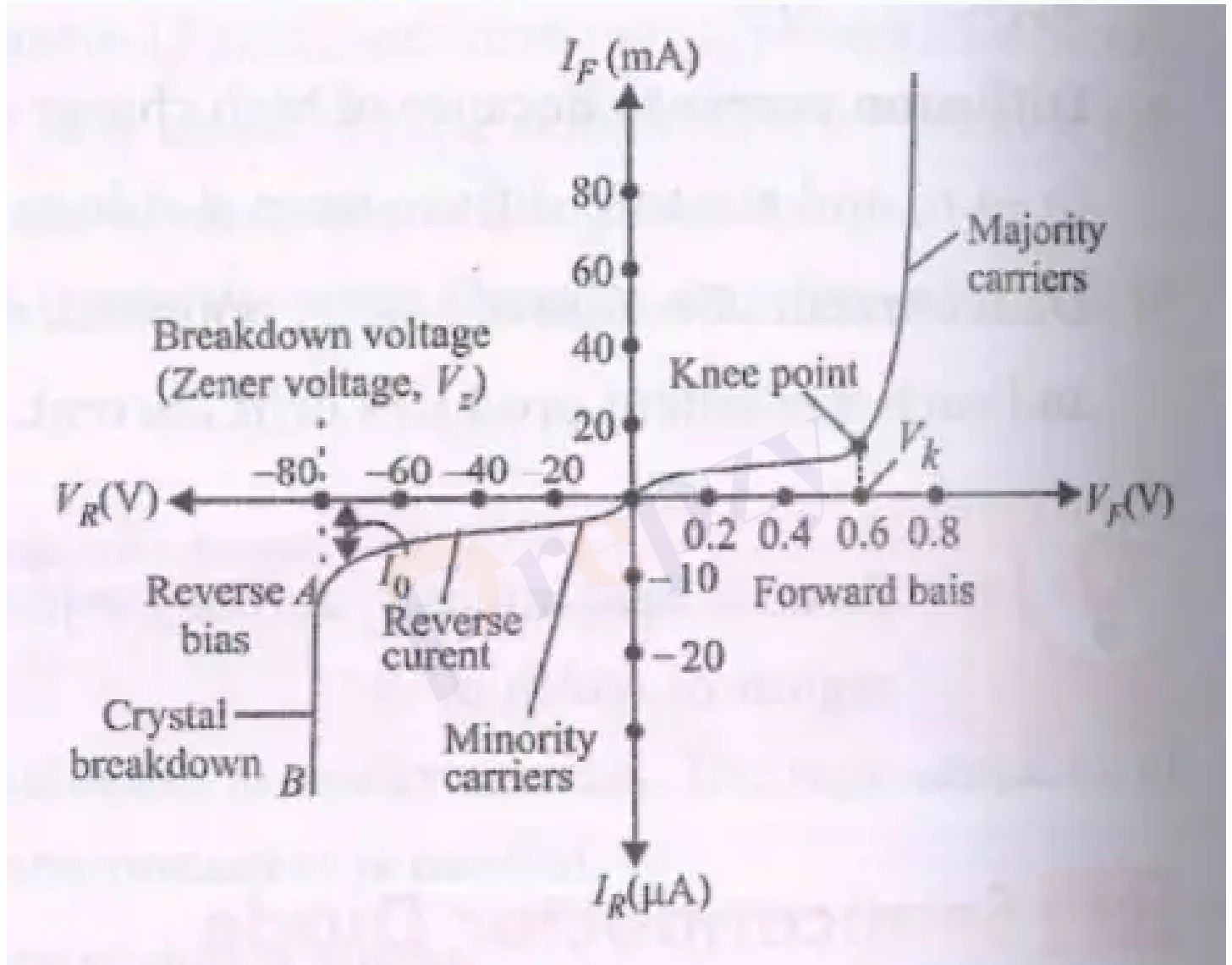

- Forward bias: Current rises rapidly after knee voltage.
- Reverse bias: Small leakage current until breakdown voltage  $V_Z$ .
- At  $V_Z$ , current increases sharply (Zener effect) without damage.
- Used for voltage regulation.

## Solved Examples

### Ex 1

- Calculate current for given  $V$  using  $I = I_0 [e^{eV/nkT} - 1]$ .
- Determine dynamic resistance from  $\Delta V$  and  $\Delta I$  values.

## Practice Set

- Q1: In the diode current equation,  $n$  equals:
  - A) 1 for Si, 2 for Ge
  - B) 2 for Si, 1 for Ge
  - C) 1 for both
  - D) 2 for both
- Q2: Dynamic resistance  $r_d$  is defined as:
  - A)  $V/I$
  - B)  $\Delta V/\Delta I$
  - C)  $I/V$
  - D)  $V \times I$
- Q3: At Zener breakdown voltage, the diode:
  - A) Blocks current
  - B) Allows large reverse current without damage
  - C) Behaves like a resistor
  - D) Stops conducting

## Answer Key

- Q1: B -  $n = 2$  for Si,  $n = 1$  for Ge.
- Q2: B - Dynamic resistance is  $\Delta V/\Delta I$ .
- Q3: B - Zener diode allows large reverse current at breakdown voltage.

## Memory Aids

- Current formula: exponential growth with voltage.
- Dynamic resistance = slope of I-V curve.
- Zener diode stabilizes voltage at breakdown point.


## Application of Junction Diode as a Rectifier

### Rectifier

- Converts AC voltage to DC voltage.
- Uses diode based on forward bias conduction and reverse bias non-conduction.

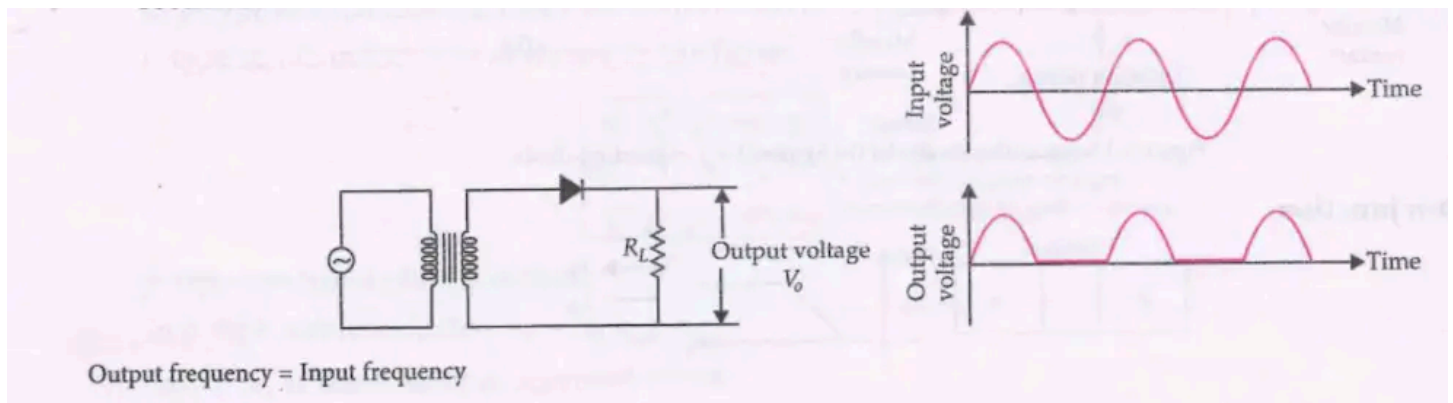
### Half wave rectifier

- Diode conducts during positive half cycle only.
- Output is unidirectional pulsating DC.
- Output frequency = input frequency.


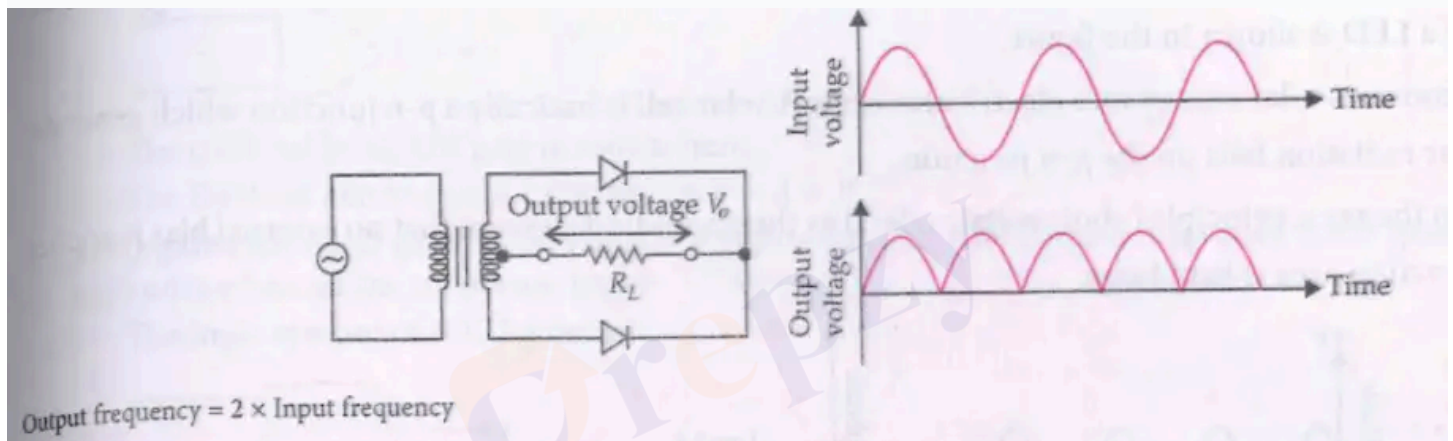
### Full wave rectifier

- Rectifies both positive and negative halves of AC input.
- Uses two diodes and transformer with center tap.
- Output frequency =  $2 \times$  input frequency.
- Output is smoother pulsating DC than half wave.



### Solved Examples

- **Ex 1:** Calculate output frequency of full wave rectifier if input frequency is 50 Hz.  
Solution: Output frequency =  $2 \times 50 = 100$  Hz.
- **Ex 2:** What is the output frequency of half wave rectifier for 60 Hz input?  
Solution: Output frequency = 60 Hz.

### Practice Set

- Q1: What does a rectifier do?
  - Converts DC to AC
  - Converts AC to DC
  - Amplifies AC
  - Blocks AC
- Q2: In half wave rectification, diode conducts during:
  - Negative half cycle
  - Positive half cycle
  - Both half cycles
  - None
- Q3: Output frequency of full wave rectifier for 50 Hz input is:
  - 25 Hz
  - 50 Hz

- C. 100 Hz
- D. 200 Hz

### Answer Key

- Q1: B - Rectifier converts AC voltage to DC voltage.
- Q2: B - Diode conducts only during positive half cycle in half wave rectifier.
- Q3: C - Full wave rectifier output frequency is twice the input frequency.

### Memory Aids

- Half wave: Conducts half cycle, output freq = input freq.
- Full wave: Conducts both halves, output freq =  $2 \times$  input freq.
- Rectifier = AC to DC converter.


## Special Purpose p-n Junction Diodes

### Zener diode

- Heavily doped p-n junction diode.
- Operates in reverse bias.
- Zener voltage remains constant over wide current range.
- Used as voltage regulator.
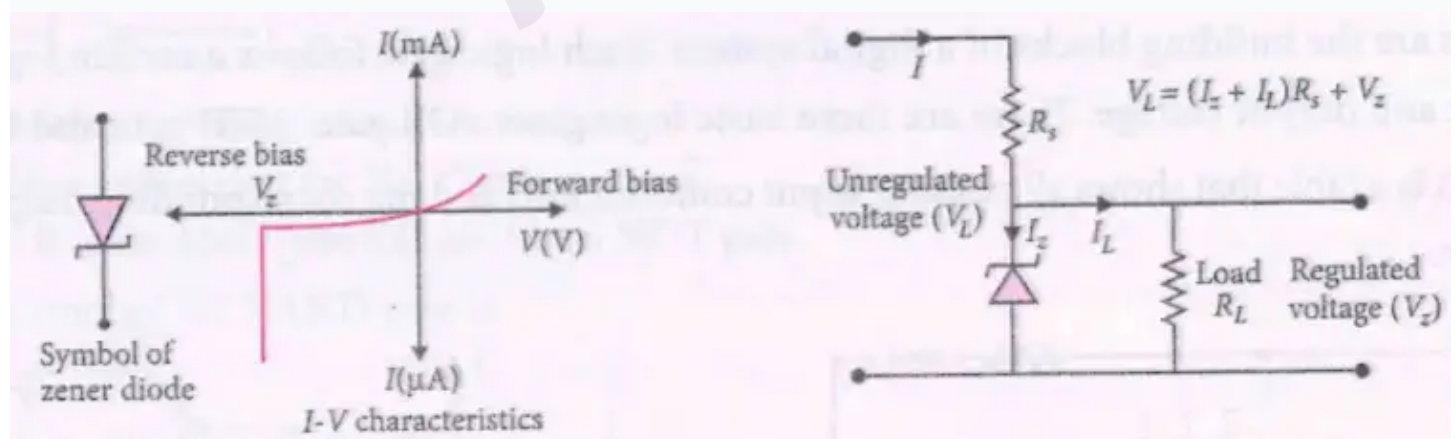
### Zener diode as voltage regulator

- Voltage across Zener diode remains constant despite input voltage changes.
- Voltage drop across series resistor changes to maintain constant voltage.



### Solved Examples

- **Ex 1:** If input voltage increases, what happens to voltage across Zener diode?  
Solution: Voltage across Zener diode remains constant.
- **Ex 2:** What is the role of series resistor in Zener voltage regulator?  
Solution: It drops excess voltage to maintain constant Zener voltage.

## Practice Set

- Q1: Zener diode operates in:
  - A. Forward bias
  - B. Reverse bias
  - C. Both
  - D. None
- Q2: Zener voltage is:
  - A. Variable with current
  - B. Constant over wide current range
  - C. Zero
  - D. Negative
- Q3: In Zener voltage regulator, if input voltage increases:
  - A. Zener voltage increases
  - B. Voltage across series resistor increases
  - C. Load voltage increases
  - D. Zener diode stops conducting

## Answer Key

- Q1: B - Zener diode is operated in reverse bias.
- Q2: B - Zener voltage remains constant over wide current range.
- Q3: B - Voltage across series resistor increases to keep Zener voltage constant.

## Memory Aids

- Zener diode = voltage regulator diode.
- Constant voltage = Zener voltage.
- Series resistor protects diode by dropping excess voltage.

## Photodiode


### Photodiode basics

- Special p-n junction diode with transparent window.
- Operated under reverse bias.
- Generates electron-hole pairs when illuminated with photon energy  $>$  semiconductor band gap.
- Produces photocurrent proportional to light intensity.


### Photodiode symbol and I-V characteristics

- Forward bias: current increases sharply after knee voltage.
- Reverse bias: very low current until breakdown voltage.
- Illumination increases reverse current (photocurrent).


## p-n Junction Diode

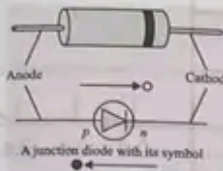


### Biasing of p-n junction

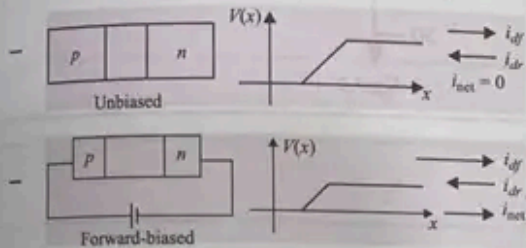

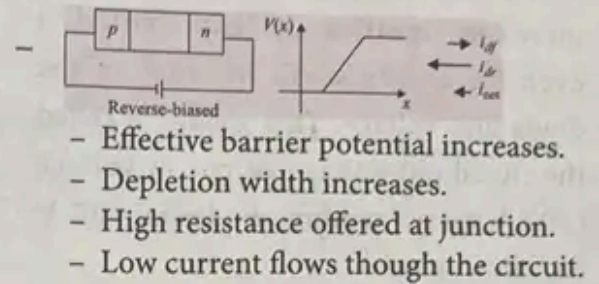- Effective barrier potential decreases.
- Depletion width decreases.
- Low resistance offered at junction.
- High current flows through the circuit.





### I-V characteristic

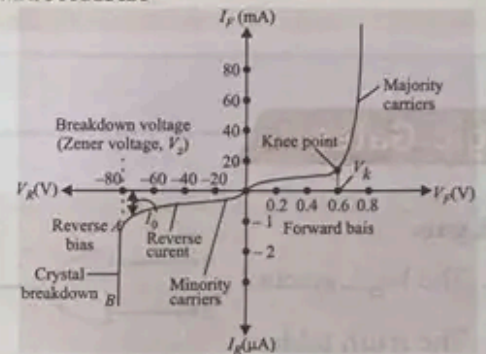
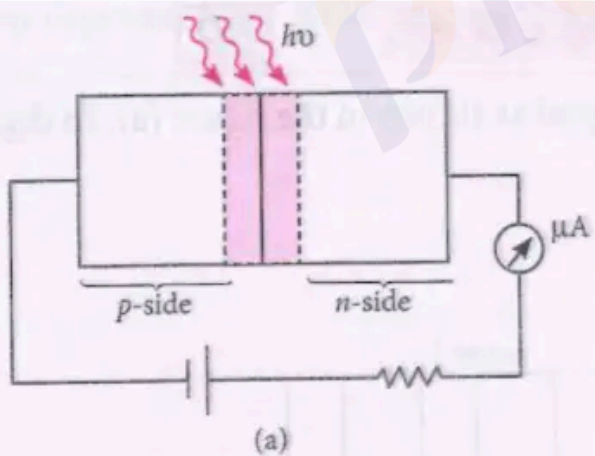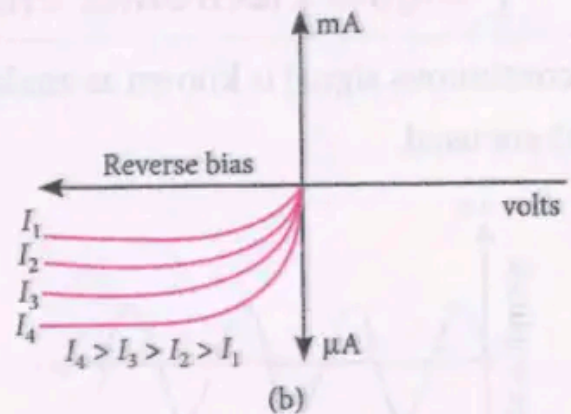
### Photodiode under illumination

- Light generates electron-hole pairs near depletion region.
- Photocurrent flows in reverse bias circuit.
- Current increases with light intensity.



### Solved Examples

- **Ex 1:** What happens to photocurrent if light intensity increases?  
Solution: Photocurrent increases proportionally.
- **Ex 2:** Why is photodiode operated in reverse bias?  
Solution: To increase depletion region width and reduce dark current.

### Practice Set

- Q1: Photodiode is operated in:  
A. Forward bias

- B. Reverse bias
- C. Both
- D. None
- Q2: Photocurrent increases with:
  - A. Voltage only
  - B. Light intensity
  - C. Temperature
  - D. Resistance
- Q3: Photodiode generates electron-hole pairs when:
  - A. Photon energy < band gap
  - B. Photon energy > band gap
  - C. No light
  - D. Forward bias only

### Answer Key

- Q1: B - Photodiode is operated under reverse bias.
- Q2: B - Photocurrent is proportional to light intensity.
- Q3: B - Electron-hole pairs generated when photon energy exceeds band gap.


### Memory Aids

- Photodiode = light-sensitive diode.
- Reverse bias operation for photocurrent.
- Photocurrent  $\propto$  light intensity.

## Light Emitting Diode
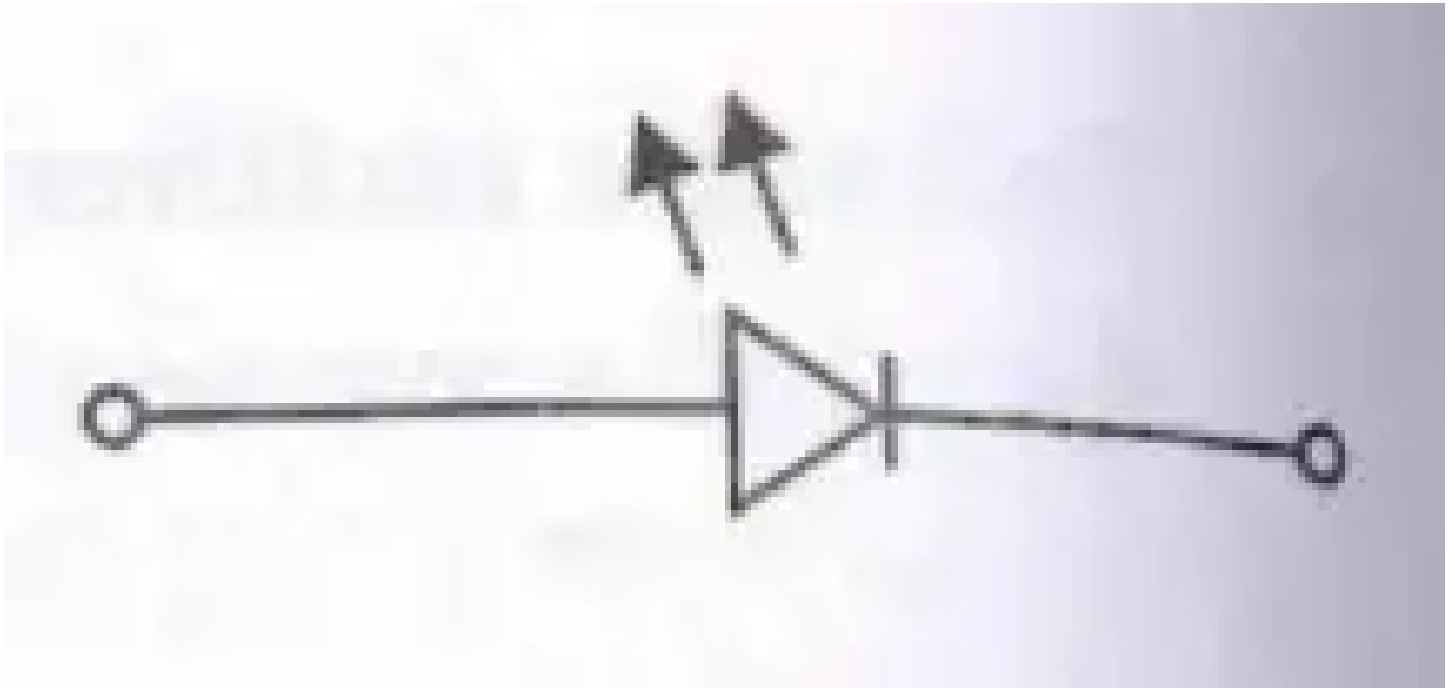
### LED basics

- Converts electrical energy into light energy.
- Heavily doped p-n junction diode.
- Emits light under forward bias by spontaneous radiation.
- Threshold voltage higher than Si diode, varies by color.
- Reverse breakdown voltage ~5 V (low).
- Made from GaAsP for colors, GaAs for infrared.



### Solved Examples

- **Ex 1:** What happens when LED is forward biased?  
Solution: LED emits light.
- **Ex 2:** Which material is used for infrared LED?  
Solution: Gallium arsenide (GaAs).

### Practice Set

- Q1: LED emits light when:  
A. Reverse biased  
B. Forward biased  
C. No bias  
D. Both biases
- Q2: Typical reverse breakdown voltage of LED is:  
A. 0.7 V  
B. 5 V  
C. 12 V  
D. 50 V
- Q3: Material used for colored LEDs is:  
A. Silicon  
B. Gallium arsenide phosphide  
C. Germanium  
D. Copper

### Answer Key

- Q1: B - LED emits light under forward bias.
- Q2: B - Reverse breakdown voltage of LED is about 5 V.
- Q3: B - GaAsP is used for colored LEDs.

### Memory Aids


- LED = Light from forward bias.

- GaAsP for colors, GaAs for IR.
- Low reverse breakdown voltage (~5 V).

## Solar Cell
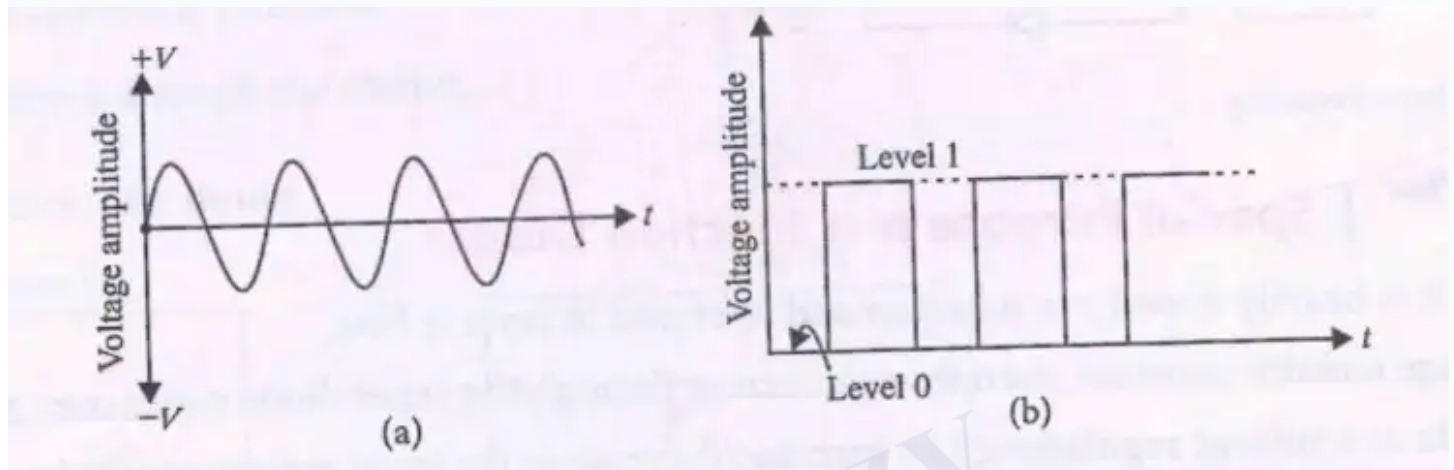
### Solar cell basics

- Converts solar energy into electrical energy.
- p-n junction generates emf when illuminated.
- Works on photovoltaic effect (like photodiode without external bias).
- Large junction area for higher power.



### Solar cell I-V characteristics

- Short circuit current  $I_{sc}$ : max current at zero voltage.
- Open circuit voltage  $V_{oc}$ : max voltage at zero current.
- Current decreases as voltage increases between these points.

### Solved Examples

- **Ex 1:** What is  $I_{sc}$  in solar cell?  
Solution: Maximum current when voltage is zero.
- **Ex 2:** What is  $V_{oc}$  in solar cell?  
Solution: Maximum voltage when current is zero.

### Practice Set

- Q1: Solar cell converts:
  - Electrical to solar energy
  - Solar to electrical energy
  - Heat to electrical energy
  - Electrical to heat energy
- Q2: Photovoltaic effect means:
  - Current flows without light
  - emf generated by light on p-n junction
  - emf generated by heat
  - emf generated by magnetic field
- Q3: In solar cell,  $V_{oc}$  is:
  - Voltage at max current

- B. Voltage at zero current
- C. Current at zero voltage
- D. Current at max voltage

### Answer Key

- Q1: B - Solar cell converts solar energy to electrical energy.
- Q2: B - Photovoltaic effect is emf generation by light on p-n junction.
- Q3: B -  $V_{oc}$  is voltage at zero current.

### Memory Aids

- Solar cell = light to electricity.
- Photovoltaic effect = emf by light.
- $I_{sc}$  and  $V_{oc}$  define performance.


## Digital Electronics and Logic Gates

### Signals

- Analog signal: continuous time-varying signal.
- Digital signal: discrete levels (0 and 1).
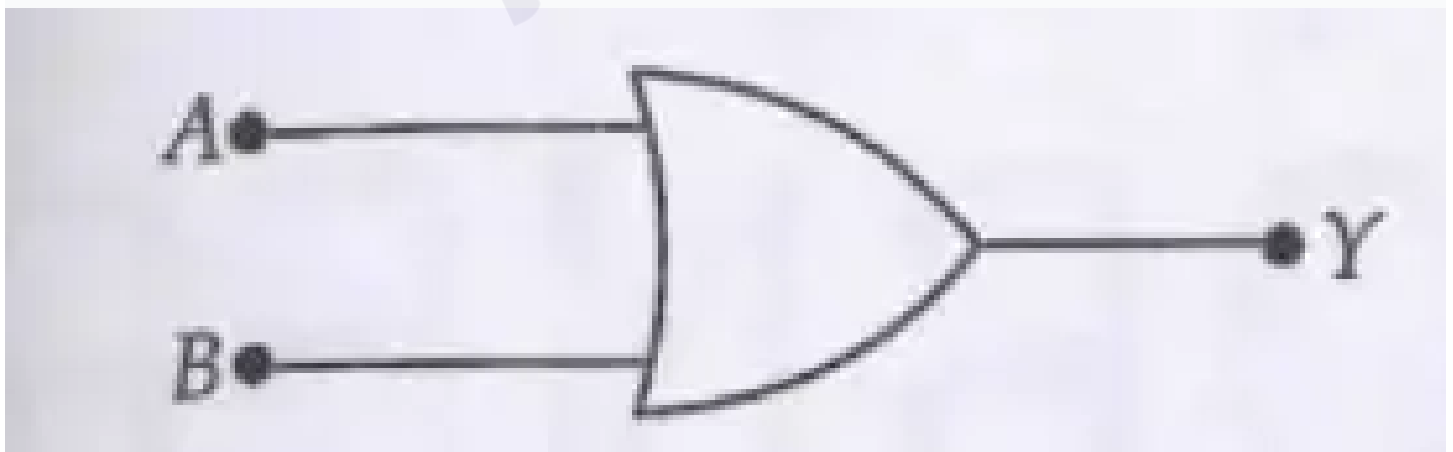
### OR gate

- Two or more inputs, one output.
- Output is high if any input is high.
- Boolean expression:  $Y = A + B$ .



### Solved Examples

- **Ex 1:** OR gate output when  $A=0$ ,  $B=1$ ?  
Solution: Output  $Y=1$ .
- **Ex 2:** Boolean expression for OR gate?  
Solution:  $Y = A + B$ .

## Practice Set

- Q1: OR gate output is high when:
  - A. Both inputs low
  - B. Any input high
  - C. Both inputs high only
  - D. No input high
- Q2: Boolean expression for OR gate is:
  - A.  $Y = A \cdot B$
  - B.  $Y = A + B$
  - C.  $Y = A$
  - D.  $Y = A + B$
- Q3: OR gate output for A=0, B=0 is:
  - A. 0
  - B. 1
  - C. Undefined
  - D. 2

## Answer Key

- Q1: B - Output is high if any input is high.
- Q2: B - Boolean expression is  $Y = A + B$ .
- Q3: A - Output is 0 when both inputs are 0.


## Memory Aids

- OR gate: Output 1 if any input 1.
- Boolean:  $Y = A + B$ .

## AND gate
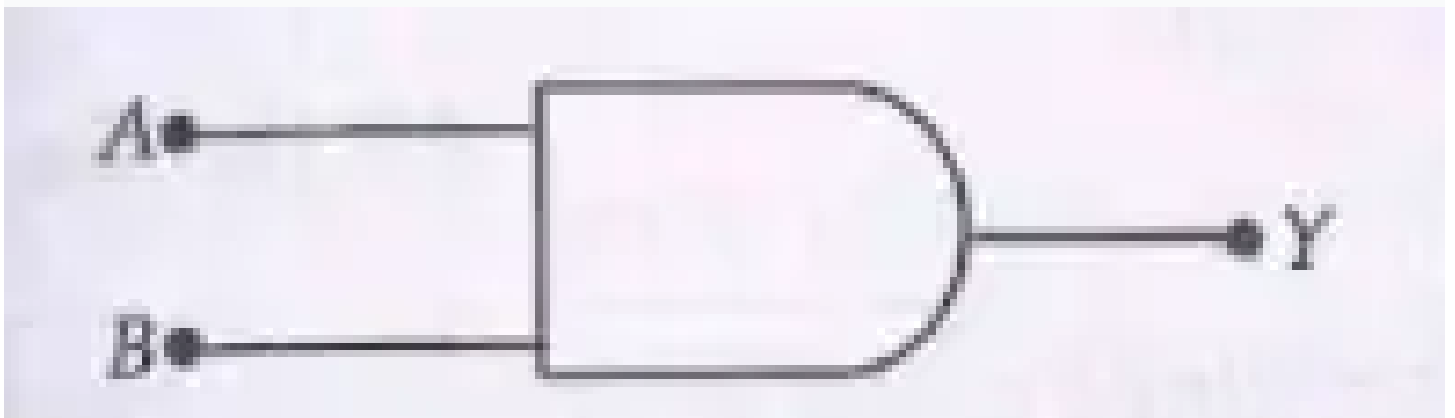
### AND gate basics

- Two or more inputs, one output.
- Output high only if all inputs are high.
- Boolean expression:  $Y = A \cdot B$ .



## Solved Examples

- **Ex 1:** AND gate output when  $A=1$ ,  $B=0$ ?  
Solution: Output  $Y=0$ .
- **Ex 2:** Boolean expression for AND gate?  
Solution:  $Y = A \cdot B$ .

## Practice Set

- Q1: AND gate output is high when:  
A. Any input high  
B. All inputs high  
C. No input high  
D. One input high
- Q2: Boolean expression for AND gate is:  
A.  $Y = A + B$   
B.  $Y = A \cdot B$   
C.  $Y = A$   
D.  $Y = A + B$
- Q3: AND gate output for  $A=1$ ,  $B=1$  is:  
A. 0  
B. 1  
C. Undefined  
D. 2

## Answer Key

- Q1: B - Output is high only if all inputs are high.
- Q2: B - Boolean expression is  $Y = A \cdot B$ .
- Q3: B - Output is 1 when both inputs are 1.


## Memory Aids

- AND gate: Output 1 if all inputs 1.
- Boolean:  $Y = A \cdot B$ .

## NOT gate
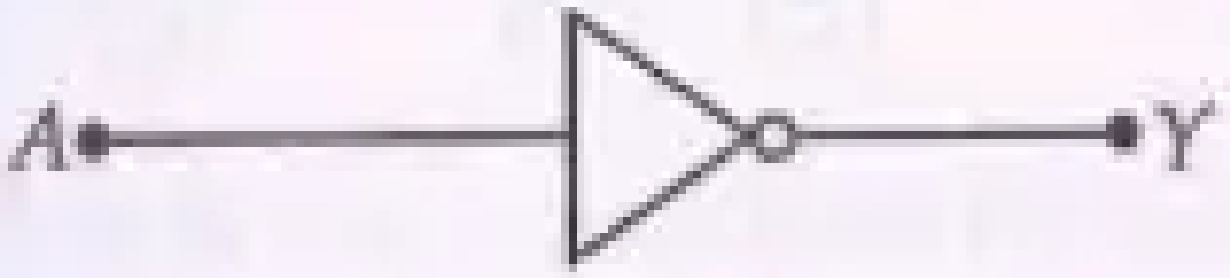
### NOT gate basics

- One input, one output.
- Output is inversion of input.
- Also called inverter.
- Boolean expression:  $Y = A$ .



### Solved Examples

- **Ex 1:** NOT gate output when  $A=0$ ?  
Solution: Output  $Y=1$ .
- **Ex 2:** Boolean expression for NOT gate?  
Solution:  $Y = \bar{A}$ .

### Practice Set

- Q1: NOT gate output for input 1 is:  
A. 1  
B. 0  
C. Undefined  
D. 2
- Q2: Boolean expression for NOT gate is:  
A.  $Y = A$   
B.  $Y = \bar{A}$   
C.  $Y = A + B$   
D.  $Y = A \cdot B$
- Q3: NOT gate has how many inputs?  
A. 1  
B. 2  
C. 3  
D. 0

### Answer Key

- Q1: B - NOT gate inverts input 1 to output 0.
- Q2: B - Boolean expression is  $Y = \bar{A}$ .
- Q3: A - NOT gate has only one input.

### Memory Aids


- NOT gate = inverter.
- Output = opposite of input.

### NAND gate
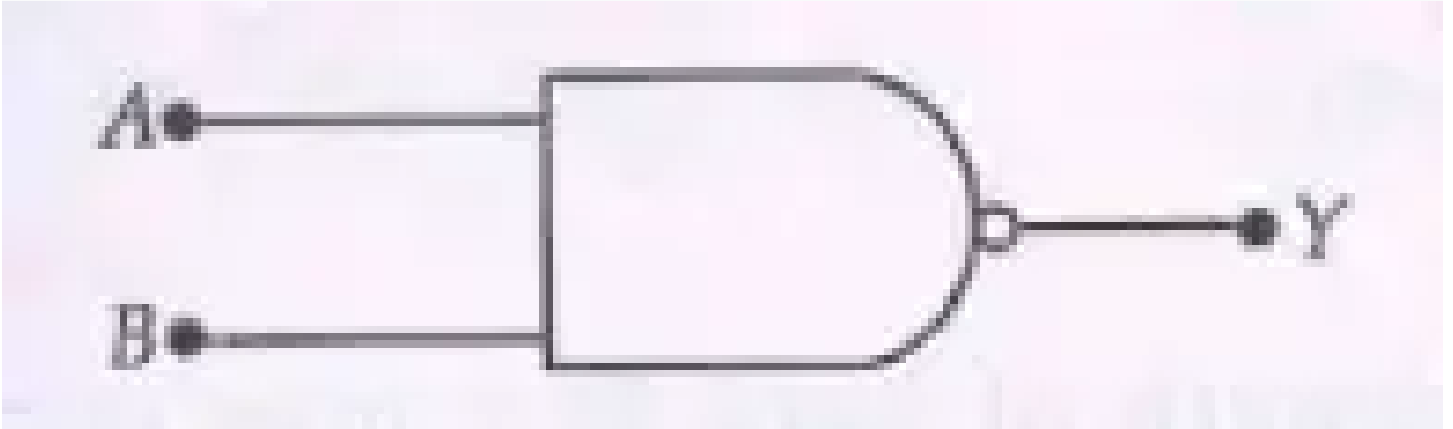
#### NAND gate basics

- AND gate followed by NOT gate.

- Output is negation of AND output.
- Boolean expression:  $A \cdot B$ .



### Solved Examples

- **Ex 1:** NAND gate output when A=1, B=1?  
Solution: Output Y=0.
- **Ex 2:** Boolean expression for NAND gate?

Solution:  $Y = A \cdot B$ .

### Practice Set

- Q1: NAND gate output is low when:  
A. Both inputs low  
B. Both inputs high  
C. Any input low  
D. No input high
- Q2: Boolean expression for NAND gate is:

A.  $Y = A + B$

B.  $Y = A \cdot B$

C.  $Y = A \cdot B$

D.  $Y = A + B$

- Q3: NAND gate output for A=0, B=1 is:  
A. 0  
B. 1  
C. Undefined  
D. 2

### Answer Key

- Q1: B - Output is low only when both inputs are high.
- Q2: B - Boolean expression is negation of AND:  $A \cdot B$ .
- Q3: B - Output is 1 when any input is low.


### Memory Aids

- NAND = AND + NOT.
- Output low only if all inputs high.

## NOR gate
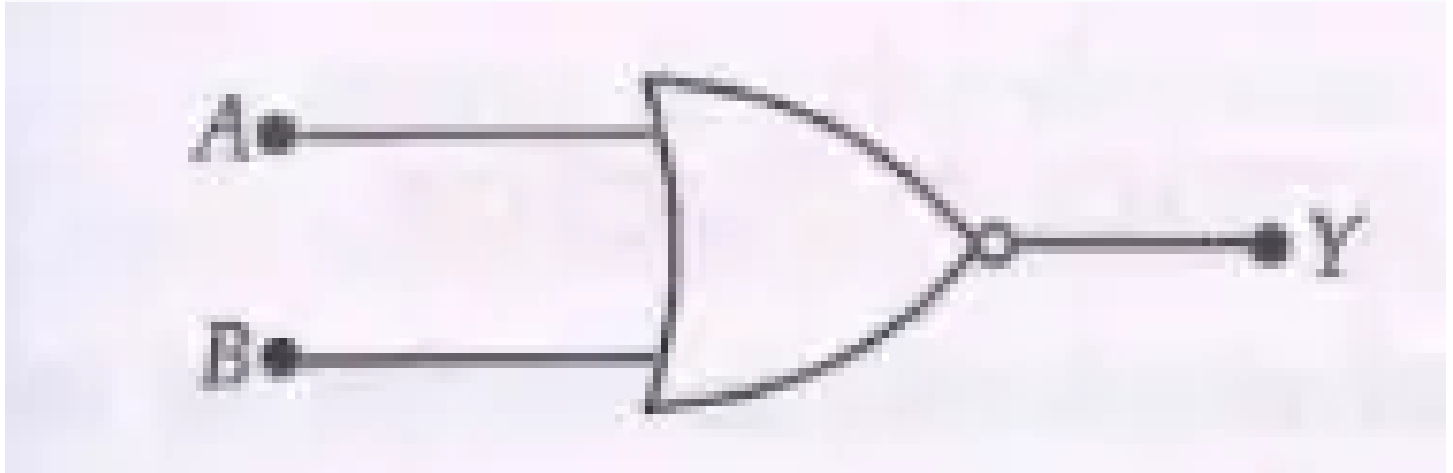
### NOR gate basics

- OR gate followed by NOT gate.
- Output is negation of OR output.
- Boolean expression:  $Y = A + B$ .



### Solved Examples

- **Ex 1:** NOR gate output when A=0, B=0?  
Solution: Output Y=1.
- **Ex 2:** Boolean expression for NOR gate?  
Solution:  $Y = A + B$ .

### Practice Set

- Q1: NOR gate output is high when:  
A. Any input high  
B. Both inputs low  
C. Both inputs high  
D. No input low
- Q2: Boolean expression for NOR gate is:  
A.  $Y = A + B$   
B.  $Y = A + B$   
C.  $Y = A \cdot B$   
D.  $Y = A + B$
- Q3: NOR gate output for A=1, B=0 is:  
A. 0  
B. 1  
C. Undefined  
D. 2

### Answer Key

- Q1: B - Output is high only when both inputs are low.
- Q2: B - Boolean expression is negation of OR:  $A + B$ .
- Q3: A - Output is 0 when any input is high.

## Memory Aids

- $\text{NOR} = \text{OR} + \text{NOT}$ .
- Output high only if all inputs low.

Prepzy